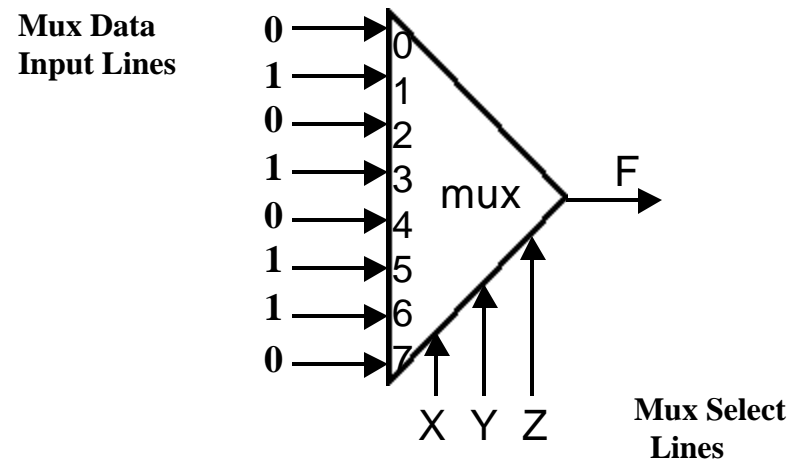


# Implementing n-variable Functions Using $2^n$ -to-1 Multiplexers

- Any n-variable logic function, in canonical sum-of-minterms form can be implemented using a single  $2^n$ -to-1 multiplexer:
  - The n input variables are connected to the mux select lines.
  - For each mux data input line  $I_i$  ( $0 \leq i \leq 2^n - 1$ ):
    - Connect 1 to mux input line  $I_i$  if  $i$  is a minterm of the function.
    - Otherwise, connect 0 to mux input line  $I_i$  (because  $i$  is not a minterm of the function thus the selected input should be 0).

## Example: 3-variable Function Using 8-to-1 mux

- Implement the function  $F(X,Y,Z) = S(1,3,5,6)$  using an 8-to-1 mux.
  - Connect the input variables X, Y, Z to mux select lines.
  - Mux data input lines 1, 3, 5, 6 that correspond to function minterms are connected to 1.
  - The remaining mux data input lines 0, 2, 4, 7 are connected to 0.




# Implementing n-variable Functions Using $2^{n-1}$ -to-1 Multiplexers

- Any n-variable logic function can be implemented using a smaller  $2^{n-1}$ -to-1 multiplexer and a single inverter (e.g. 4-to-1 mux to implement 3 variable functions) as follows:
  - Express function in canonical sum-of-minterms form.
  - Choose n-1 variables as inputs to mux select lines.
  - Construct the truth table for the function, but grouping inputs by selection line values (i.e. select lines as most significant inputs).
  - Determine multiplexer input line i values by comparing the remaining input variable and the function F for the corresponding selection lines value i:
    - Four possible mux input line i values:
      - Connect to 0 if the function is 0 for both values of remaining variable.
      - Connect to 1 if the function is 1 for both values of remaining variable.
      - Connect to remaining variable if function is equal to the remaining variable.
      - Connect to the inverted remaining variable if the function is equal to the remaining variable inverted.

# Example: 3-variable Function Using 4-to-1 mux

- Implement the function  $F(X,Y,Z) = S(0,1,3,6)$  using a single 4-to-1 mux and an inverter.
  - We choose the two most significant inputs X, Y as mux select lines.
  - Construct truth table:

Select Lines Value i	Select Lines			F	Mux Input i
	X	Y	Z		
0	0	0	0	1	1
	0	0	1	1	
1	0	1	0	0	Z
	0	1	1	1	
2	1	0	0	0	0
	1	0	1	0	
3	1	1	0	1	Z'
	1	1	1	0	

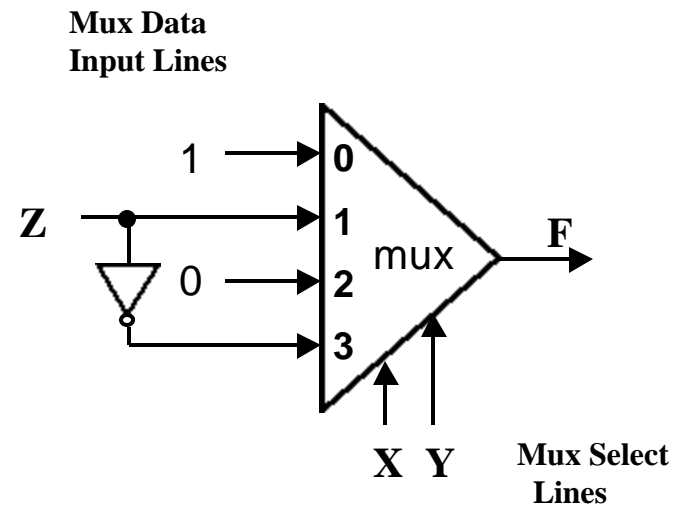


- We Determine multiplexer input line i values by comparing the remaining input variable Z and the function F for the corresponding selection lines value i:
  - when XY=00 the function F=1 (for both Z=0, Z=1) thus mux input0 = 1
  - when XY=01 the function F=Z thus mux input1 = Z
  - when XY=10 the function F=0 (for both Z=0, Z=1) thus mux input2 = 0
  - when XY=11 the function F=Z' thus mux input3 = Z'

# Example: 4-variable Function Using 8-to-1 mux

- Implement the function  $F(x_1, x_2, x_3, x_4) = \sum(0, 1, 2, 3, 4, 9, 13, 14, 15)$  using a single 74151A 8-to-1 mux and an inverter.
  - We choose the three most significant inputs  $x_1, x_2, x_3$  as mux select lines.
  - Construct truth table.
  - Determine multiplexer Data input line  $D_i$  values.

	C	B	A					
$i$	$x_1$	$x_2$	$x_3$	$x_4$	$f$	$f$		$Y$
0	0	0	0	0	1			$D_0 = 1$
	0	0	0	1	1	1		
1	0	0	1	0	1			$D_1 = 1$
	0	0	1	1	1	1		
2	0	1	0	0	1			$D_2 = \bar{x}_4$
	0	1	0	1	0	$\bar{x}_4$		
3	0	1	1	0	0			$D_3 = 0$
	0	1	1	1	0	0		
4	1	0	0	0	0			$D_4 = x_4$
	1	0	0	1	1	$x_4$		
5	1	0	1	0	0			$D_5 = 0$
	1	0	1	1	0	0		
6	1	1	0	0	0			$D_6 = x_4$
	1	1	0	1	1	$x_4$		
7	1	1	1	0	1			$D_7 = 1$
	1	1	1	1	1	1		

(a)

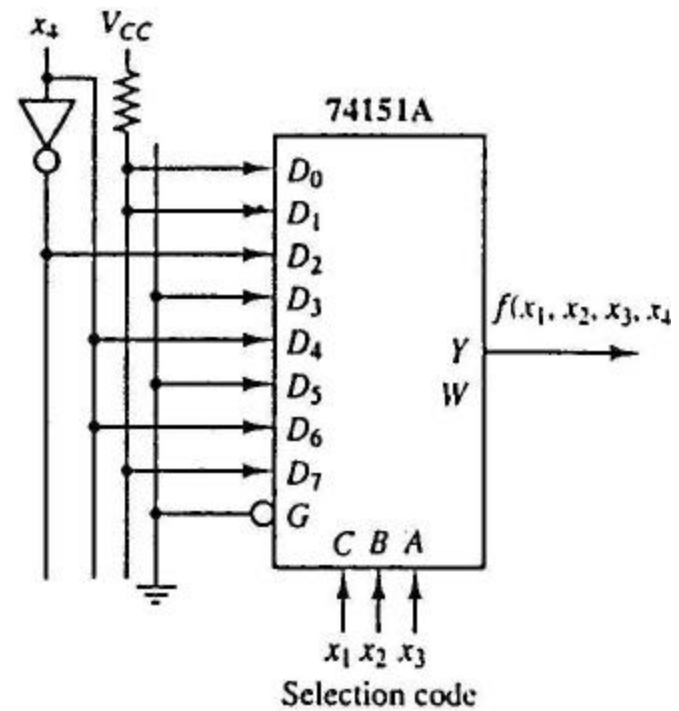

(b)