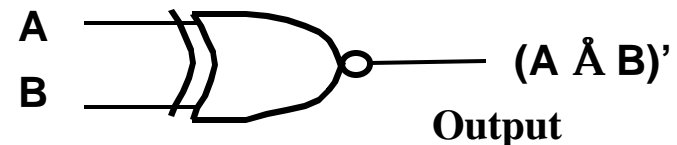


# Combinational Comparators

- Comparing two binary inputs  $A$ ,  $B$  each  $n$  bits for equality (i.e.  $A = B$ ) is a common operation in computers.
- A single output combinational circuit to accomplish this can be constructed using  $n$  2-input XNOR gates for bit-wise comparison plus one  $n$ -input AND gate. The output = 1 if  $A = B$
- This can also be done by subtraction ( $A - B$ ) and checking for a zero result using a single  $n$ -input NOR gate.
- Example: 1-bit comparator:  $A$ ,  $B$  1-bit each.
  - The 1-bit comparison requires a single XNOR gate

Truth table:                      Output


A	B	$(A \oplus B)'$
0	0	1
0	1	0
1	0	0
1	1	1



1-bit comparator
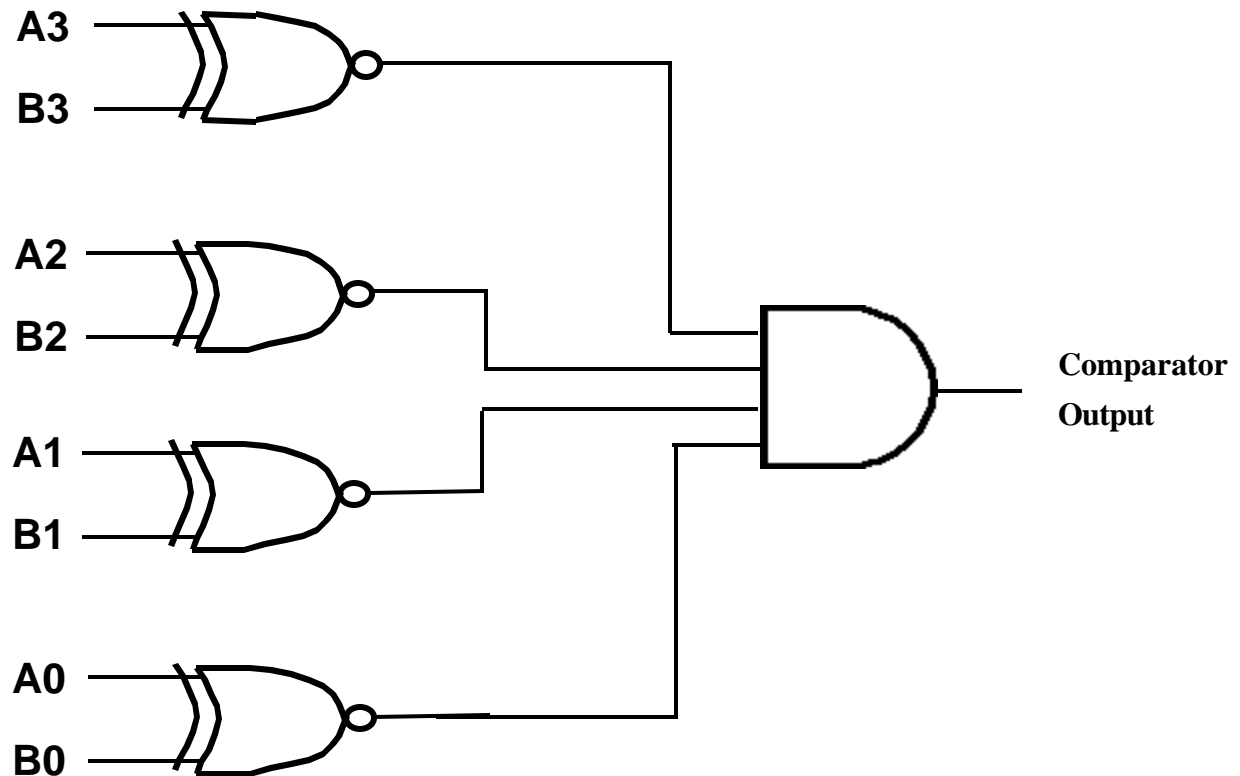
# Example: 4-bit Comparator

Compares  $A = A_3 A_2 A_1 A_0$  with  $B = B_3 B_2 B_1 B_0$   
Output = 1 if  $A = B$




# Combinational Shift Circuits

- An n-bit shift circuit (shifter) has a single n-bit data input A, and a single n-bit output R and a number of control inputs to determine the shift amount (0 to n-1).
- Possible shift operations include:
  - Shift left or right:
    - Arithmetic right shift (the sign bit is shifted in),
    - logic shift (0 is shifted in)
    - Rotate left or right.
- Example: Original data input A = 11011
  - Shift left by one : 10110
  - Logic shift right by one: 01101
  - Arithmetic shift right by one: 11101
  - Rotate left by one: 10111
- Combinational shift circuits are usually constructed using a number of levels of multiplexeres.

# Example: Combinational 8-Bit Right Shifter


Basic Building Block 2-to-1 Mux

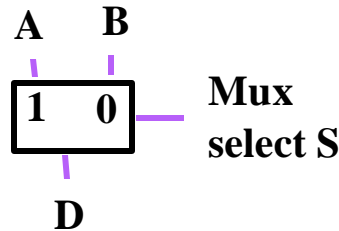

$S_2 S_1 S_0$   
shift amount from 0 to 7

Three levels of Muxes used

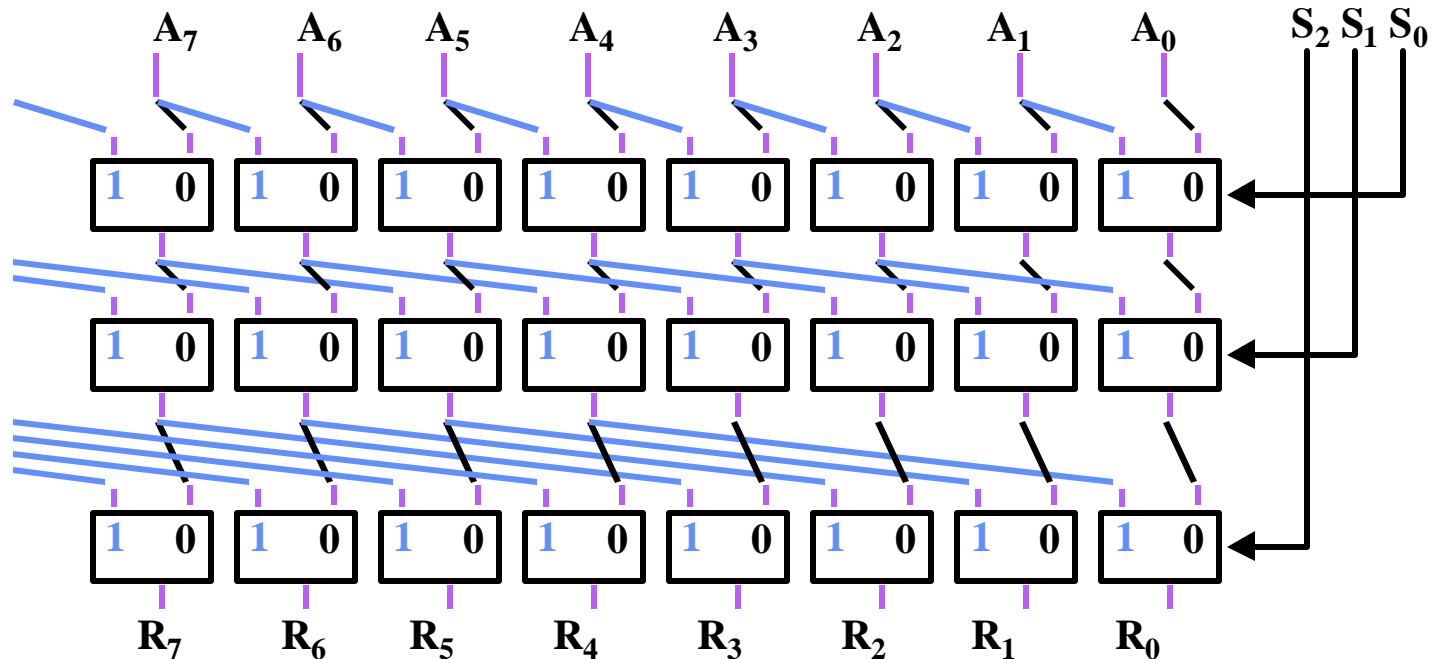Connect to:  
0 for logic  
right shift  
or to A7  
for arithmetic  
right shift  
or to A0 - A6  
for rotate right



- Propagation delay: 2 gate delays per level x 3 levels = 6 gate delays
- How many Mux levels for 32-bit shifter? Propagation delay?