

Clocked Synchronous State-Machines

- Such machines have the characteristics:
 - Sequential circuits designed using flip-flops.
 - All flip-flops use a common clock (clocked synchronous).
 - A machine using n flip-flops (state memory) has n state variables (the outputs of the flip-flops) and 2^n states.
 - In general, the next state and output of the machine both depend on the current state of the machine and on the current input:

Next state = $F(\text{current state, input})$

output = $G(\text{current state, input})$

This type of state machine is called Mealy Machine


- In some cases the next output depends only on the current state and not directly on the current input

Next state = $F(\text{current state, input})$ output = $G(\text{current state})$

Such machines are called Moore machines.

Clocked Synchronous State-Machine Model

(Mealy machine)

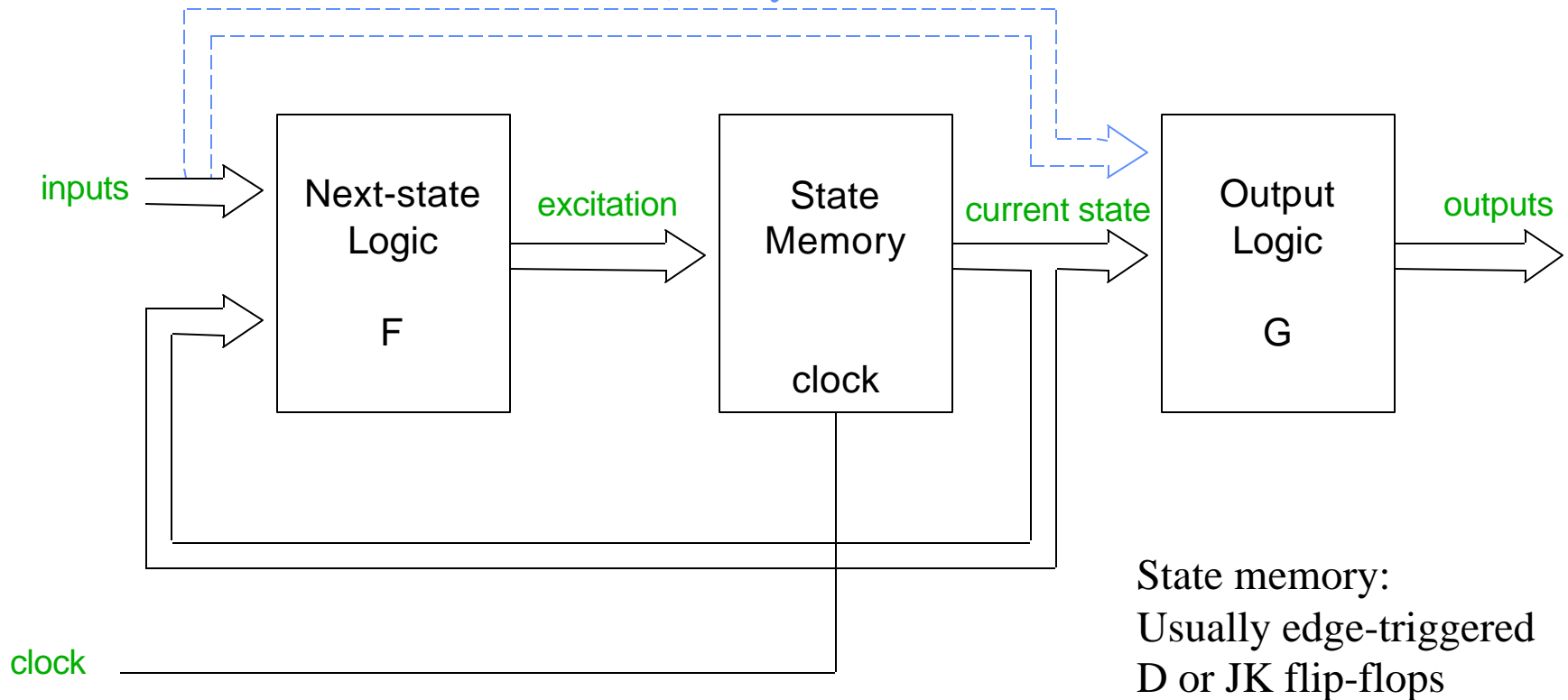

State memory:
Usually edge-triggered
D or JK flip-flops

Moore Machine

Latch/Flip-Flop Characteristic Equations

- The next output of a flip flop (or next state) can be obtained from the function table of each type of flip-flop.
- This latch/flip-flop next output behavior is expressed in as a characteristic function which gives the next state in terms of the current state and output:

$$Q^* = f(Q, \text{inputs})$$

(Q^* is the next state of Q).

- Vary important in state machine analysis and design.

Characteristic Equations

D latch or flip-flop

input	present state	next state
D	$Q(t)$	Q^*
0	0	0
0	1	0
1	0	1
1	1	1

Characteristic Equation:

$$Q^* = D$$

S-R latch

S	R	Q(t)	Q*
0	0	0	0
0	0	1	1
0	1	X	0
1	0	X	1
1	1	X	X

Characteristic Equation:

$$Q^* = S + R' \cdot Q$$

Characteristic Equations

J-K flip-flop

J	K	Q	Q*	
0	0	0	0	
0	0	1	1	= hold
0	1	0	0	
0	1	1	0	= reset
1	0	0	1	
1	0	1	1	= set
1	1	0	1	
1	1	1	0	= flip

Characteristic Equation:

$$Q^* = J \cdot Q' + K' \cdot Q$$

T flip-flop with enable

T	Q	Q*
0	0	0
0	1	1
1	0	1
1	1	0

Characteristic Equation:

$$Q^* = T \cdot Q' + T' \cdot Q$$

Latch/Flip-Flop Characteristic Equations

<u>Device</u>	<u>Characteristic Equations</u>
S-R latch	$Q^* = S + R'.Q$
D latch	$Q^* = D$
Edge-triggered D flip-flop	$Q^* = D$
Master/Slave S-R flip-flop	$Q^* = S + R'.Q$
Master/Slave J-K flip flop	$Q^* = J.Q' + K'.Q$
Edge Triggered J-K flip-flop	$Q^* = J.Q' + K'.Q$
T flip-flop	$Q^* = Q'$
T flip-flop with enable	$Q^* = EN.Q' + EN'.Q$


Clocked Synchronous State-machine Analysis

Given the circuit diagram of a state machine:

- 1 Analyze the combinational logic to determine flip-flop input (excitation) equations: $D_i = F_i(Q, \text{inputs})$
 - The input to each flip-flop is based upon current state and circuit inputs.
- 2 Substitute excitation equations into flip-flop characteristic equations, giving transition equations: $Q_i^* = H_i(D_i)$
- 3 From the circuit, find output equations: $Z = G(Q, \text{inputs})$
 - The outputs are based upon the current state and possibly the inputs.
- 4 Construct a state transition/output table from the transition and output equations:
 - Similar to truth table.
 - Present state on the left side.
 - Outputs and next state for each input value on the right side.
 - Provide meaningful names for the states in state table, if possible.
- 5 Draw the state diagram which is the graphical representation of state table.

State Diagram

Basic Format:

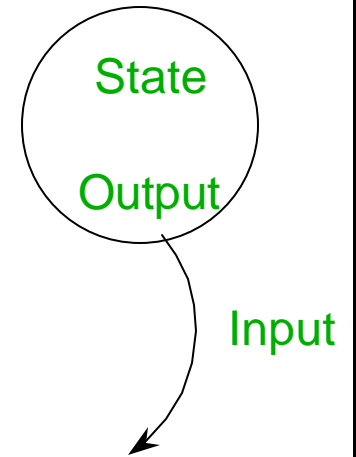


Moore


Format:

Arc = input X

Node = state/output Q

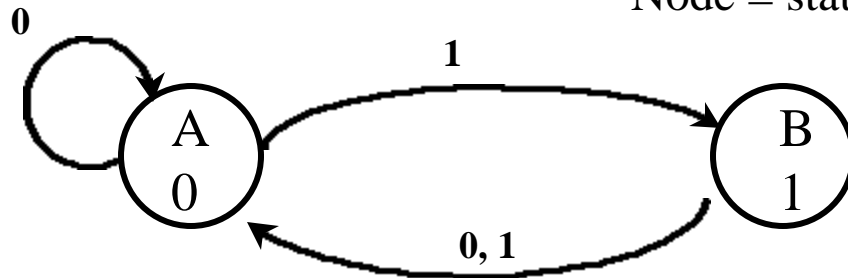

Mealy

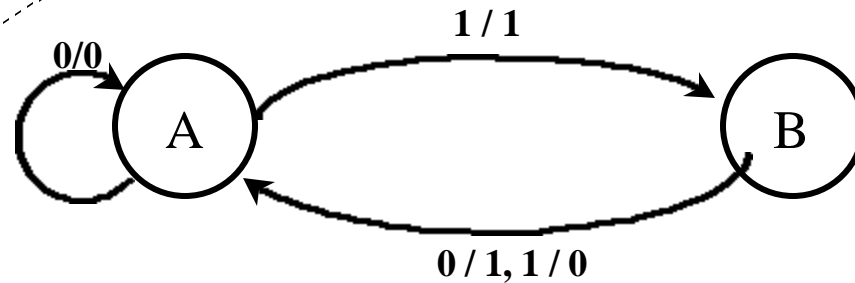


Format:

Arc = input X / mealy output Y

Node = state

State Machine Analysis Example

Analyze the state machine:

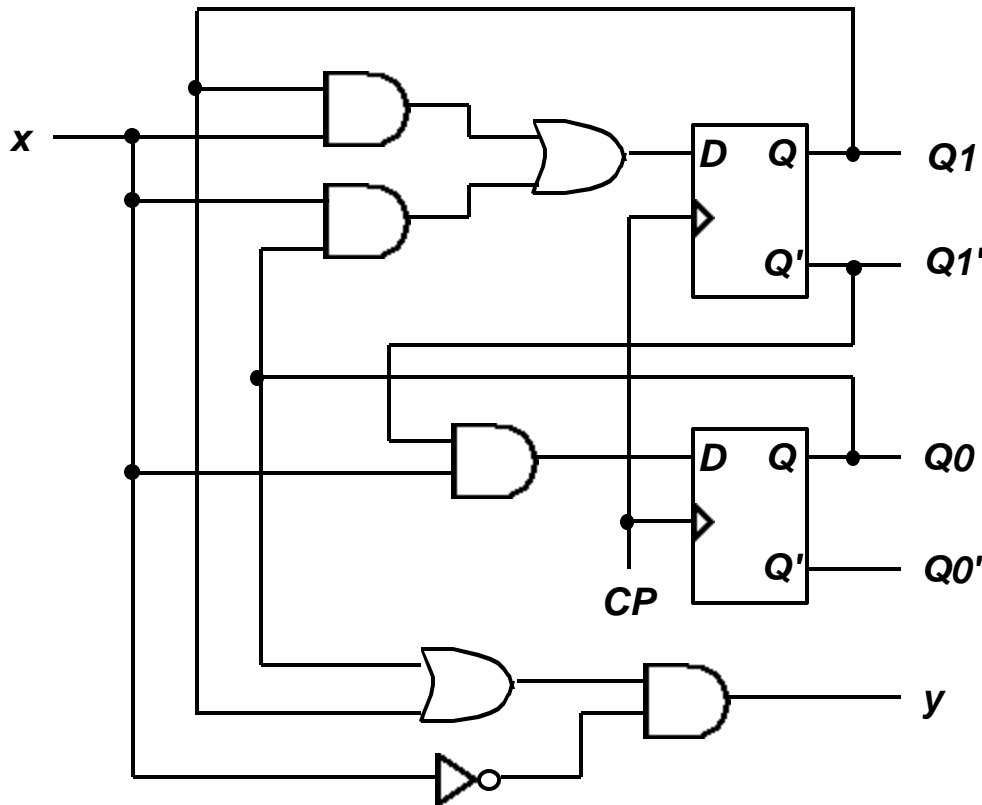

1 Input (or excitation) equations:

$$D0 = Q1' \cdot X$$

$$D1 = Q1 \cdot x + Q0 \cdot x$$

2 Characteristic equations:

$$Q0^* = D0$$

$$Q1^* = D1$$

Find State equations:

$$Q0^* = Q1' \cdot x$$

$$Q1^* = Q1 \cdot x + Q0 \cdot x$$

3 Output equation:

$$y = (Q0 + Q1) \cdot x'$$

This is a Mealy Machine since output = G(current state, input)

State Machine Analysis Example

4 From the *state equations* and *output equation*, construct the *state transition/output table*:

State equations:

$$Q0^* = Q1' \cdot x$$

$$Q1^* = Q1 \cdot x + Q0 \cdot x$$

Output equation:

$$y = (Q0 + Q1) \cdot x'$$

		x ← Input	
		0	1
Q1	Q0		
0	0	00,0	01,0
0	1	00,1	11,0
1	0	00,1	10,0
1	1	00,1	10,0

Current State

Next State when x = 0

Output for current state when x = 0

Next State when x = 1

Output for current state when x = 1

$Q1^* Q0^* , y$

State Machine Analysis Example


5 Draw the state diagram of the state machine.

state transition/output table

Q1	Q0	x	
		0	1
0	0	00,0	01,0
0	1	00,1	11,0
1	0	00,1	10,0
1	1	00,1	10,0

Q1* Q0* , y

state diagram

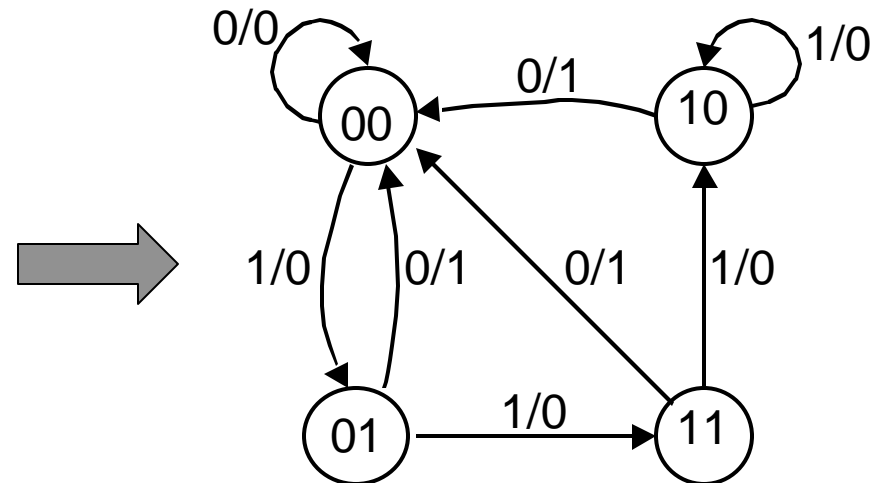

Arc = input x / output y
Node = state