
 

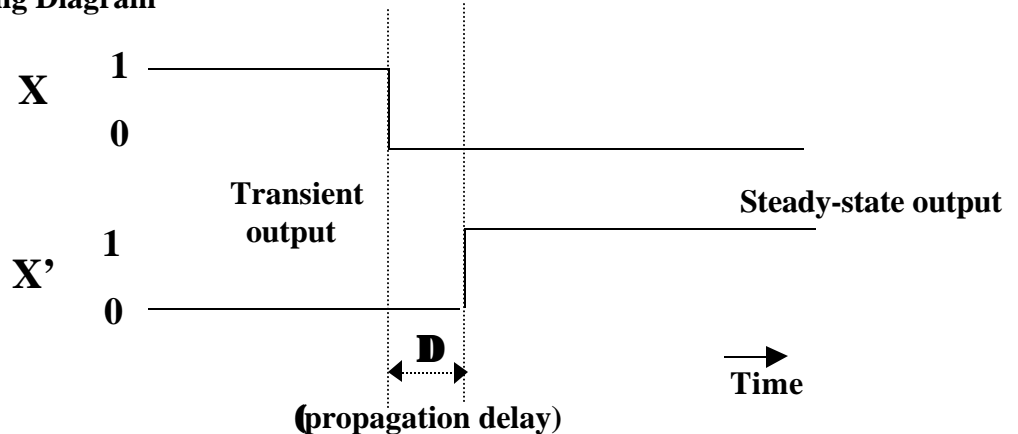
# Combinational Logic Circuit Transient Vs. Steady-state Output

- **Gate propagation delay:** The time between an input change and the corresponding change of the output.
- **Circuit steady-state output:** The output is evaluated when the inputs have been stable for a long time relative to the gate delays.
- **Circuit transient output behavior:** The circuit output when one or more inputs change values.
- **Example:** For an inverter with propagation delay, **D** when input changes from 1 to 0:




Timing Diagram




- The circuit analysis done so far ignores propagation delays and considers only steady-state output when all propagation delays have completed though all the circuit gates.
 
# Combinational Logic Hazards

- **Output glitch:** A momentary unexpected transient output change (short pulse) when an input changes and usually caused by gate propagation delays.
- **Hazards:** A hazard exists in a combinational circuit when it produces an output glitch when one or more inputs change.
- **Types of combinational logic hazards:**
- **Static Hazards:**
  - **Static-1 Hazard:** The output should be 1 but goes momentarily to 0 as a result of an input change. (possible in AND-OR circuits)
  - **Static-0 Hazard:** The output should be 0 but goes momentarily to 1 as a result of an input change. (possible in OR-AND circuits)



 - **Dynamic Hazards:** The output changes more than once as a result of a single input change (impossible in 2-level circuits).




- **Static hazards can be detected and eliminated for 2-level logic circuits using K-maps.**


# Example: Circuit with Static-1 Hazard

- A static-1 hazard exists in the following AND-OR circuit when  $X = 1$ ,  $Y = 1$  and  $Z$  changes from 1 to 0 (assume all gates have propagation delay  $D$ ):


Circuit

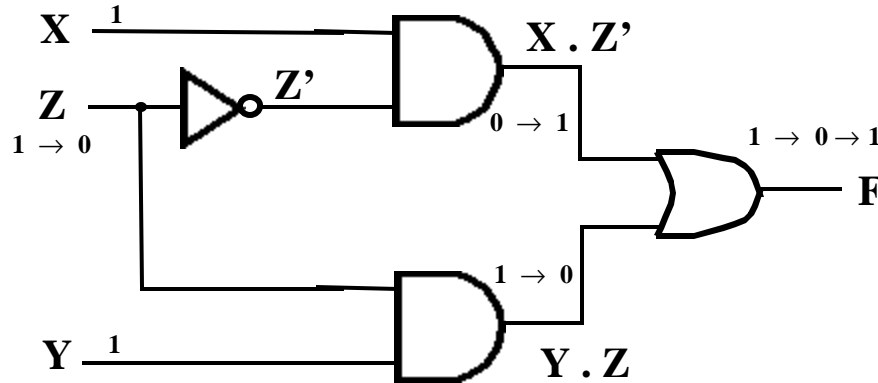

Timing Diagram

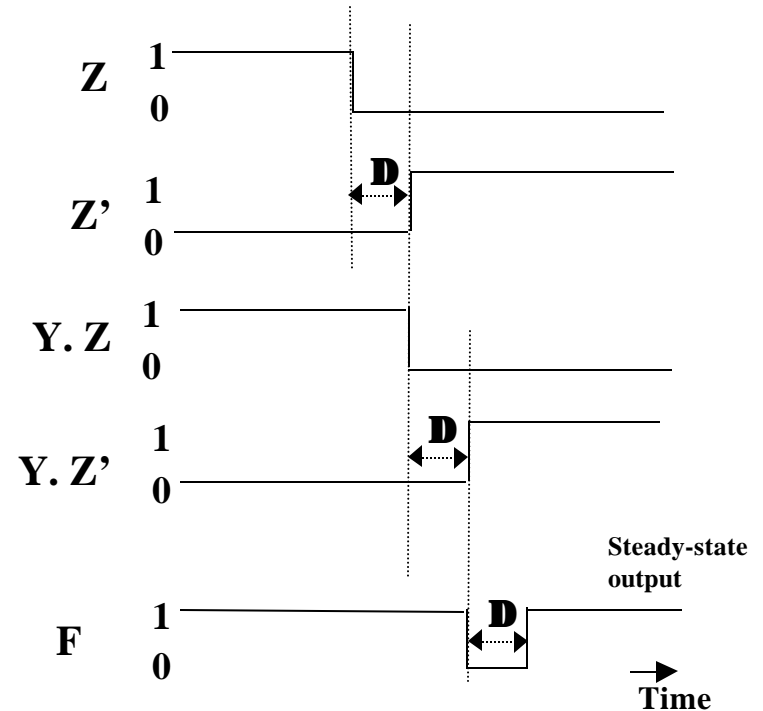


K-map

 

 
# Eliminating Static-1 Hazards Using K-maps

- A static-1 hazard occurs in AND-OR circuits when an input variable and its complement are connected to two different AND gates.
- Static-1 hazards are found using k-maps by finding adjacent 1 cells that are covered by different product terms.
- To eliminate static-1 hazards, additional product terms (prime implicants) are needed to cover such cells thus covering the transition of the variable causing the hazard.
- For in the previous example the static-1 hazard is eliminated by including the additional product term  $X \cdot Y$



$$\text{New } F = X \cdot Z' + Y \cdot Z + X \cdot Y$$

Circuit with static-1 hazard eliminated

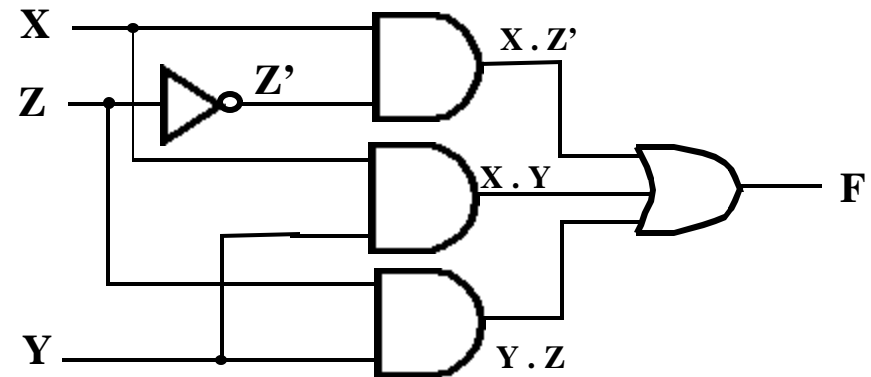

# Eliminating Static-0 Hazards Using K-maps

- A static-0 hazard occurs in OR-AND circuits when an input variable and its complement are connected to two different OR gates.
- The procedure to find and eliminate static-0 hazards using K-maps is done in a dual way to finding static-1 hazards.
- Static-0 hazards are found using k-maps by finding adjacent 0 cells that are covered by different sum terms.
- To eliminate static-0 hazards, additional sum terms (prime implicants) are needed to cover such cells thus covering the transition of the variable causing the hazard.