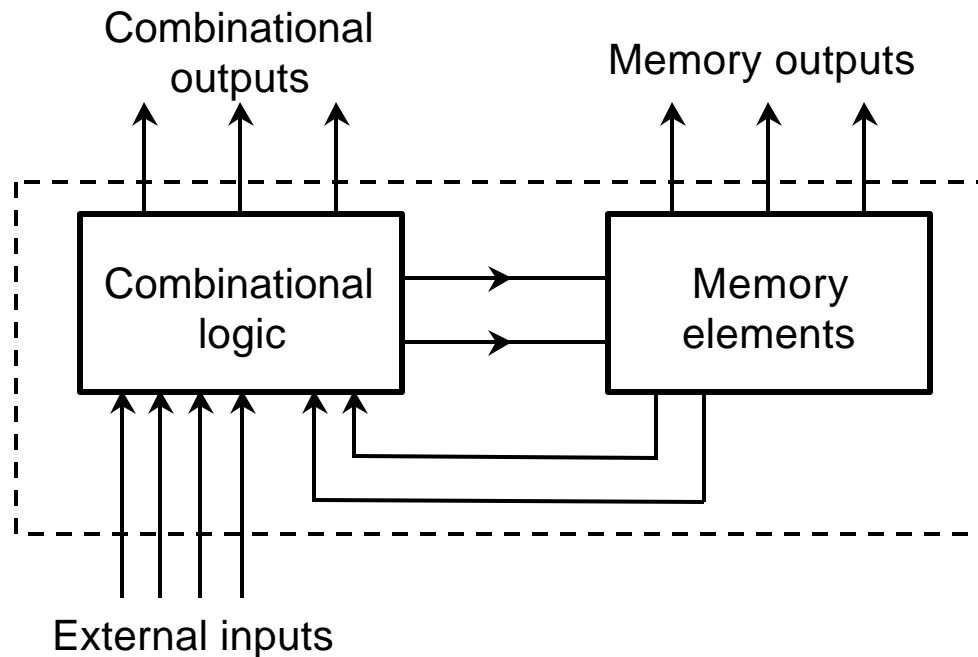


Types of Logic Circuits

- **Combinational logic circuits:**
 - Outputs depend only on its current inputs.
 - A combinational circuit may contain an arbitrary number of logic gates and inverters but no feedback loops.
 - A feedback loop is a connection from the output of one gate to propagate back into the input of that same gate
 - The function of a combinational circuit represented by a logic diagram is formally described using logic expressions and truth tables.
- **Sequential logic circuits:**
 - Outputs depend not only on the current inputs but also on the past sequences of inputs.
 - Sequential logic circuits contain combinational logic in addition to memory elements formed with feedback loops.
 - The behavior of sequential circuits is formally described with state transition tables and diagrams.

Sequential Circuits

- **The general structure of a sequential Circuit:**
 - **Combinational logic + Memory Elements**




Memory element: a device that can remember value indefinitely, or change value on command from its inputs.

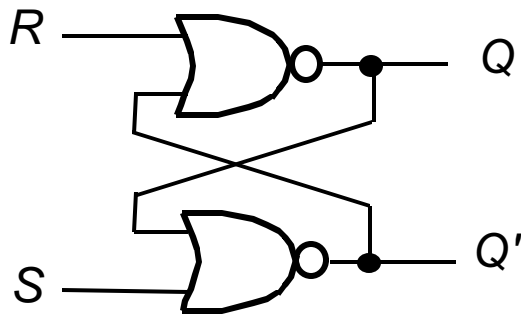- **Examples: latches and flip-flops**

Memory Element Example: S-R (Set-Reset) Latch

- The output Q represents the state of the latch
- When Q is HIGH, the latch is in *SET* state.
- When Q is LOW, the latch is in *RESET* state



S-R latch using
NOR gates

| S | R | Q | Q' | |
|---|---|----|----|---|
| 0 | 0 | NC | NC | No change. Latch remained in present state. |
| 1 | 0 | 1 | 0 | Latch SET. |
| 0 | 1 | 0 | 1 | Latch RESET. |
| 1 | 1 | 0 | 0 | Invalid condition. |

Characteristics or function
table

- **Combinational Circuit Analysis:**

- Start with a logic diagram of the circuit.
- Proceed to a formal description of the function of the circuit using truth tables or logic expressions.


- **Combinational Circuit Synthesis:**

- May start with an informal (possibly verbal) description of the function performed.
- A formal description of the circuit function in terms of a truth table or logic expression.
- The logic expression is manipulated using Boolean (or switching) algebra and optimized to minimize the number of gates needed, or to use specific type of gates.
- A logic diagram is generated based on the resulting logic expression.


Boolean or Switching Algebra

- Set of Elements: {0,1}
- Set of Operations: { . , + , ' } AND (logical multiplication, .), OR (logical addition, +), NOT


| x | y | $x \cdot y$ |
|---|---|-------------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

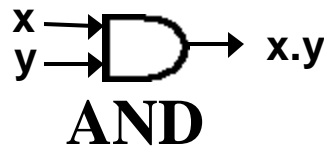

| x | y | $x + y$ |
|---|---|---------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

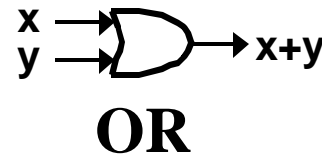

| x | x' |
|---|------|
| 0 | 1 |
| 1 | 0 |

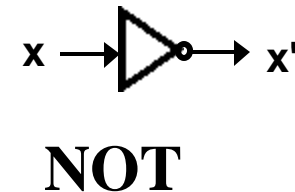

- Symbolic variables such as X used to represent the condition of a logic signal (0 or 1, low or high, on or off).
- Switching Algebra Axioms (or postulates):
 - Minimal set basic definitions (A1-A5, A1'-A5') that are assumed to be true and completely define switching algebra.
 - All other switching algebra theorems (T1-T15) can be proven using these axioms as a starting point.

Switching Algebra Axioms

- **First two axioms state that a variable X can only take on only one of two values:**

$$(A1) \quad X = 0 \quad \text{if} \quad X \neq 1$$

$$(A1') \quad X = 1 \quad \text{if} \quad X \neq 0$$

- **Not Axioms, formally define X' (X prime or NOT X):**

$$(A2) \quad \text{If} \quad X = 0, \text{ then } X' = 1$$

$$(A2') \quad \text{if} \quad X = 1, \text{ then, } X' = 0$$

Note: Above axioms are stated in pairs with only difference being the interchange of the symbols 0 and 1.

Three More Switching Algebra Axioms

- The following three Boolean Algebra axioms state and formally define the AND, OR operations:

$$(A3) \quad 0 \cdot 0 = 0$$

$$(A3') \quad 1 + 1 = 1$$

$$(A4) \quad 1 \cdot 1 = 1$$

$$(A4') \quad 0 + 0 = 0$$

$$(A5) \quad 0 \cdot 1 = 1 \cdot 0 = 0$$

$$(A5') \quad 1 + 0 = 0 + 1 = 1$$

Axioms A1-A5, A1'-A5' completely define switching algebra.

Switching Algebra: Single-Variables Theorems

- **Switching-algebra theorems are statements known to be always true (proven using axioms) that allow us to manipulate algebraic logic expressions to allow for simpler analysis.**

(e.g . $X + 0 = X$ allow us to replace every $X + 0$ with X)

The Theorems: (T1-T5, T1'-T5')

$$(T1) \quad X + 0 = X$$

$$(T1') \quad X \cdot 1 = X \quad (\text{Identities})$$

$$(T2) \quad X + 1 = 1$$

$$(T2') \quad X \cdot 0 = 0 \quad (\text{Null elements})$$

$$(T3) \quad X + X = X$$

$$(T3') \quad X \cdot X = X \quad (\text{Idempotency})$$

$$(T4) \quad (X')' = X$$

(Involution)

$$(T5) \quad X + X' = 1$$

$$(T5') \quad X \cdot X' = 0 \quad (\text{Complements})$$

Perfect Induction

- Most theorems in switching algebra are simple to prove using *perfect induction*:

Since a switching variable can only take the values 0 and 1 we can prove a theorem involving a single variable X by proving it true for $X = 0$ and $X = 1$

Example: To prove (T1) $X + 0 = X$

[$X = 0$] $0 + 0 = 0$ true according to axiom A4'

[$X = 1$] $1 + 0 = 1$ true according to axiom A5'

Switching Algebra:

Two- and Three-Variable Theorems

(Commutativity)

$$(T6) \quad X + Y = Y + X$$

$$(T6') \quad X \cdot Y = Y \cdot X$$

(Associativity)

$$(T7) \quad (X + Y) + Z = X + (Y + Z)$$

$$(T7') \quad (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$$

T6-T7, T6' -T7' are similar to commutative and associative laws for addition and multiplication of integers and reals.

Two- and Three-Variable Theorems (Continued)

(Distributivity)

$$(T8) \quad X \cdot Y + X \cdot Z = X \cdot (Y + Z)$$

$$(T8') \quad (X + Y) \cdot (X + Z) = X + Y \cdot Z$$

- **T8 allows to multiply-out an expression to get sum-of-products form** (*distribute logical multiplication over logical addition*):

For example:

$$V \cdot (W + X) \cdot (Y + Z) = V \cdot W \cdot Y + V \cdot W \cdot Z + V \cdot X \cdot Y + V \cdot X \cdot Z$$

sum-of-products form

- **T8' allows to add-out an expression to get a product-of-sums form** (*distribute logical addition over logical multiplication*):

For example:

$$(V \cdot W \cdot X) + (Y \cdot Z) = (V + Y) \cdot (V + Z) \cdot (W + Y) \cdot (W + Z) \cdot (X + Y) \cdot (X + Z)$$

product-of-sums form

Theorem Proof using Truth Table

- Can use truth table to prove T8 by perfect induction.
- i.e Prove that: $X \cdot Y + X \cdot Z = X \cdot (Y + Z)$

(i) Construct truth table for both sides of above equality.

| x | y | z | y + z | x.(y + z) | x.y | x.z | x.y + x.z |
|---|---|---|-------|-----------|-----|-----|-----------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

(ii) Check that from truth table check that that $X \cdot Y + X \cdot Z = X \cdot (Y + Z)$

This is satisfied because output column values for $X \cdot Y + X \cdot Z$ and output column values for $X \cdot (Y + Z)$ are equal for all cases.

Two- and Three-Variable Theorems (Continued)

(Covering)

$$(T9) \quad X + X \cdot Y = X$$

$$(T9') \quad X \cdot (X + Y) = X$$

(Combining)

$$(T10) \quad X \cdot Y + X \cdot Y' = X$$

$$(T10') \quad (X + Y) \cdot (X + Y') = X$$

- **T9-T10 used in the minimization of logic functions.**

Two- and Three-Variable Theorems (Continued)

(Consensus)

$$(T11) \quad X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$$

$$(T11') \quad (X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$$

- In T11 the term $Y \cdot Z$ is called the consensus of the term $X \cdot Y$ and the term $X' \cdot Z$:
 - If $Y \cdot Z = 1$, then either $X \cdot Y$ or $X' \cdot Z$ must also be 1.
 - Thus the term $Y \cdot Z$ is redundant and may be dropped.

n-Variable Theorems

(Generalized idempotency)

$$(T12) \quad X + X + \dots + X = X$$

$$(T12') \quad X \cdot X \cdot \dots \cdot X = X$$

(DeMorgan's theorems)

$$(T13) \quad (X_1 \cdot X_2 \cdot \dots \cdot X_n)' = X_1' + X_2' + \dots + X_n'$$

$$(T13') \quad (X_1 + X_2 + \dots + X_n)' = X_1' \cdot X_2' \cdot \dots \cdot X_n'$$

(T13), (T13') are probably the most commonly used theorems of switching algebra.

Examples Using DeMorgan's theorems

Example: Equivalence of NAND Gate:

A two-input NAND Gate has the output expression

$$Z = (X \cdot Y)' \text{ using (T13)} \quad Z = (X \cdot Y)' = (X' + Y')$$

The function of a NAND gate can be achieved with an OR gate with an inverter at each input.

Example: Equivalence of NOR Gate

A two-input NOR Gate has the output expression $Z=(X+Y)'$

using (T13') $Z = (X + Y)' = X' \cdot Y'$

The function of a NOR gate can be achieved with an AND gate with an inverter at each input.

n-Variable Theorems (Continued)

(Generalized DeMorgan's theorem)

$$(T14) [F(X_1, X_2, \dots, X_n, +, \cdot)]' = F(X_1', X_2', \dots, X_n', \cdot, +)$$

- States that given any n-variable logic expression its complement can be found by swapping + and \cdot and complementing all variables.

Example:

$$F(W,X,Y,Z) = (W' \cdot X) + (X \cdot Y) + (W \cdot (X' + Z'))$$

$$= ((W)') \cdot X + (X \cdot Y) + (W \cdot ((X)') + (Z)')$$

$$[F(W,X,Y,Z)]' = ((W')' + X') \cdot (X' + Y') \cdot (W' + ((X')') \cdot (Z')')$$

Using T4, $(X')' = X$ simplifies it to:

$$[F(W,X,Y,Z)]' = (W + X') \cdot (X' + Y') \cdot (W' + (X \cdot Z))$$