

Combinational Circuit Minimization

- Canonical sum and product logic expressions do not provide a circuit realization with the minimum number of gates.
- Minimization methods reduce the cost of two level AND-OR, NAND-NAND, OR-AND, NOR-NOR circuits in three ways:

- 1 By minimizing the number of first level gates
- 2 By minimizing the number of inputs of each first-level gate.
- 3 Minimizing the inputs of the second level gate

- Most minimization methods are based on the combining theorems T10, T10':

given product term. Y + given product term. Y' = given product term
(given sum term+ Y). (given sum term + Y') = given sum term

Karnaugh Maps

- A Karnaugh Map or (K-map for short) is a graphical representation of the truth table of a logic function.
- The K-map for an n-input logic function is an array with 2^n cells or squares, one for each input combination or minterm.
- The rows and columns are labeled so that the input combination for any cell is determined from the row and column headings.
- The row and columns of the map are ordered in such a way that each cell differs from an adjacent cell in only one input variable:
 - Thus for an n-variable K-map, each cell has n adjacent cells.
- The K-map for a function is filled by putting:
 - a '1' in the square corresponding to a minterm
 - a '0' otherwise (maybe omitted)


2-Variable K-map

For a 2-variable logic function $F(X,Y)$:

Truth Table:

Row	X	Y	F	Minterm
0	0	0	$F(0,0)$	$X'.Y'$
1	0	1	$F(0,1)$	$X'.Y$
2	1	0	$F(1,0)$	$X.Y'$
3	1	1	$F(1,1)$	$X.Y$

K-map

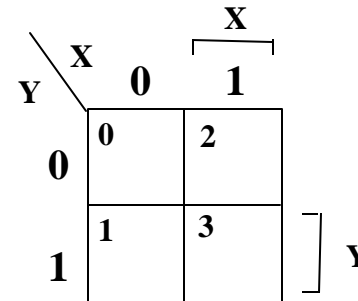


Example: For the function $F(X,Y) = \mathbf{S}_{X,Y} (1,2,3)$

Truth Table:

Row	X	Y	F
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

K-map

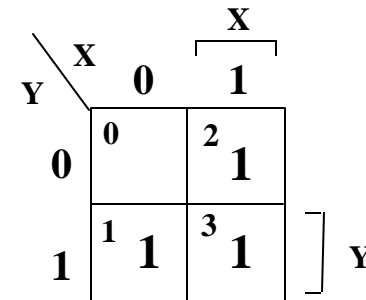


3-Variable K-map

For a 3-variable logic function $F(X,Y,Z)$:

Truth Table:

Row	X	Y	Z	F	Minterm
0	0	0	0	$F(0,0,0)$	$X'.Y'.Z'$
1	0	0	1	$F(0,0,1)$	$X'.Y'.Z$
2	0	1	0	$F(0,1,0)$	$X'.Y.Z'$
3	0	1	1	$F(0,1,1)$	$X'.Y.Z$
4	1	0	0	$F(1,0,0)$	$X.Y'.Z'$
5	1	0	1	$F(1,0,1)$	$X.Y'.Z$
6	1	1	0	$F(1,1,0)$	$X.Y.Z'$
7	1	1	1	$F(1,1,1)$	$X.Y.Z$

K-map

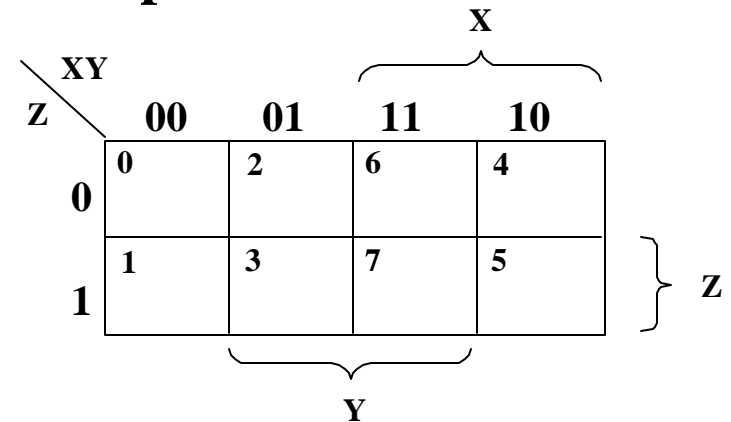


Example: For the function $F(X,Y,Z) = \mathbf{S}_{X,Y,Z}(1,2,5,7)$

Truth Table:

Row	X	Y	Z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

K-map

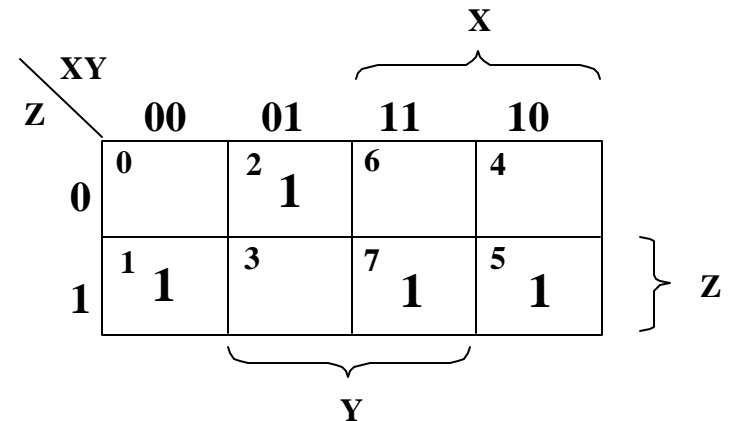


3-Variable K-map (continued)

- There is a horizontal adjacency wrap-around in the 3-variable K-map:

For example:

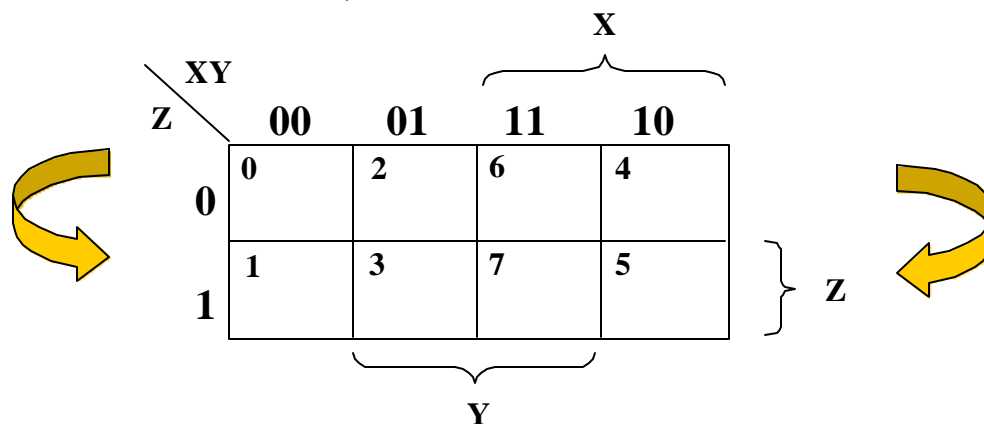- Cell 0 (minterm 0 = $X'.Y'.Z'$) is adjacent to:
 - cell 4 (minterm 4, = $X.Y'.Z'$) by wrap-around.
 - in addition to being adjacent to cells 1, 2 (minterm 1 = $X'.Y'.Z$
minterm 2, = $X'.Y.Z'$)
- Cell 1 (minterm 1, $X'.Y'.Z$) is adjacent to:
 - cell 5 (minterm 5, $X.Y'.Z$) by wrap-around.
 - in addition to being adjacent to cells 0 , 2 (minterm 0 = $X'.Y'.Z'$
minterm 3 = $X'.Y.Z$)




4-Variable K-map

For a 4-variable logic function $F(W,X,Y,Z)$:

Truth Table:


K-map

Row	W	X	Y	Z	F	Minterm
0	0	0	0	0	F(0,0,0,0)	$W'.X'.Y'.Z'$
1	0	0	0	1	F(0,0,0,1)	$W'.X'.Y'.Z$
2	0	0	1	0	F(0,0,1,0)	$W'.X'.Y.Z'$
3	0	0	1	1	F(0,0,1,1)	$W'.X'.Y.Z$
4	0	1	0	0	F(0,1,0,0)	$W'.X.Y'.Z'$
5	0	1	0	1	F(0,1,0,1)	$W'.X.Y'.Z$
6	0	1	1	0	F(0,1,1,0)	$W'.X.Y.Z'$
7	0	1	1	1	F(0,1,1,1)	$W'.X.Y.Z$
8	1	0	0	0	F(1,0,0,0)	$W.X'.Y'.Z'$
9	1	0	0	1	F(1,0,0,1)	$W.X'.Y'.Z$
10	1	0	1	0	F(1,0,1,0)	$W.X'.Y.Z'$
11	1	0	1	1	F(1,0,1,1)	$W.X'.Y.Z$
12	1	1	0	0	F(1,1,0,0)	$W.X.Y'.Z'$
13	1	1	0	1	F(1,1,0,1)	$W.X.Y'.Z$
14	1	1	1	0	F(1,1,1,0)	$W.X.Y.Z'$
15	1	1	1	1	F(1,1,1,1)	$W.X.Y.Z$

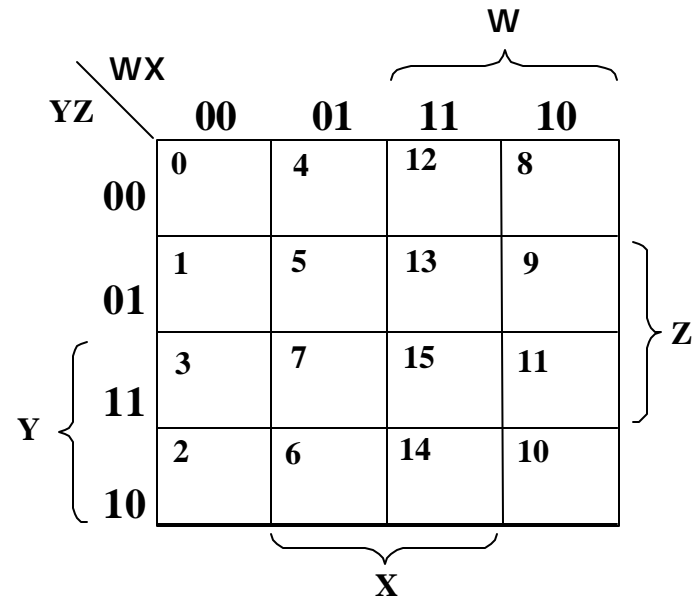

4-Variable K-map (continued)

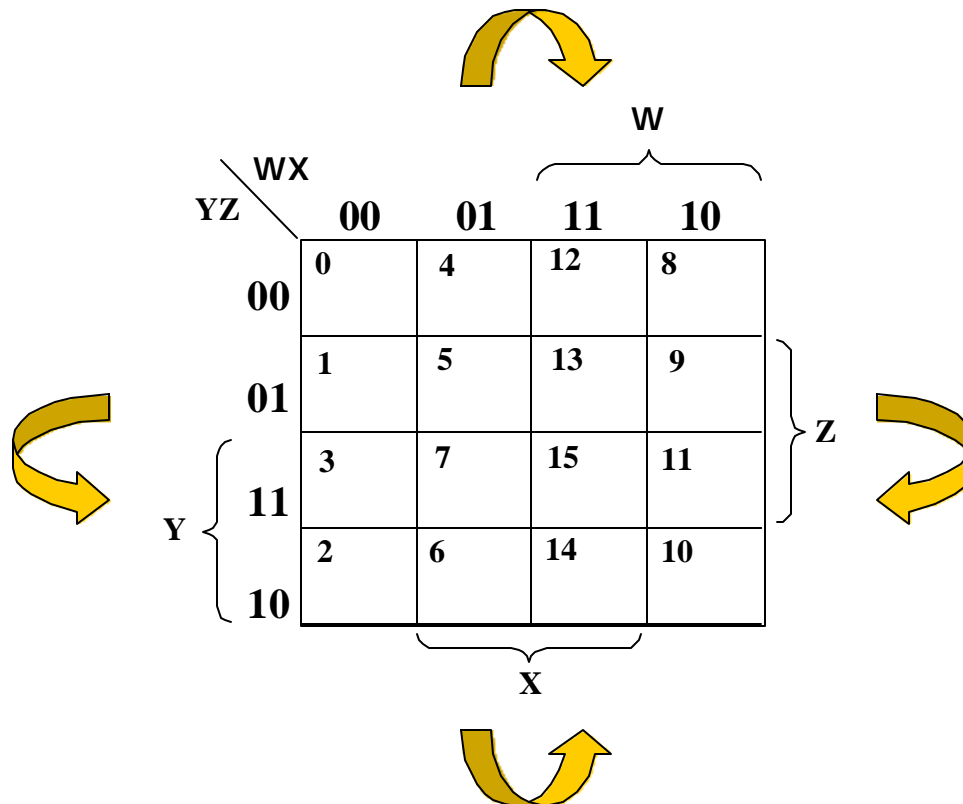- There are 2 adjacency wrap-arounds in the 4-variable K-map : a horizontal wrap-around and a vertical wrap-around.
- Every cell thus has 4 neighbours. For example, cell 0 corresponding to minterm 0 is adjacent to: cells 1, 2, 4, 8



4-Variable K-map Example

For the function $F(W,X,Y,Z) = \mathbf{S}_{W,X,Y,Z} (5,7,12,13,14,15)$

Truth Table:

Row	W	X	Y	Z	F
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

K-map

		W			
		}			
YZ	WX	00	01	11	10
	00	0	4	12 1	8
01	1	5 1	13 1	9	
Y	11	3	7 1	15 1	11
	10	2	6	14 1	10
		} X			

Minimizing Sum of Products using K-maps

- Each input combination with “1” in a Karnaugh map or truth table correspond to a minterm in the function’s canonical sum representation.
- Pairs of adjacent “1” cells in the Karnaugh map indicate minterms that differ in only one variable.
- Using the generalization of T10, such adjacent minterm pairs can be combined into a single product term.
- In general, one can simplify a logic function by combining pairs of adjacent 1-cell minterms and writing a sum of products expression to cover all of the 1-cells.

K-Map Minimization Rules and Definitions

- A minimal sum of a logic function $F(X_1, X_2, \dots, X_n)$ is a sum-of-products expression for F such that no other similar expression for F has fewer product terms, and other expressions with the same number of product terms have at least the same number of literals.
- A set of 2^i 1-cells are combined into a single square or rectangle if i variables take all 2^i possible combinations within the set while the remaining variables have the same value.
- The corresponding product term for the combined cells has $n-i$ literals.
- Only the variables that have the same value appear in the resulting product term:
 - A variable in the resulting product term is complemented if it appears as 0 in all the 1-cells, and uncomplemented if it appears as 1.

Minimization Using K-maps

- **Group or combine as many adjacent 1-cells as possible:**
 - The larger the group is, the fewer the number of literals in the resulting product term.
 - Each group of combined adjacent 1-cells must have a number of cells equal to *powers of two*: 1, 2, 4, 8, ...
 - Grouping 2 adjacent 1-cells eliminates 1 variable, grouping 4 1-cells eliminates 2 variables, grouping 8 1-cells eliminates 3 variables, and so on. In general, grouping 2^n squares eliminates n variables.
- **Select as few groups as possible to cover all the 1-cells (minterms) of the function:**
 - The fewer the groups, the fewer the number of product terms in the minimized function.

3-Variable K-map Minimization Example

- Using K-map, find a minimal sum of products (SOP) expression for the function:

$$F(X,Y,Z) = \mathbf{S}_{X,Y,Z} (1,2,5,7)$$

K-map

		X			
		00	01	11	10
Z	0	0 0	2 1	6	4
	1	1 1	3	7 1	5 1
		Y			

} Z

Truth Table


Row	X	Y	Z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

3-Variable K-map Minimization Example

- Using K-map, find a minimal sum of products (SOP) expression for the function:

$$F(X,Y,Z) = \mathbf{S}_{X,Y,Z} (1,2,5,7)$$

K-map

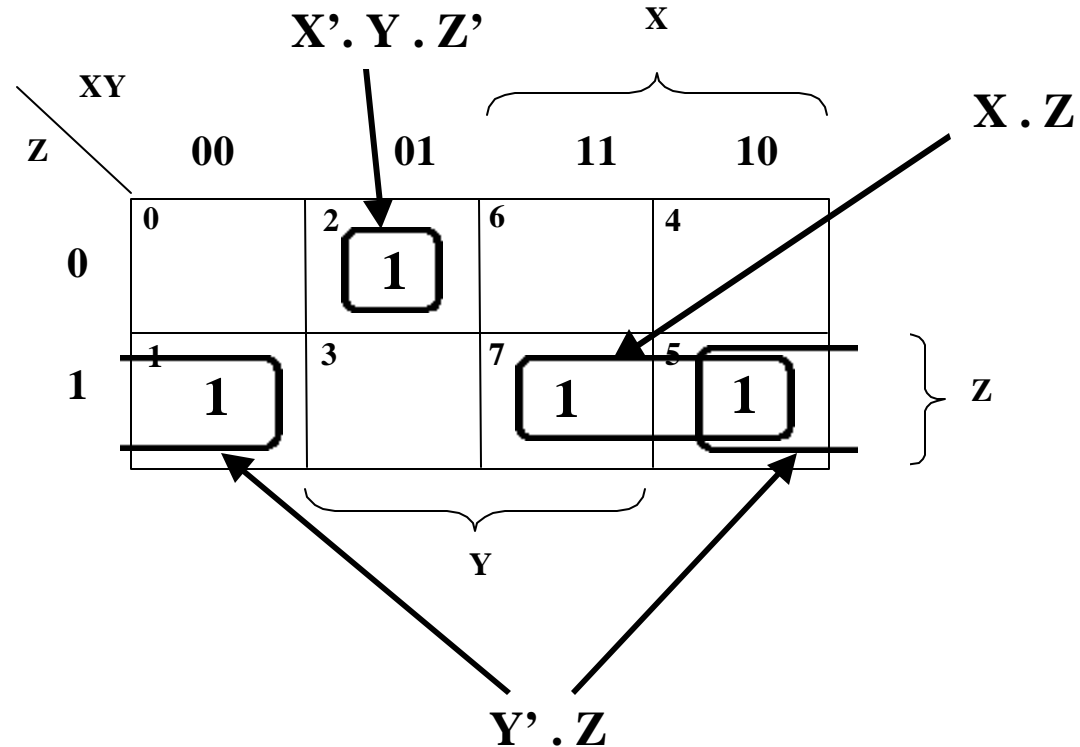

Truth Table

Row	X	Y	Z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

Minimum SOP for F = $X'.Y.Z' + X.Z + Y'.Z$

3-Variable K-map Minimization Example

- Using K-map, find a minimal sum of products (SOP) expression for the function:

$$F(X,Y,Z) = \mathbf{S}_{X,Y,Z} (0,1,4,5, 6)$$

K-map

		X			
		00	01	11	10
Z	0	0 1	2	6 1	4 1
	1	1 1	3	7	5 1

Y

Z

Truth Table


Row	X	Y	Z	F
0	0	0	0	1
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

3-Variable K-map Minimization Example

- Using K-map, find a minimal sum of products (SOP) expression for the function:

$$F(X,Y,Z) = \sum_{X,Y,Z} (0,1,4,5, 6)$$

K-map

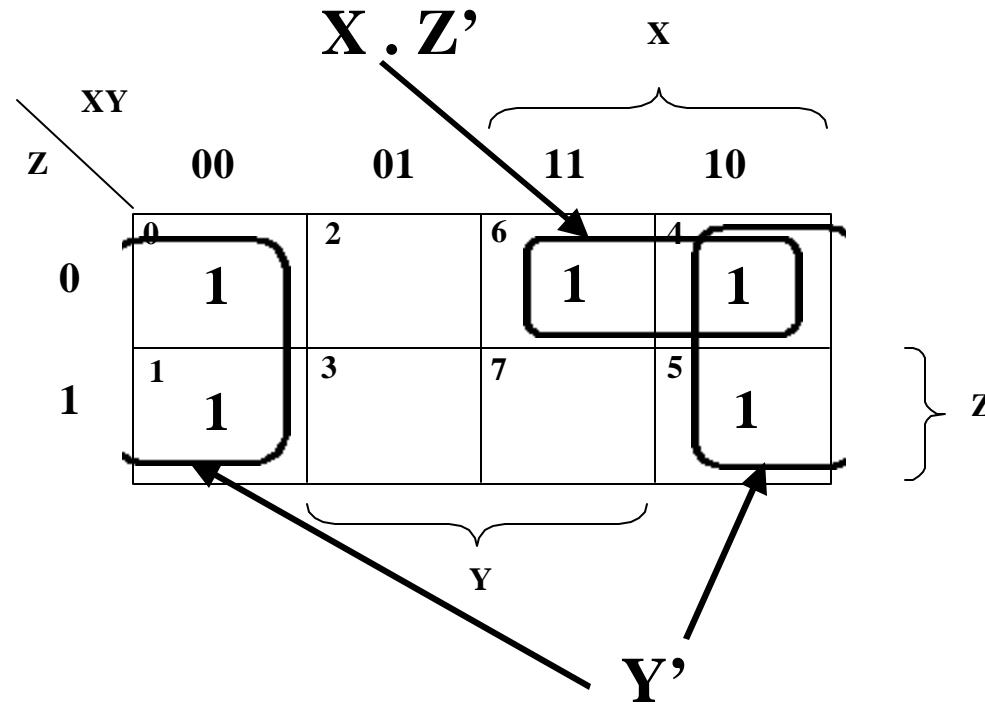

Truth Table

Row	X	Y	Z	F
0	0	0	0	1
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Minimum SOP for $F = Y' + X.Z'$

4-Variable K-map Minimization Example

- Using K-map, find a minimal sum of products (SOP) expression for the function:

$$F(N3, N2, N1, N0) = \sum_{N3, N2, N1, N0} (1, 2, 3, 5, 7, 11, 13)$$

K-map

Truth Table:

Row	W	X	Y	Z	F
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	0

		N3 N2			
		00	01	11	10
N1	00	0	4	12	8
	01	1 1	5 1	13 1	9
11	11	3 1	7 1	15	11 1
	10	2 1	6	14	10

The K-map is annotated with groupings:

- A bracket labeled **N3** groups the top two columns (00 and 01).
- A bracket labeled **N2** groups the bottom two columns (11 and 10).
- A bracket labeled **N1** groups the left two rows (00 and 01).
- A bracket labeled **N0** groups the right two columns (11 and 10).

4-Variable K-map Minimization Example


- Using K-map, find a minimal sum of products (SOP) expression for the function:

$$F(N3, N2, N1, N0) = \sum_{N3, N2, N1, N0} (1, 2, 3, 5, 7, 11, 13)$$

Truth Table:

Row	W	X	Y	Z	F
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	0

K-map

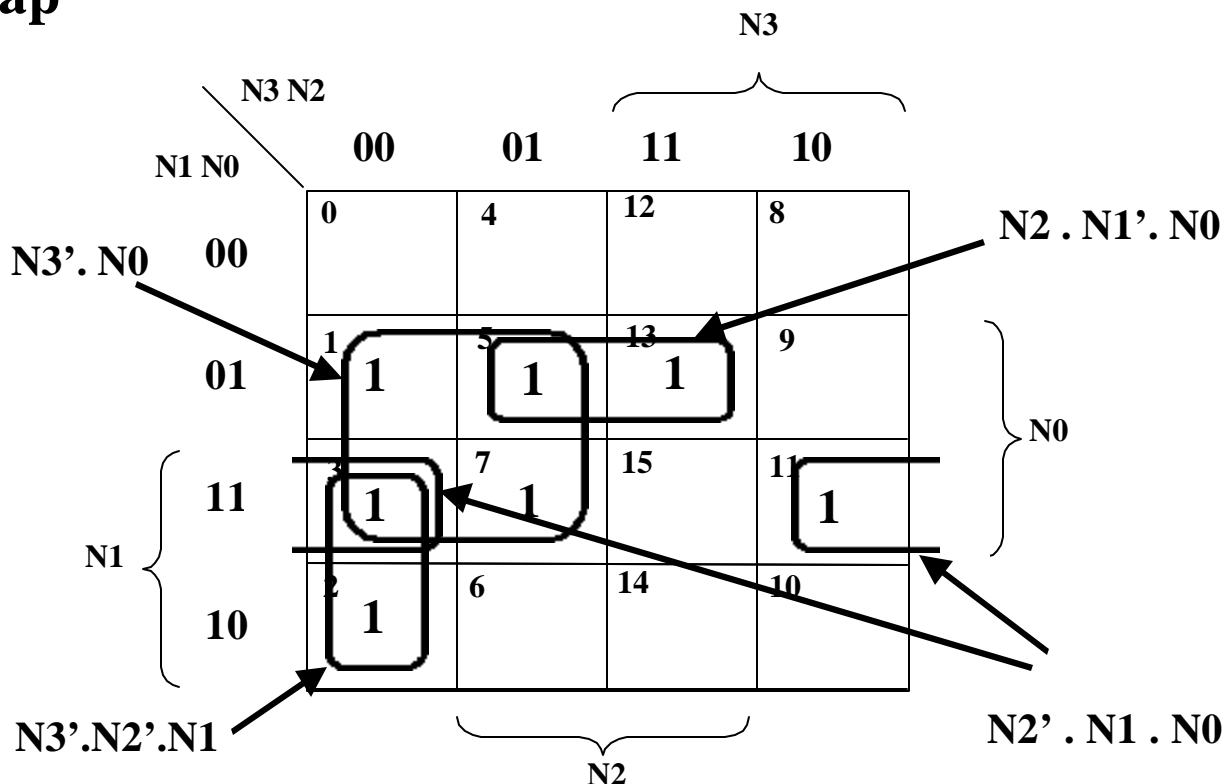

Minimum SOP for $F = N3'.N0 + N3'.N2'.N1 + N2'.N1.N0 + N2.N1'.N0$

K-Map Minimization Rules and Definitions

- A logic function $P(X_1, X_2, ..X_n)$ implies a logic function $F(X_1, ..., X_n)$ if for every input combination such that $P=1$, then $F=1$ (F includes P , or F covers P).
- A prime implicant of a logic function $F(X_1, ..X_n)$ is a normal product term $P(X_1, ..X_n)$ that implies F, such that if any variable is removed from P, the the resulting product term does not imply F.
- A minimal sum is a sum of prime implicants (not necessarily all of them).
- A distinguished 1-cell of a logic function is an input combination that is covered by only one prime implicant.
- An essential prime implicant of a logic function is a prime implicant that covers one or more distinguished 1-cells and *must* be included every minimal sum expression for the function.

4-Variable K-map Minimization Example

- Using K-map, find a minimal sum of products (SOP) expression for the function:

$$F(W,X,Y,Z) = \mathbf{S}_{W,X,Y,Z} (2,3,4,5,6,7,11,13,15)$$

- Also identify all prime implicants, distinguished 1-cells and the corresponding essential prime implicants that cover them.

K-map

		W			
		00	01	11	10
Y	YZ				
	00	0	4 1	12	8
	01	1	5 1	13 1	9
	11	3 1	7 1	15 1	11 1
10	2 1	6 1	14	10	
		X			

Z

4-Variable K-map Minimization Example

- Using K-map, find a minimal sum of products (SOP) expression for the function: $F(W,X,Y,Z) = \sum_{w,x,y,z} (2,3,4,5,6,7,11,13,15)$
- Also identify all prime implicants, distinguished 1-cells and the corresponding essential prime implicants that cover them.

From K-map:

Prime Implicants:

$W'.Y$ $W'.X$ $Y.Z$ $X.Z$

Distinguished 1-cells:

Cell 2 covered by $W'.Y$

Cell 4 covered by $W'.X$


Cell 11 covered by $Y.Z$

Cell 13 covered by $X.Z$

Here all prime implicants are essential prime implicants and all of them must be included in minimum SOP expression:

$$F = W'.Y + W'.X + Y.Z + X.Z$$

K-map

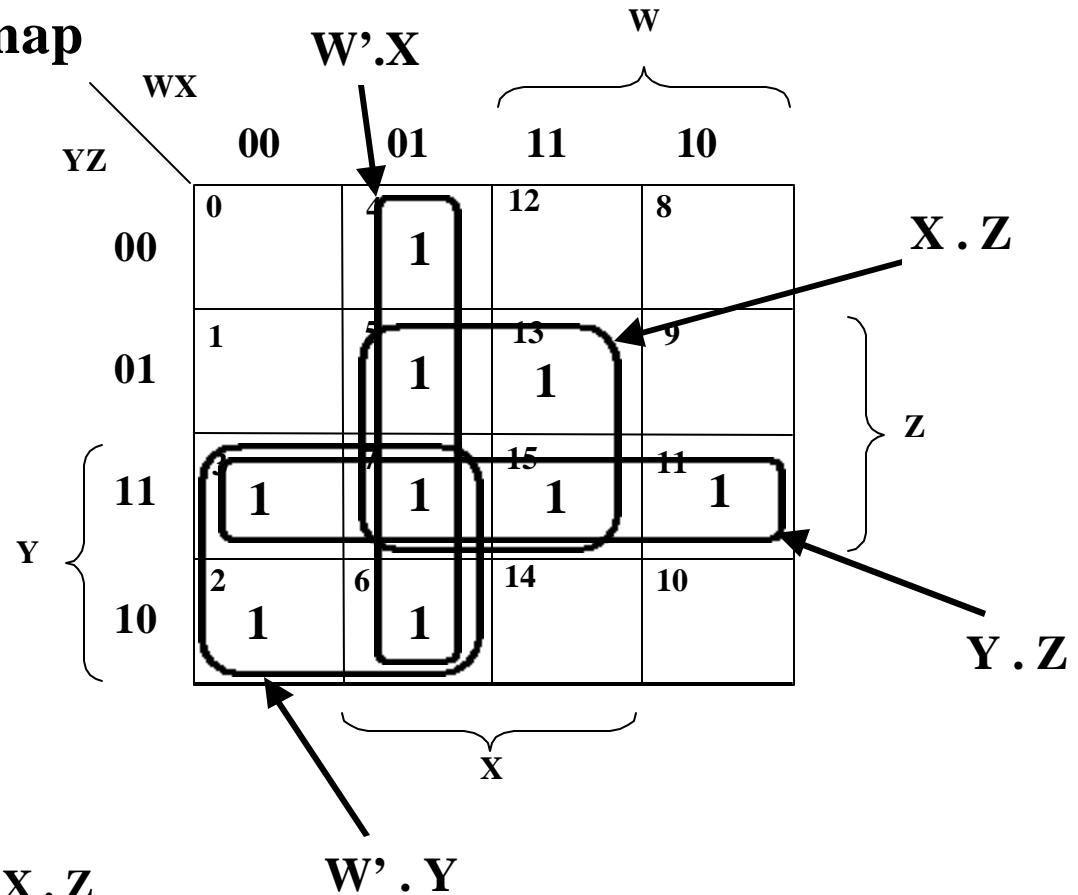

Minimization with Don't care Input Combinations

- **In some cases, the output of a combinational circuit doesn't matter for certain input combinations.**
- **Such combinations are called don't cares and the output is represented in the truth table and K-maps as "d".**
- **When using K-maps to minimize such functions:**
 - **Allow d's to be included when circling sets of 1's to make the sets as large as possible.**
 - **Do not circle any set that only contains d's.**

4-Variable K-map Minimization Example With Don't cares

- Using K-map, find a minimal sum of products (SOP) expression for prime BCD-digit detector which gives 1 when the input BCD digit is prime,
- Since the values 10-15 do not occur in a BCD digit minterms 10-15 are treated as don't cares giving the expression:

$$F(N_3, N_2, N_1, N_0) = \sum_{N_3, N_2, N_1, N_0} (1, 2, 3, 5, 7) + d(10, 11, 12, 13, 14, 15)$$

From K-map:

Prime Implicants:

$$N_3' \cdot N_0 \quad N_2' \cdot N_1 \quad N_2 \cdot N_0$$


Distinguished 1-cells:

Cell 1 covered by $N_3' \cdot N_0$

Cell 2 covered by $N_2' \cdot N_1$

Here not all prime implicants are essential prime implicants that must be included minimum SOP expression:

$$F = N_3' \cdot N_0 + N_2' \cdot N_1$$

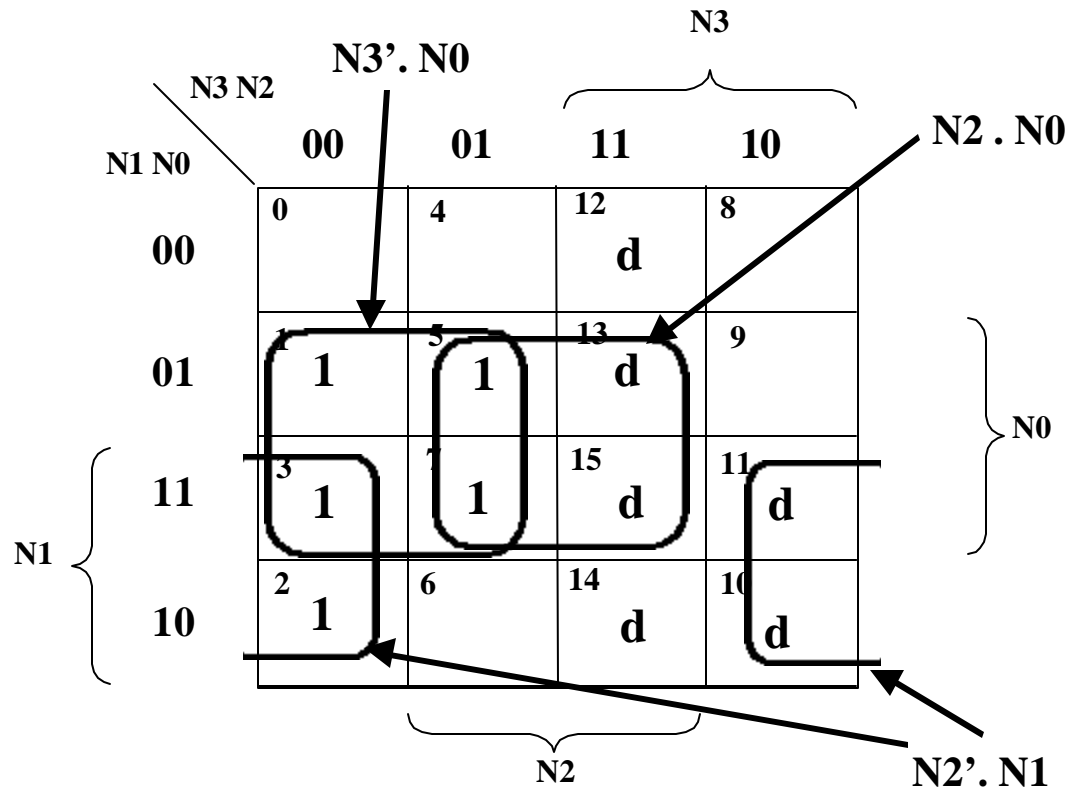

K-map Minimization of Product of Sums

- Similar to K-map minimization of sum of products by using duality and looking at 0-cells instead of 1-cells.
- A set of 2^i 0-cells may be combined if i variables take all 2^i possible combinations within the set while the remaining variables have the same value.
- In the resulting $n-i$ literals sum term, a variable is complemented if it appears as 1 in all the 0-cells, and uncomplemented if it appears as 0.
- A prime implicate of a logic function $F(X_1, ..X_n)$, is a normal sum term $S(X_1, ..X_n)$ implied by F , such as if any variable is removed from S , then the resulting sum term is not implied by F .
- A minimal product is a product of prime implicates.

K-map Product of Sums Minimization Example 1

- Using K-map, find a minimal product of sums (POS) expression for the function:

$$F(X,Y,Z) = \mathbf{P}_{X,Y,Z} (0,3,4,7)$$

K-map

		X			
				}	
Z	XY	00	01	11	10
	0	0			0
1			0	0	
		}			
		Y			

Truth Table


Row	X	Y	Z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

K-map Product of Sums Minimization Example 1

- Using K-map, find a minimal product of sums (POS) expression for the function:

$$F(X,Y,Z) = \mathbf{P}_{X,Y,Z} (0,3,4,7)$$

K-map

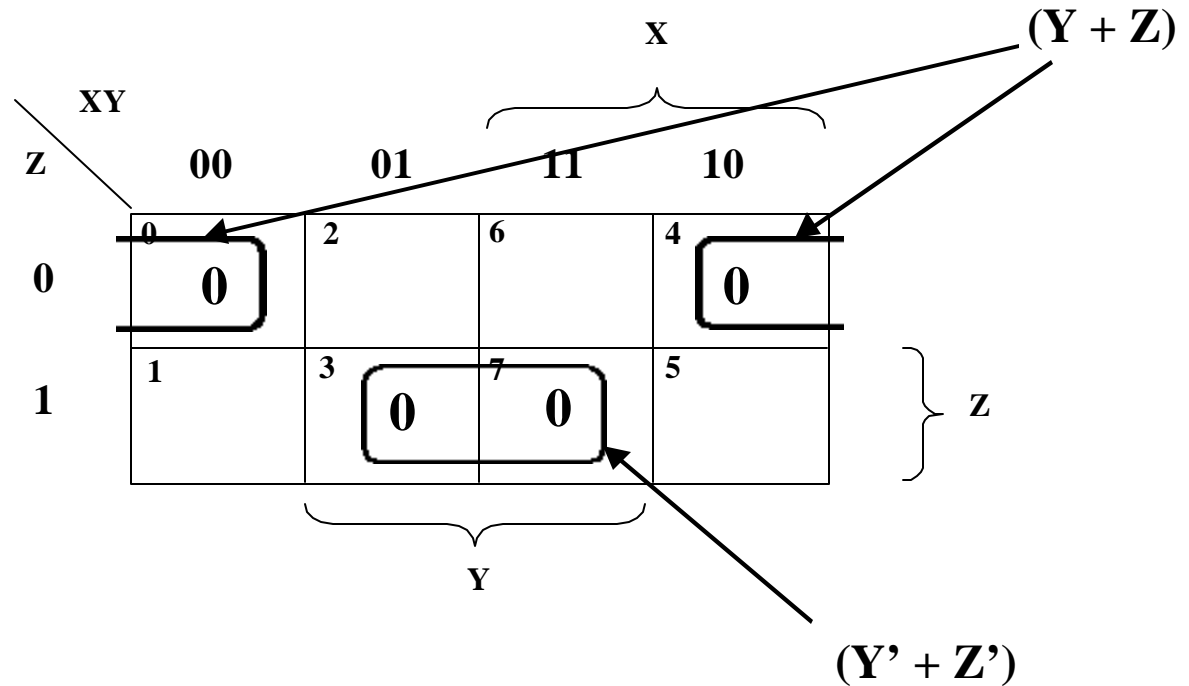

Truth Table

Row	X	Y	Z	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Minimum POS for $F = (Y + Z) \cdot (Y' + Z')$

K-map Product of Sums Minimization Example 2

- Using K-map, find a minimal product of sums (POS) expression for the function:

$$F(W,X,Y,Z) = \mathbf{P}_{W,X,Y,Z} (1,3,8,10,12,13,14,15)$$

K-map

		W			
		00	01	11	10
Y	YZ	00	01	11	10
	00	0	4	12 0	8 0
	01	1 0	5	13 0	9
	11	3 0	7	15 0	11
10	2	6	14 0	10 0	
		X			


Z

K-map Product of Sums Minimization Example 2

- Using K-map, find a minimal product of sums (POS) expression for the function:

$$F(W,X,Y,Z) = \mathbf{P}_{W,X,Y,Z} (1,3,8,10,12,13,14,15)$$

K-map

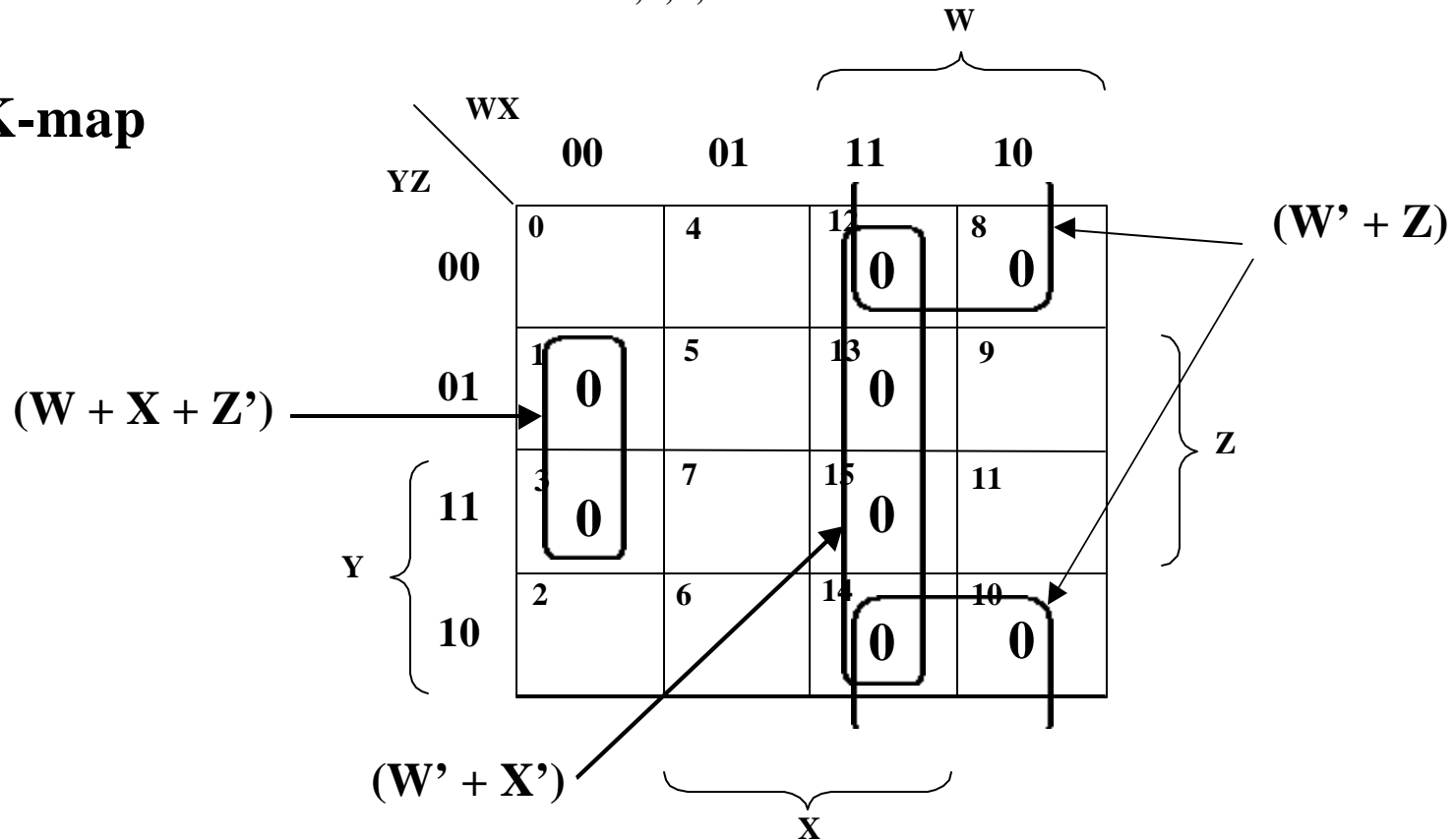

Minimum POS for F = (W + X + Z') . (W' + Z) . (W' + X')

5-variable K-maps

- The K-map for a 5-variable logic function $F(V,W,X,Y,Z)$ is organized as two 4-variable K-maps:

		W			
		X			
YZ	WX	00	01	11	10
	00	0	4	12	8
01	1	5	13	9	
11	3	7	15	11	
10	2	6	14	10	
Y		Z			
		V = 0			

		W			
		X			
YZ	WX	00	01	11	10
	00	16	20	28	24
01	17	21	29	25	
11	19	23	31	27	
10	18	22	30	26	
Y		Z			
		V = 1			

Corresponding squares of each map are adjacent.
 Can be visualised as being one 4-variable map on top of another 4-variable map.

5-Variable K-map SOP Minimization Example

- Using K-map, find a minimal sum of products (SOP) expression for the function:

$$F(V,W,X,Y,Z) = \mathbf{S}_{V,W,X,Y,Z} (4,5,6,7,9,11,13,15,25,27,29,31)$$

K-map

		W			
		WX			
Y	YZ	00	01	11	10
	00	0	4 1	12	8
	01	1	5 1	13 1	9 1
	11	3	7 1	15 1	11 1
10	2	6 1	14	10	
		X			
		V = 0			


		W			
		WX			
Y	YZ	00	01	11	10
	00	16	20	28	24
	01	17	21	29 1	25 1
	11	19	23	31 1	27 1
10	18	22	30	26	
		X			
		V = 1			

5-Variable K-map SOP Minimization Example

- Using K-map, find a minimal sum of products (SOP) expression for the function:

$$F(V,W,X,Y,Z) = \sum_{V,W,X,Y,Z} (4,5,6,7,9,11,13,15,25,27,29,31)$$

K-map

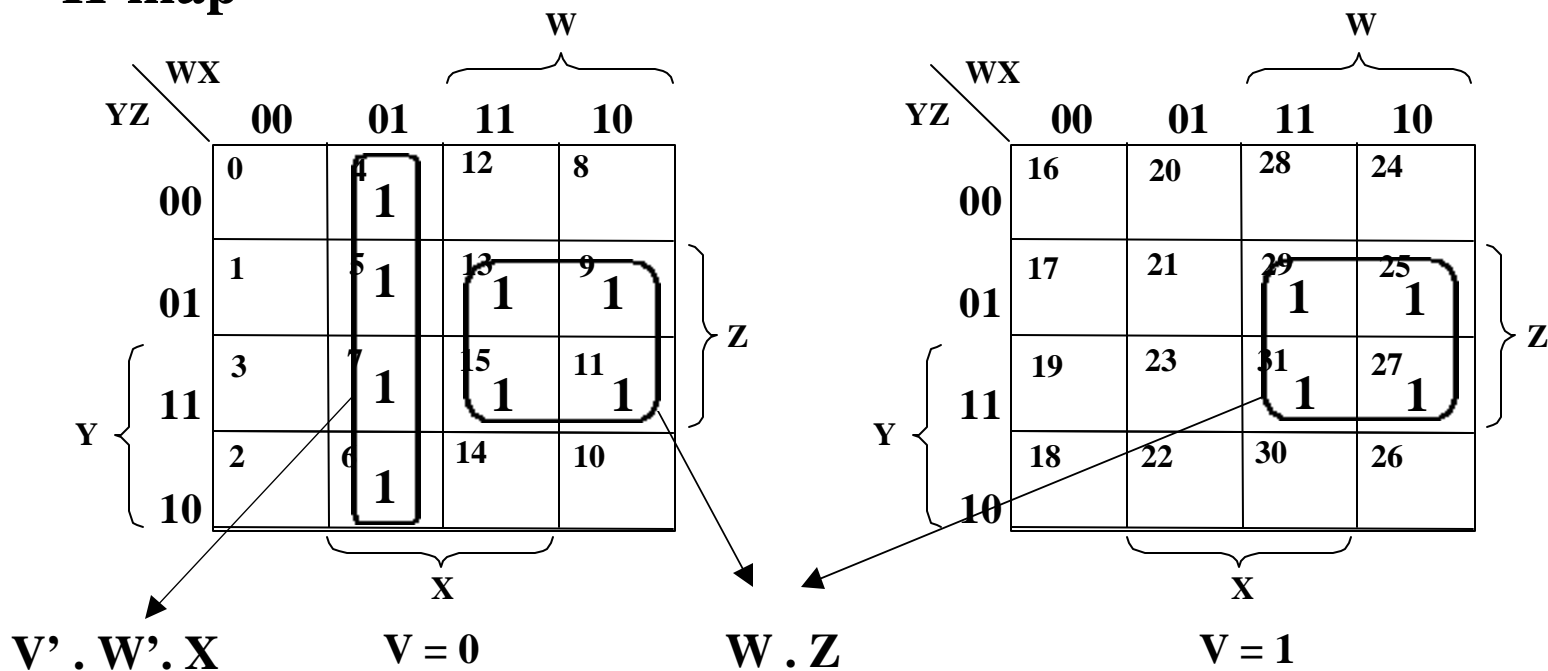

Minimum SOP for $F = V' \cdot W' \cdot X + W \cdot Z$

6-variable K-maps

K-map for a 6-variable logic function $F(U,V,W,X,Y,Z)$ is organized as two 5-variable K-maps:

		W				
		WX				
Y	YZ	00	01	11	10	}
	00	0	4	12	8	
	01	1	5	13	9	
	11	3	7	15	11	
	10	2	6	14	10	
		X				

$U,V = 0,0$

		W				
		WX				
Y	YZ	00	01	11	10	}
	00	16	20	28	24	
	01	17	21	29	25	
	11	19	23	31	27	
	10	18	22	30	26	
		X				

$U,V = 0,1$

		W				
		WX				
Y	YZ	00	01	11	10	}
	00	32	36	44	40	
	01	33	37	45	41	
	11	35	39	47	43	
	10	34	38	46	42	
		X				

$U,V = 1,0$

		W				
		WX				
Y	YZ	00	01	11	10	}
	00	48	52	60	56	
	01	49	53	61	57	
	11	51	55	63	59	
	10	50	54	62	58	
		X				

$U,V = 1,1$