 


# Introduction to Digital Systems

- **Analog devices and systems process time-varying signals that can take on any value across a continuous range.**




- **Digital systems use digital circuits that process digital signals which can take on one of two values, we call:**

**0 and 1 (digits of the binary number system)**


**or LOW and HIGH**

**or FALSE and TRUE**

 

- **Digital computers represent the most common digital systems.**
- **Once-analog Systems that use digital systems today:**

 - Audio recording (CDs, DAT, mp3)
- Phone system switching
- Automobile engine control
- Movie effects
- Still and video cameras....



# **Advantages of Digital Systems Over Analog Systems**

- **Reproducibility of the results and accuracy.**
- **More reliable than analog systems due to better immunity to noise.**
- **Ease of design: No special math skills needed to visualize the behavior of small digital (logic) circuits.**
- **Flexibility and functionality.**
- **Programmability.**
- **Speed: A digital logic element can produce an output in less than 10 nanoseconds ( $10^{-8}$  seconds).**
- **Economy: Due to the integration of millions of digital logic elements on a single miniature chip forming low cost integrated circuit (ICs).**

# Boolean Algebra

What is an **Algebra**? (e.g. algebra of integers)

set of elements (e.g. 0,1,2,..)

set of operations (e.g. +, -, \*,,..)

postulates/axioms (e.g.  $0+x=x,..$ )

- **Boolean Algebra** named after George Boole who used it to study human logical reasoning – calculus of proposition.
- Elements : *true* or *false* ( 0, 1)
- Operations: a **OR** b; a **AND** b, **NOT** a

e.g.     $0 \text{ OR } 1 = 1$        $0 \text{ OR } 0 = 0$

$1 \text{ AND } 1 = 1$        $1 \text{ AND } 0 = 0$

$\text{NOT } 0 = 1$        $\text{NOT } 1 = 0$

# Boolean Algebra

- Set of Elements:  $\{0,1\}$
- Set of Operations:  $\{., +, \neg\}$  — Sometimes denoted by ' , for example  $a'$


x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

AND




x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

OR

 

x	$\neg x$
0	1
1	0

NOT

 

**Signals: High = 5V = 1; Low = 0V = 0**

# **Digital (logic) Elements: Gates**












- **Digital devices or gates have one or more inputs and produce an output that is a function of the current input value(s).**
- **All inputs and outputs are binary and can only take the values 0 or 1**
- **A gate is called a combinational circuit because the output only depends on the current input combination.**
- **Digital circuits are created by using a number of connected gates such as the output of a gate is connected to to the input of one or more gates in such a way to achieve specific outputs for input values.**
- **Digital or logic design is concerned with the design of such circuits.**

# Logic Gates

Symbol set 1

Symbol set 2

(ANSI/IEEE Standard 91-1984)

           

# Truth Tables

- Provides a **listing** of every possible combination of values of binary inputs to a digital circuit and the corresponding outputs.

INPUTS	OUTPUTS
...	...
...	...

- **Example (2 inputs, 2 outputs):**

Truth table


inputs

outputs

x	y	$x \cdot y$	$x + y$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

inputs

outputs

 

# Realizing Logic in Hardware

- **Boolean Algebra and truth tables are essential important tools to express logical relationships.**
- **To use these tools in the real world , we must have some physical way to represent TRUE and FALSE (T and F).**
- **In, digital electronic circuits, T and F are represented by voltage levels:**
  - **The transistor-transistor logic (TTL) 74LS family of digital integrated circuits produces two voltage levels:**
    - **$< .5V$  which represents low voltage L (0) and,**
    - **$> 2.7V$  which represents high voltage H (1) for the digital device.**




# Logic Gates: The Inverter

- The **Inverter**



A	A'
0	1
1	0

Truth table

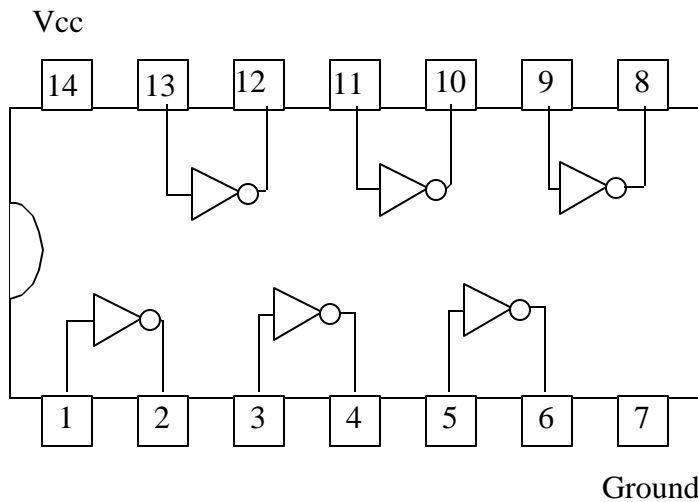

Top View of a TTL 74LS family 74LS04 Hex Inverter IC Package


# Logic Gates: The AND Gate

- The **AND** Gate




A	B	A . B
0	0	0
0	1	0
1	0	0
1	1	1

Truth table

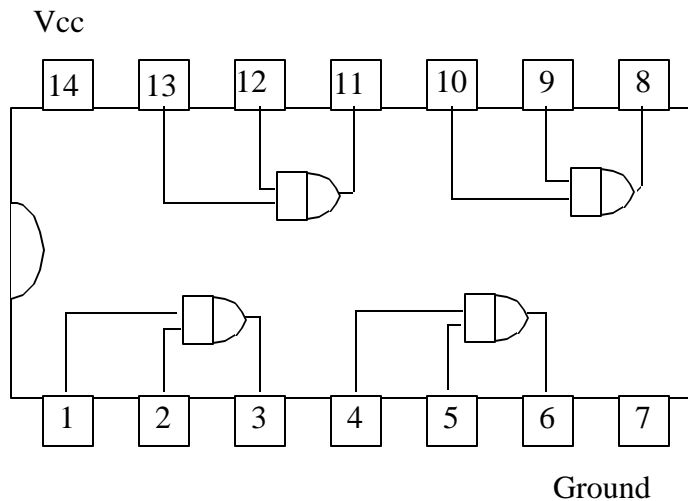


Top View of a TTL 74LS family 74LS08 Quad 2-input AND Gate IC Package
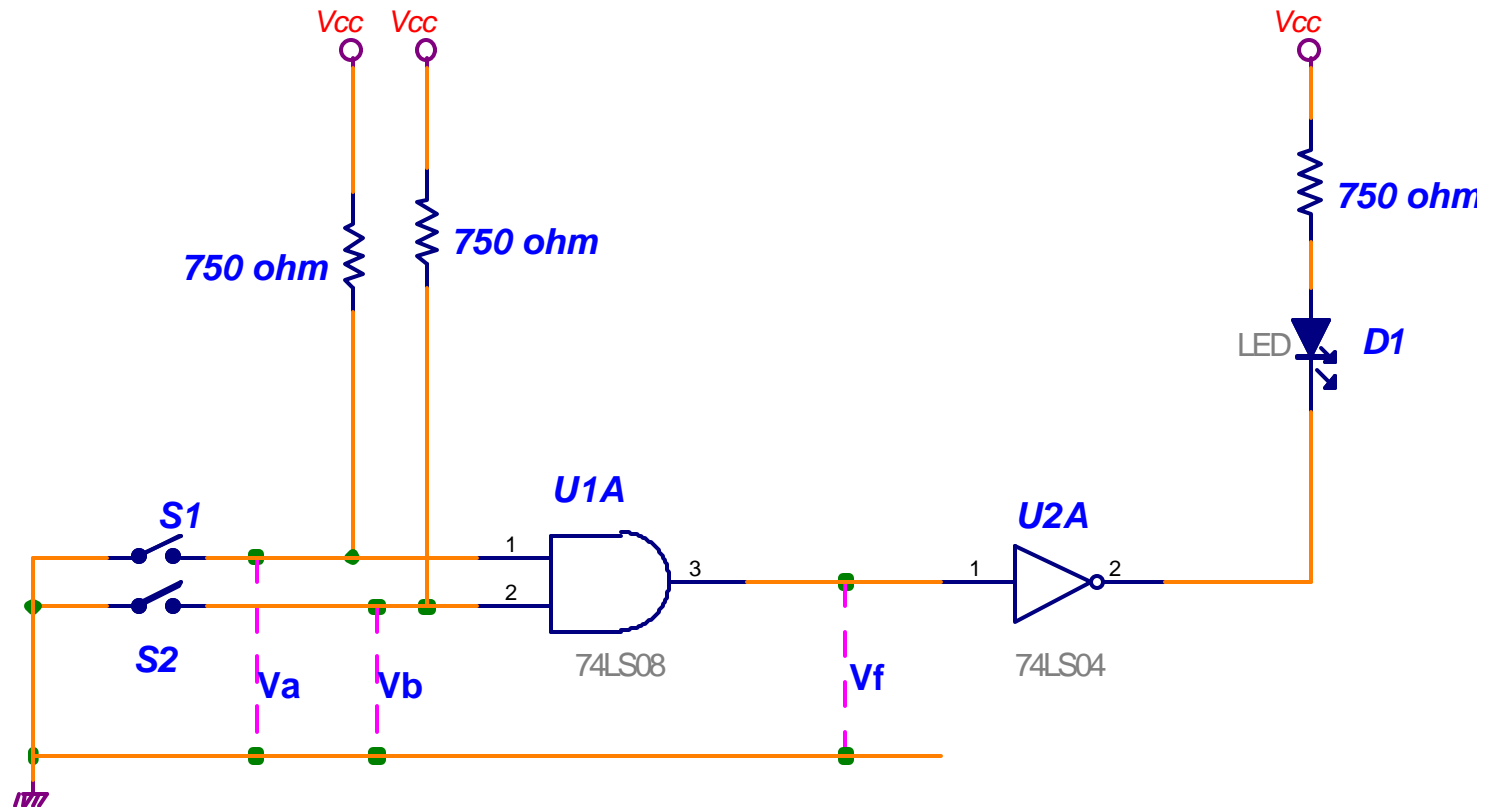
# Circuit to determine AND Gate Truth Table (From Lab 1)




# Logic Gates: The OR Gate

- The **OR** Gate

 

A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1


Truth table

 


Top View of a TTL 74LS family 74LS08 Quad 2-input OR Gate IC Package

# Logic Gates: The NAND Gate

- The **NAND** Gate

 

 - NAND gate is **self-sufficient** (can build any logic circuit with it).
- Can be used to implement AND/OR/NOT.
- Implementing an inverter using NAND gate:





A	B	$(A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

Truth table


Top View of a TTL 74LS family 74LS00 Quad 2-input NAND Gate IC Package

# Logic Gates: The NOR Gate

- The **NOR** Gate

  

 - NOR gate is also **self-sufficient** (can build any logic circuit with it).
- Can be used to implement AND/OR/NOT.
- Implementing an inverter using NOR gate:  $x \rightarrow x'$




A	B	$(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0

Truth table

Top View of a TTL 74LS family 74LS02 Quad 2-input NOR Gate IC Package


# Logic Gates: The XOR Gate

- The **XOR** Gate

 

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

 


Top View of a TTL 74LS family 74LS86 Quad 2-input XOR Gate IC Package

# Drawing Logic Circuits

- When a Boolean expression is provided, we can easily draw the logic circuit.
- Examples:

$$F1 = xyz'$$


(note the use of a 3-input AND gate)

 


 
# Analysing Logic Circuits


- When a logic circuit is provided, we can analyse the circuit to obtain the logic expression.
- Example: What is the Boolean expression of F4?



$$F4 = (A'B'+C)'$$

# Analysing Logic Circuit

 - **Example:** What is Boolean expression of F5?



**F5 =**

# Simple Circuit Design: Two-input Multiplexer


- Multiplexer with two input bits, A, B and a control input bit S and output Z. Depending on the value of S, the circuit is to transfer either the the value of A or B to the output Z

Truth table from circuit description

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Using logic design methods (to be studied later) we get the optimal logic function for Z

$$Z = S'.A + S.B$$

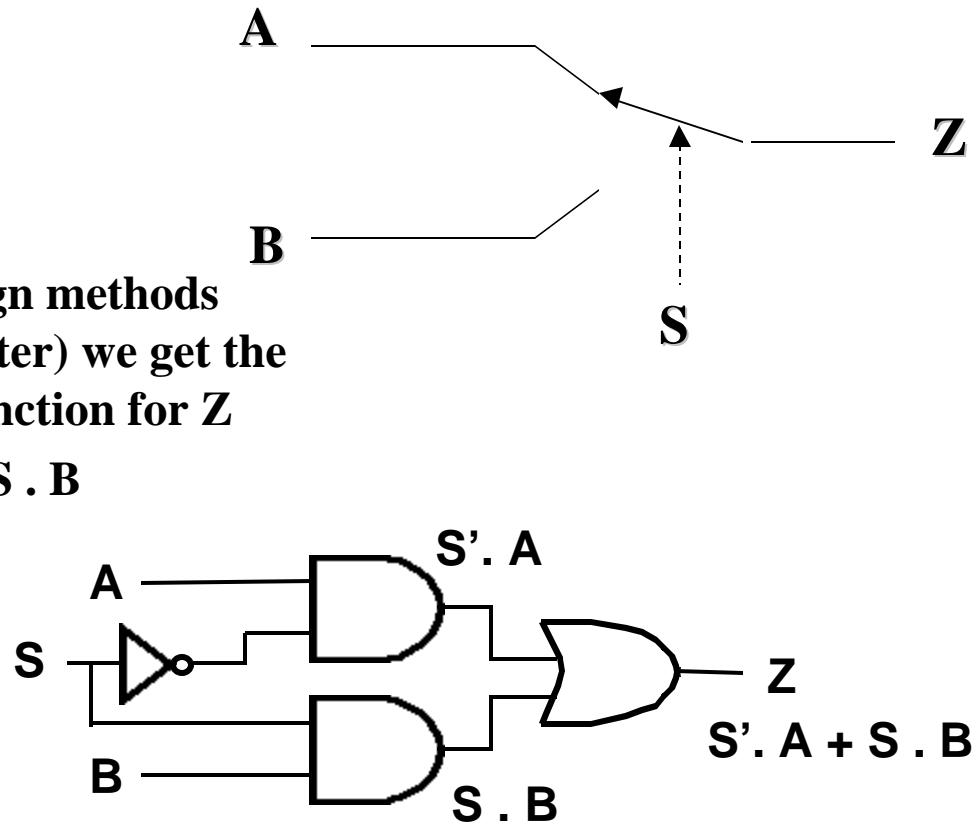


# Integrated Circuits

- **An Integrated circuit (IC) is a number of logic gated fabricated on a single silicon chip.**
- **ICs can be classified according to how many gates they contain as follows:**
  - **Small-Scale Integration (SSI):** Contain 1 to 20 gates.
  - **Medium-Scale Integration (MSI):** Contain 20 to 200 gates. Examples: Registers, decoders, counters.
  - **Large-Scale Integration (LSI):** Contain 200 to 200,000 gates. Include small memories, some microprocessors, programmable logic devices.
  - **Very Large-Scale Integration (VLSI):** Usually stated in terms of number of transistors contained usually over 1,000,000. Includes most microprocessors and memories.

# Computer Hardware Generations

- **The First Generation, 1946-59: Vacuum Tubes, Relays, Mercury Delay Lines:**
  - **ENIAC (Electronic Numerical Integrator and Computer):** First electronic computer, 18000 vacuum tubes, 1500 relays, 5000 additions/sec.
  - **First stored program computer: EDSAC (Electronic Delay Storage Automatic Calculator).**
- **The Second Generation, 1959-64: Discrete Transistors.**  
(e.g IBM 7000 series, DEC PDP-1)
- **The Third Generation, 1964-75: Small and Medium-Scale Integrated (SSI, MSI) Circuits.** (e.g. IBM 360 mainframe)
- **The Fourth Generation, 1975-Present: The Microcomputer, VLSI-based Microprocessors.**

# Hierarchy of Computer Architecture

 

EECC341 - Shaaban

# A Hierarchy of Computer Design

Level	Name	Modules	Primitives	Descriptive Media
1	Electronics	Gates, FF's	Transistors, Resistors, etc.	Circuit Diagrams
2	Logic	Registers, ALU's ...	Gates, FF's ....	Logic Diagrams
3	Organization	Processors, Memories	Registers, ALU's ...	Register Transfer Notation (RTN)
<b>Low Level - Hardware</b>				
4	Microprogramming	Assembly Language	Microinstructions	Microprogram
<b>Firmware</b>				
5	Assembly language programming	OS Routines	Assembly language Instructions	Assembly Language Programs
6	Procedural Programming	Applications Drivers ..	OS Routines High-level Languages	High-level Language Programs
7	Application	Systems	Procedural Constructs	Problem-Oriented Programs
<b>High Level - Software</b>				

**EECC341 - Shaaban**