 


Registers & Counters


- **Registers.**
- **Shift Registers:**
 - Serial in, serial out shift register
 - Serial in, parallel out shift register
 - Parallel in, serial out shift register
 - Parallel in, parallel out shift register
 - Shift Register Applications
- **Counters:**
 - Ripple Counters
 - Synchronous Counters
 - Counter Applications

Registers

- An n-bit register is a collection of n D flip-flops with a common clock used to store n related bits.





**Example: 74LS175
4-bit register**

 



Shift Registers

- **Multi-bit register that moves stored data bits left/right (1 bit position per clock cycle)**



- **Shift Left is towards MSB**

  

  - **Shift Right (or Shift Up) is towards MSB**



Serial In, Serial Out Shift Register

 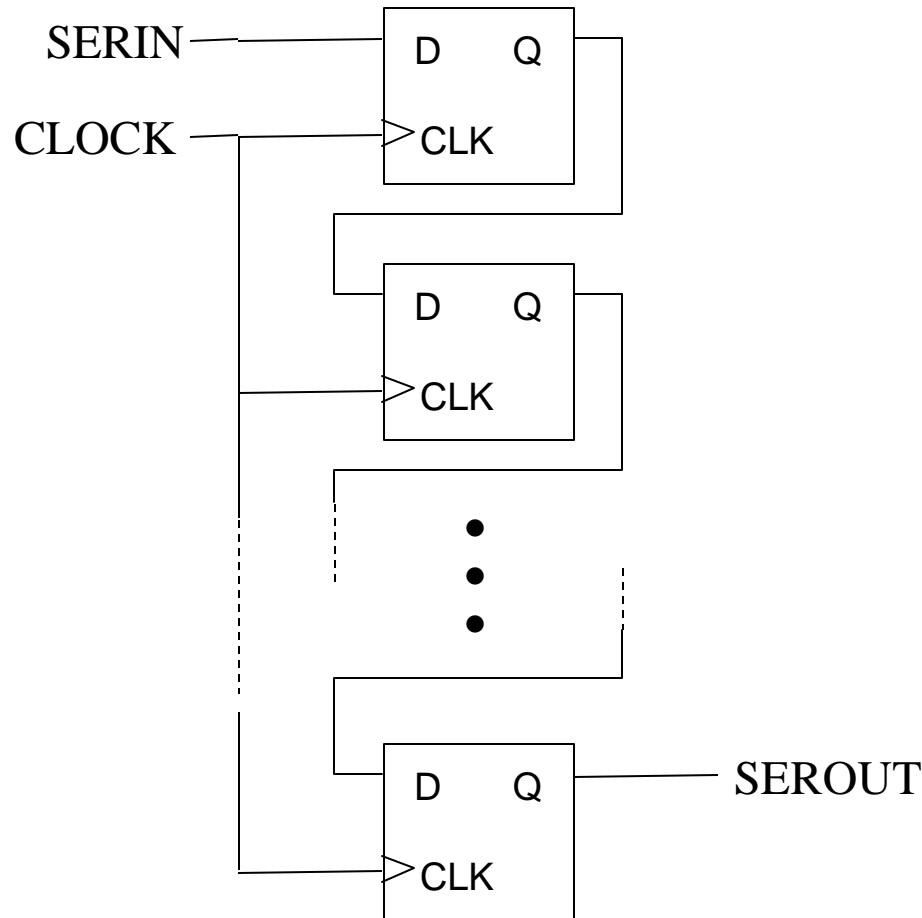

For a n-bit SRG:
Serial Out = Serial In delayed
by n clock period



4-bit shift register example:

serin: 1 0 1 1 0 0 1 1 1 0

serout: - - - - 1 0 1 1 0 0

clock: $\uparrow\uparrow\uparrow\uparrow\uparrow\uparrow\uparrow\uparrow\uparrow\uparrow$

Serial In, Parallel Out Shift register

 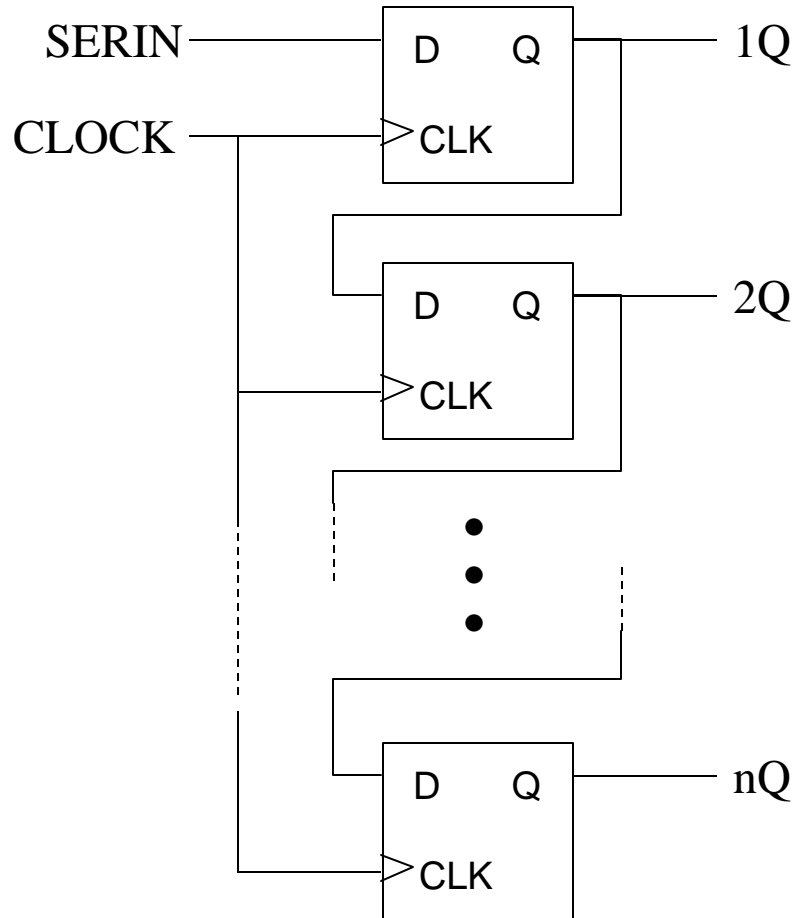


Serial to Parallel Converter


4-bit shift register example:

serin:	1	0	1	1	0	0	1	1	1	0
1Q:	-	1	0	1	1	0	0	1	1	1
2Q:	-	-	1	0	1	1	0	0	1	1
3Q:	-	-	-	1	0	1	1	0	0	1
4Q:	-	-	-	-	1	0	1	1	0	0
clock:	↑	↑	↑	↑	↑	↑	↑	↑	↑	↑

Parallel In, Serial Out Shift Register

 


Parallel In, Parallel Out Shift Register

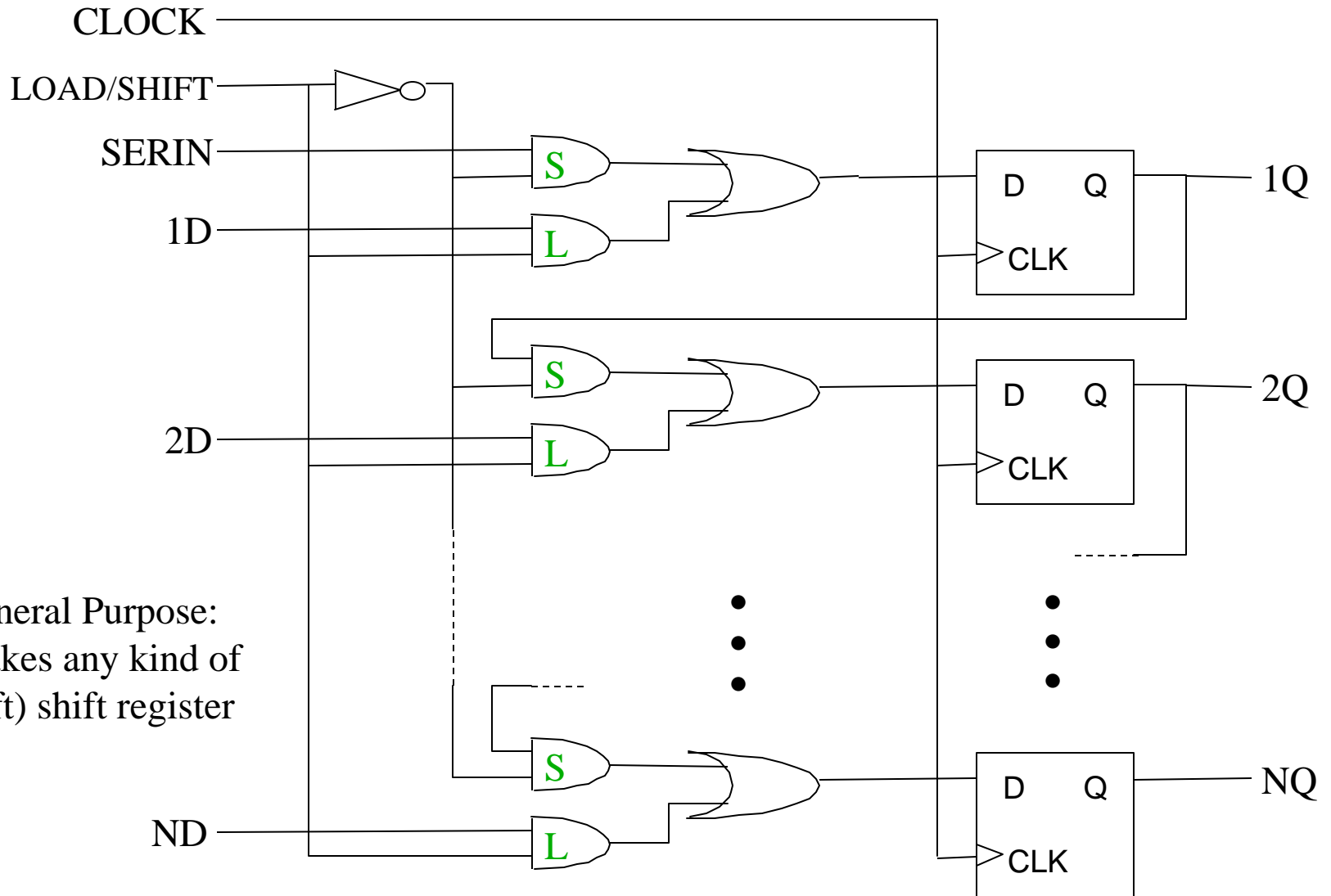


General Purpose:
Makes any kind of
(left) shift register

Bi-directional Universal Shift Registers

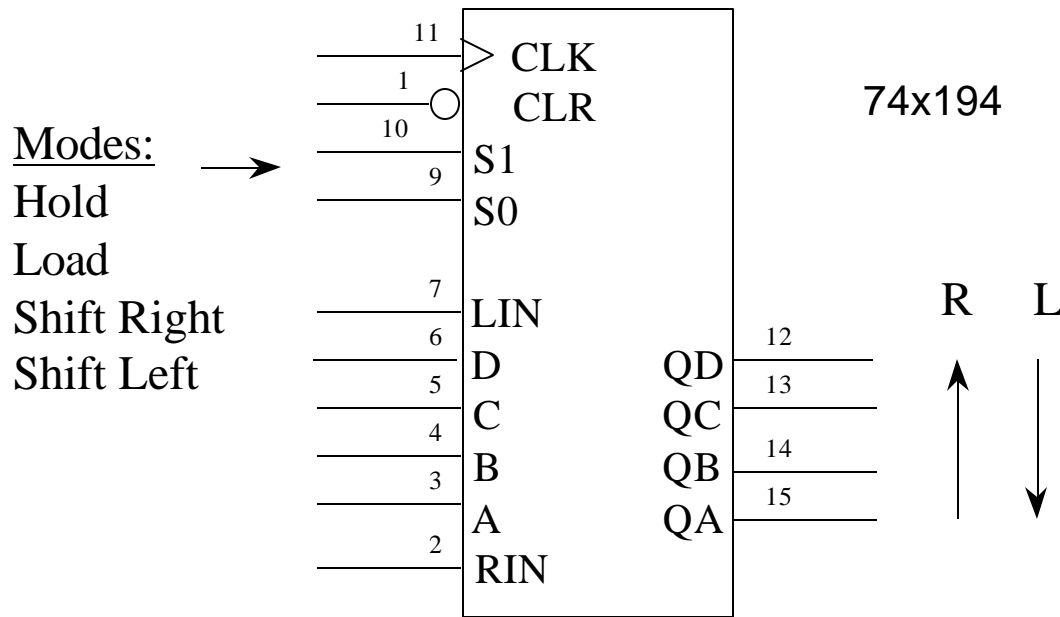

4-bit Bi-directional Universal (4-bit) PIPO

Function	Mode		Next state				
	S1	S0	QA*	QB*	QC*	QD*	
Hold	0	0	QA	QB	QC	QD	
Shift right/up	0	1	RIN	QA	QB	QC	→
Shift left/down	1	0	QB	QC	QD	LIN	←
Load	1	1	A	B	C	D	

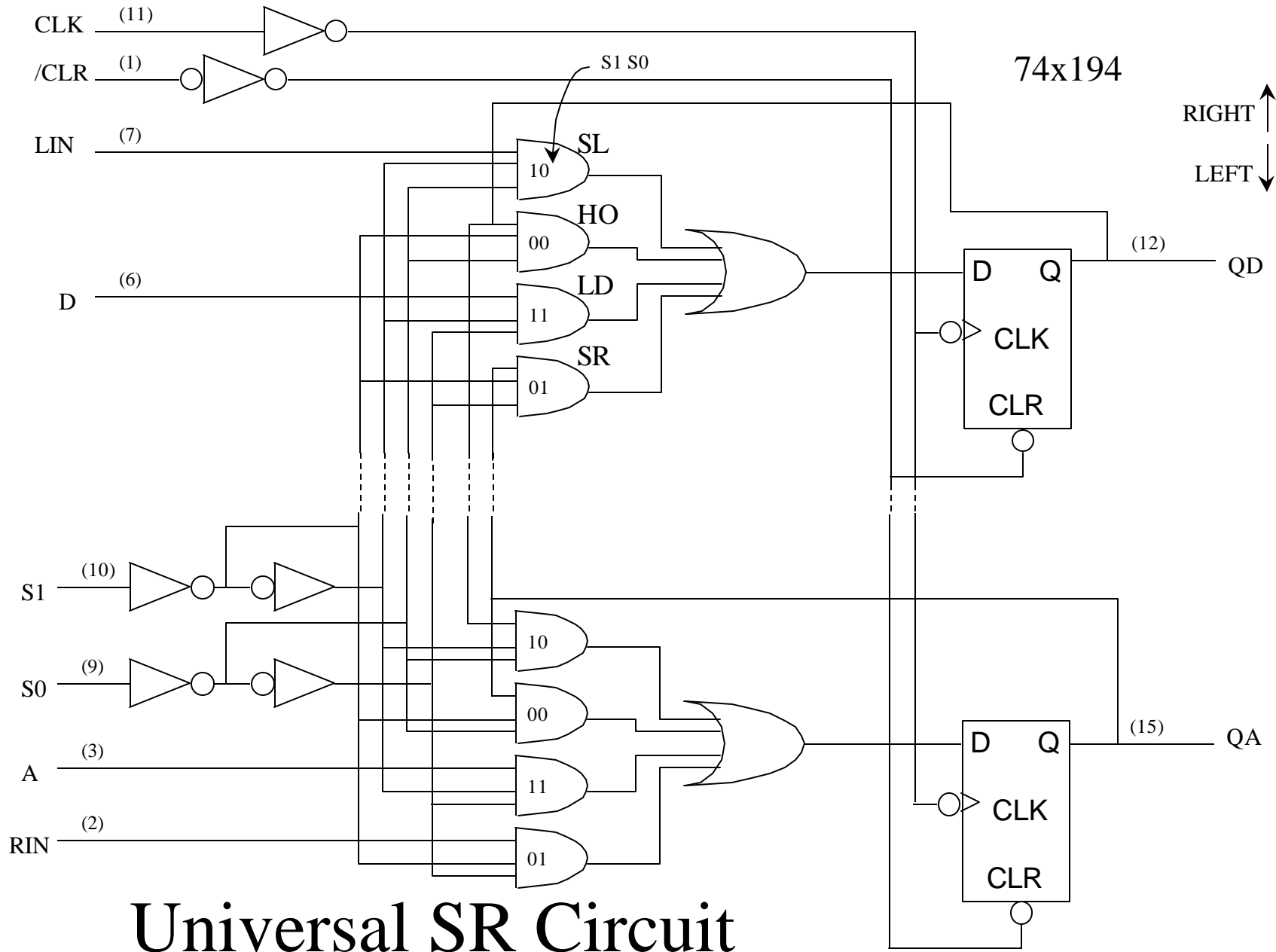

Universal SR Circuit

Shift Register Applications

- **State Registers**

- Shift registers are often used as the state register in a sequential device. Usually, the next state is determined by shifting right and inserting a primary input or output into the next position (i.e. a finite memory machine)
- Very effective for sequence detectors


- **Serial Interconnection of Systems**

- keep interconnection cost low with serial interconnect


- **Bit Serial Operations**

- Bit serial operations can be performed quickly through device iteration
- Iteration (a purely combinational approach) is expensive (in terms of # of transistors, chip area, power, etc).
- A sequential approach allows the reuse of combinational functional units throughout the multi-cycle operation

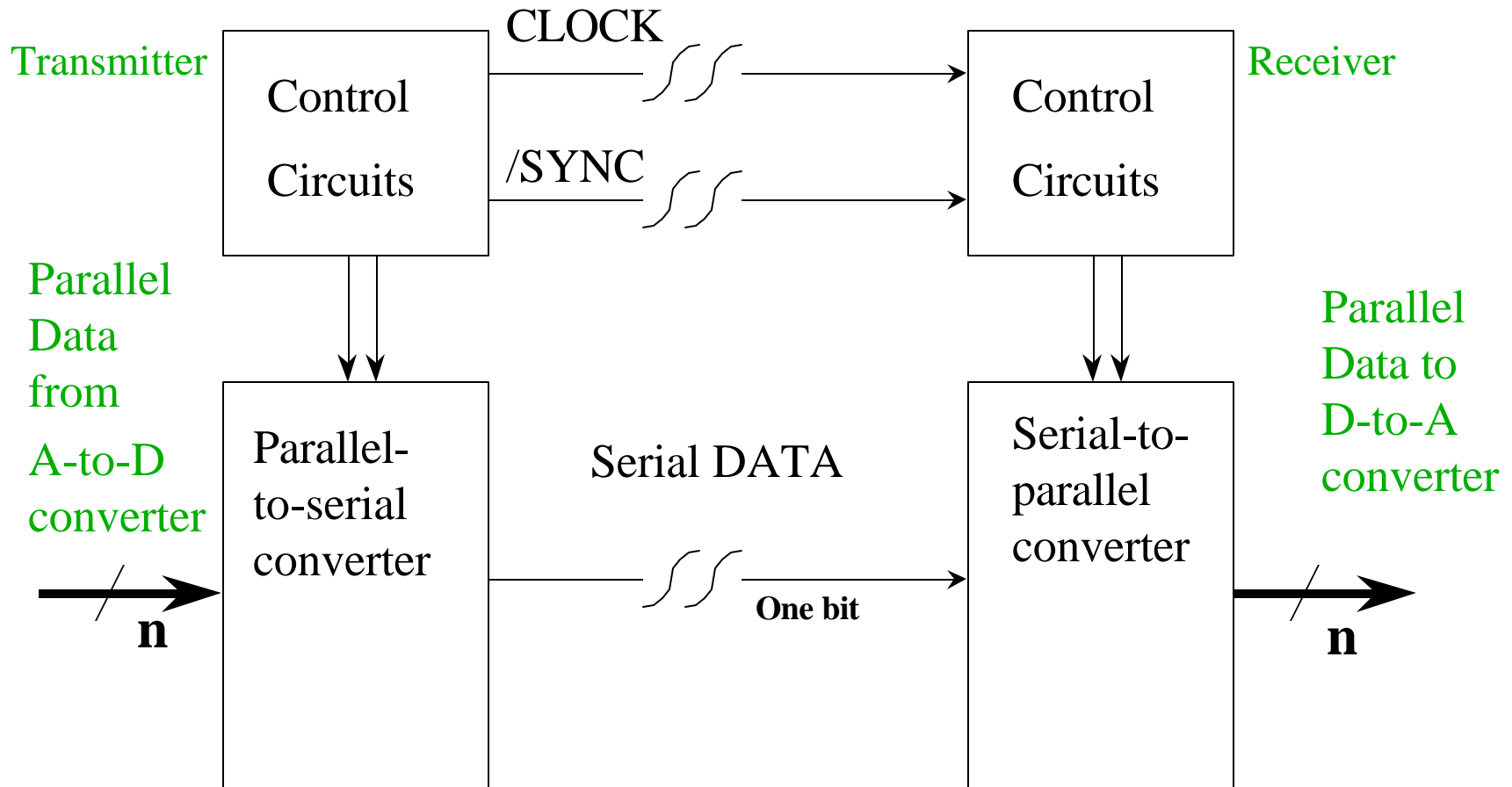Shift Register Applications: Serial Interconnection of Systems



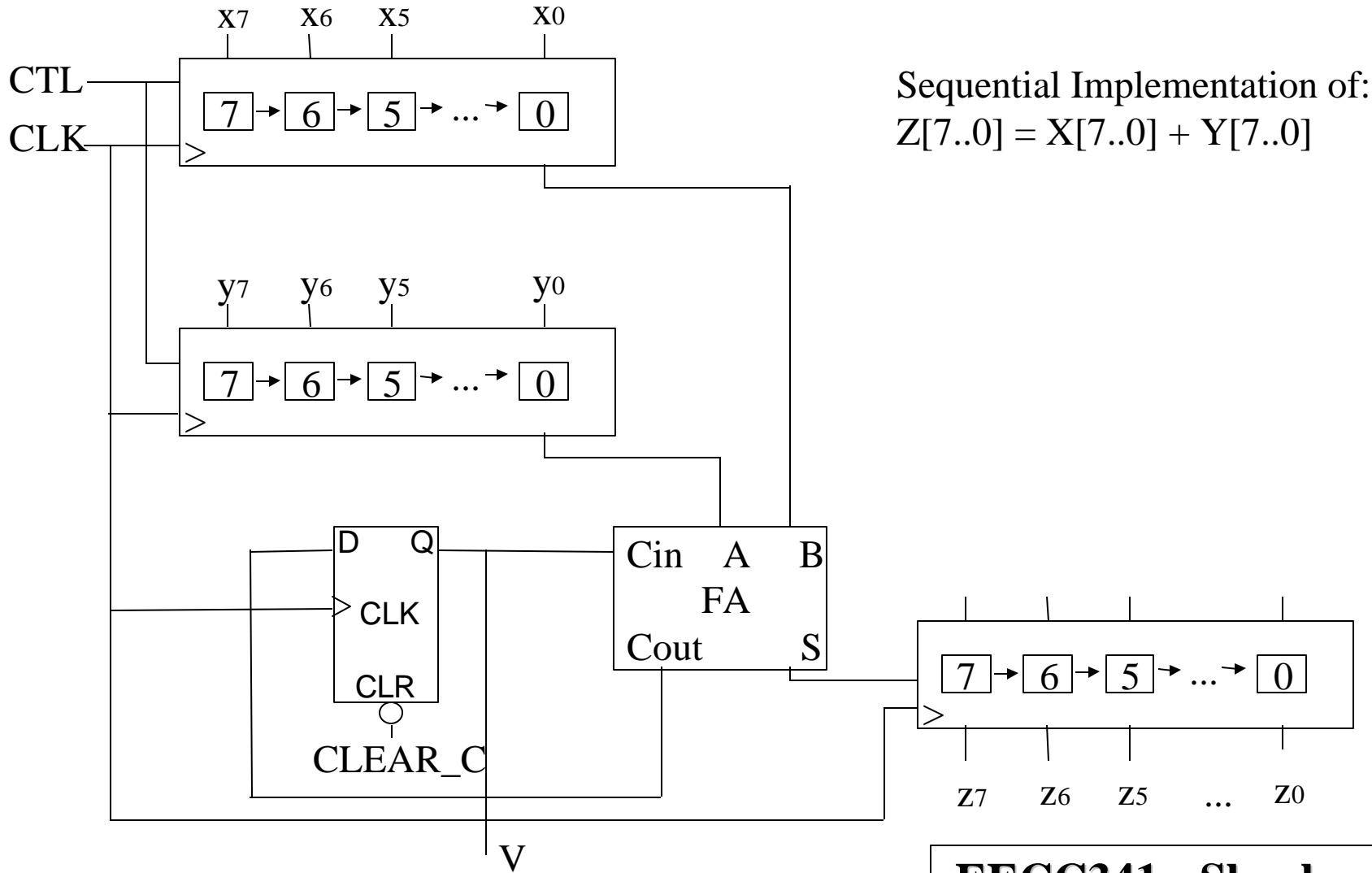
Shift Register Applications Example: 8-Bit Serial Adder



Sequential Implementation of:
 $Z[7..0] = X[7..0] + Y[7..0]$

Counters

 
- **Clocked sequential circuit with single-cycle state diagram**
 - **Modulo-m counter = divide-by-m counter**



- **Most Common:**


n-bit binary counter, where $m = 2^n \rightarrow$ n flip-flops,
counts $0 \dots 2^n - 1$

4-bit Ripple Counter

 


Uses
Minimal
Logic

Ripple Counter Timing

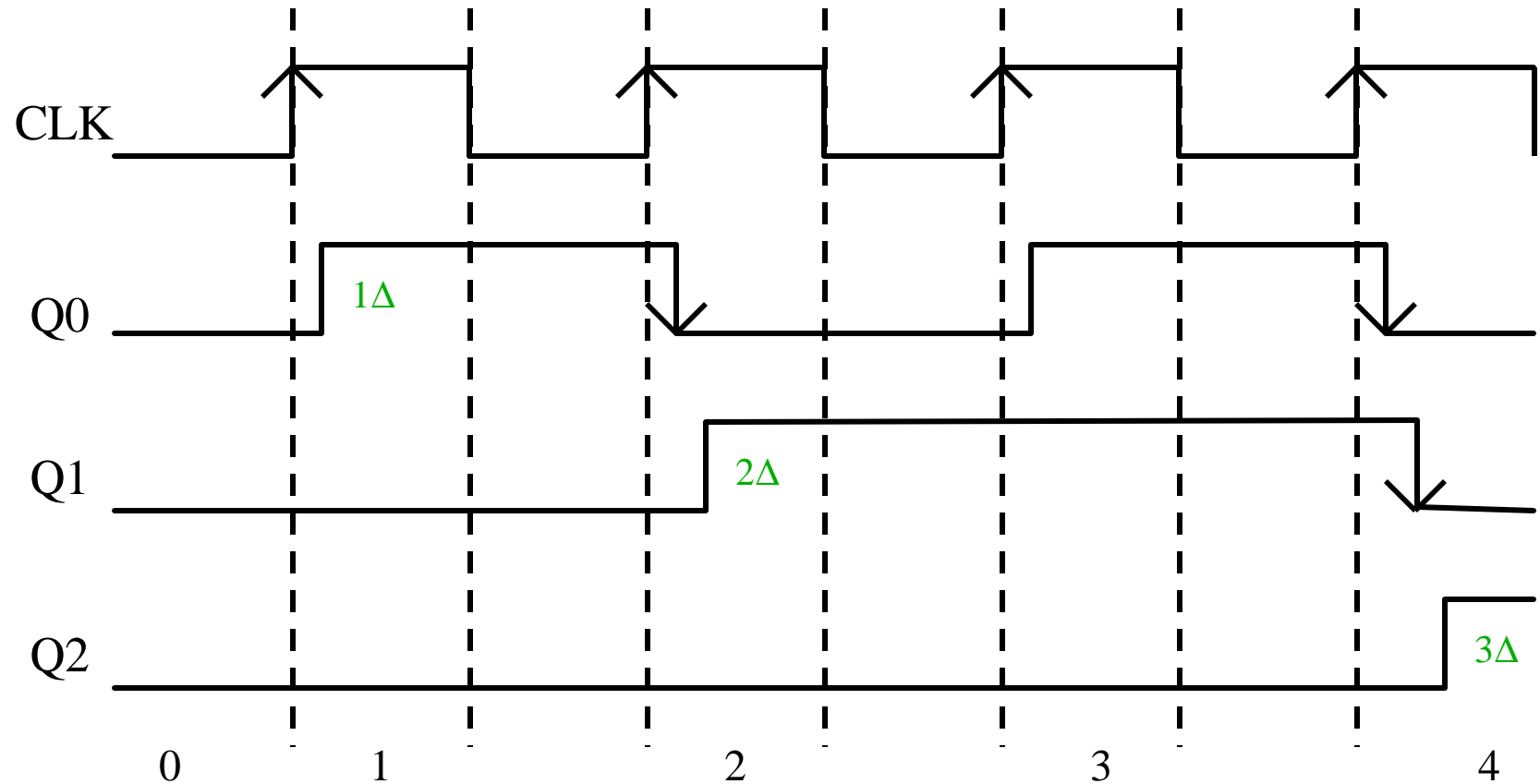

Ripple Counter Problem

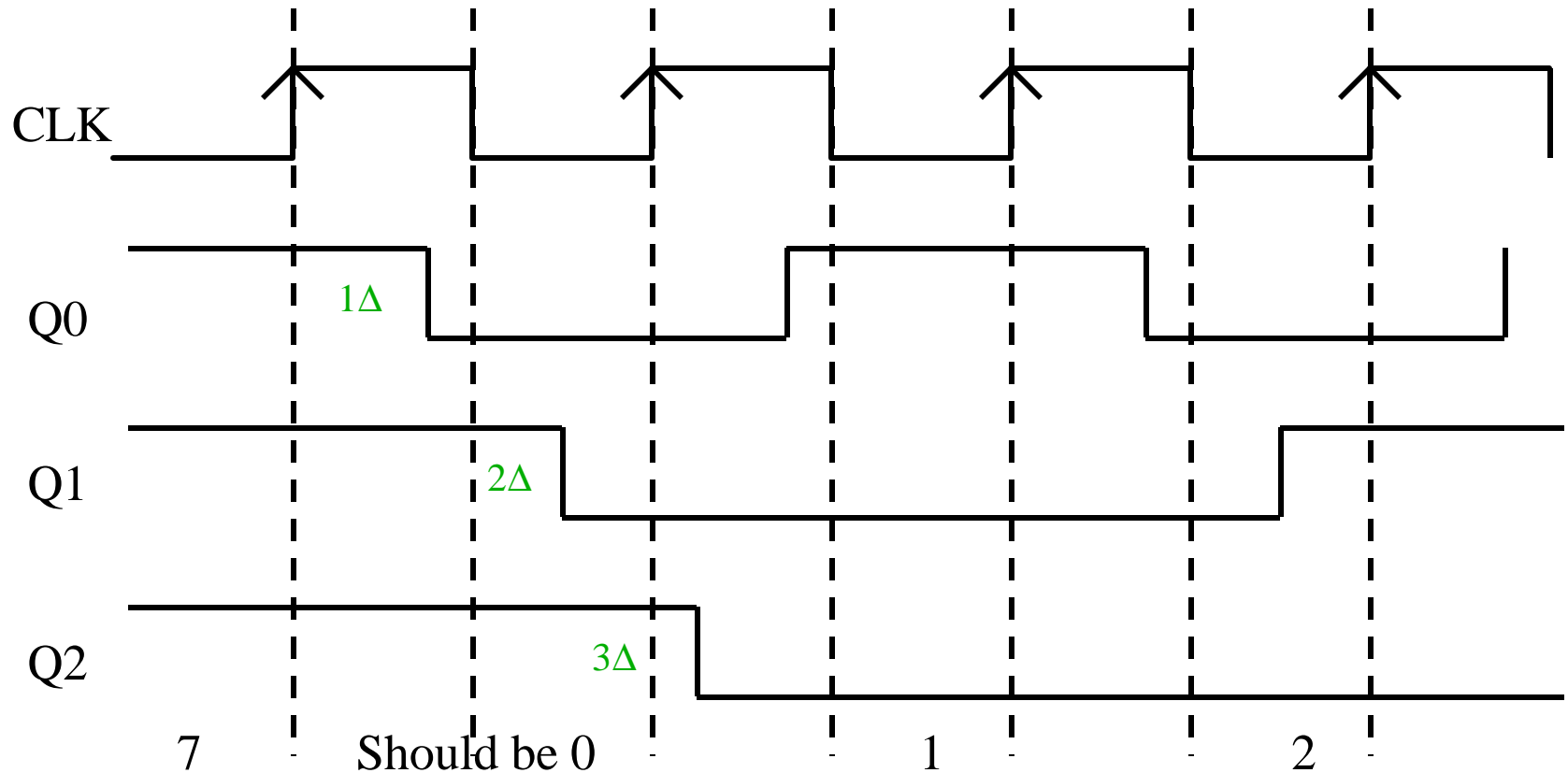$n \cdot T_{CQ}$ for MSB change for n-bit ripple counter \Rightarrow minimum clk period




Synchronous Counters


- **All clock inputs connected to common CLK signal**
 - **All flip-flop outputs change simultaneously t_{CQ} after CLK**
 - **Faster than ripple counters**
 - **More complex logic**
 - **Most frequently used type of counter**

Synchronous Serial Counter

 - Flip-flops enabled when all lower flip-flops = 1.
- Enable propagates serially — limits speed
- Requires $(n-1) \Delta t < T_{CLK}$
- All outputs change simultaneously t_{cQ} after $CLK \uparrow$




Synchronous Parallel Counter

 

- **Single-level enable logic per flip-flop**
- **Fastest and most complex type of counter**
- **Requires $\mathbf{D}t < T_{CLK}$**
- **All outputs change simultaneously t_{CQ} after $\mathbf{CLK}\uparrow$**

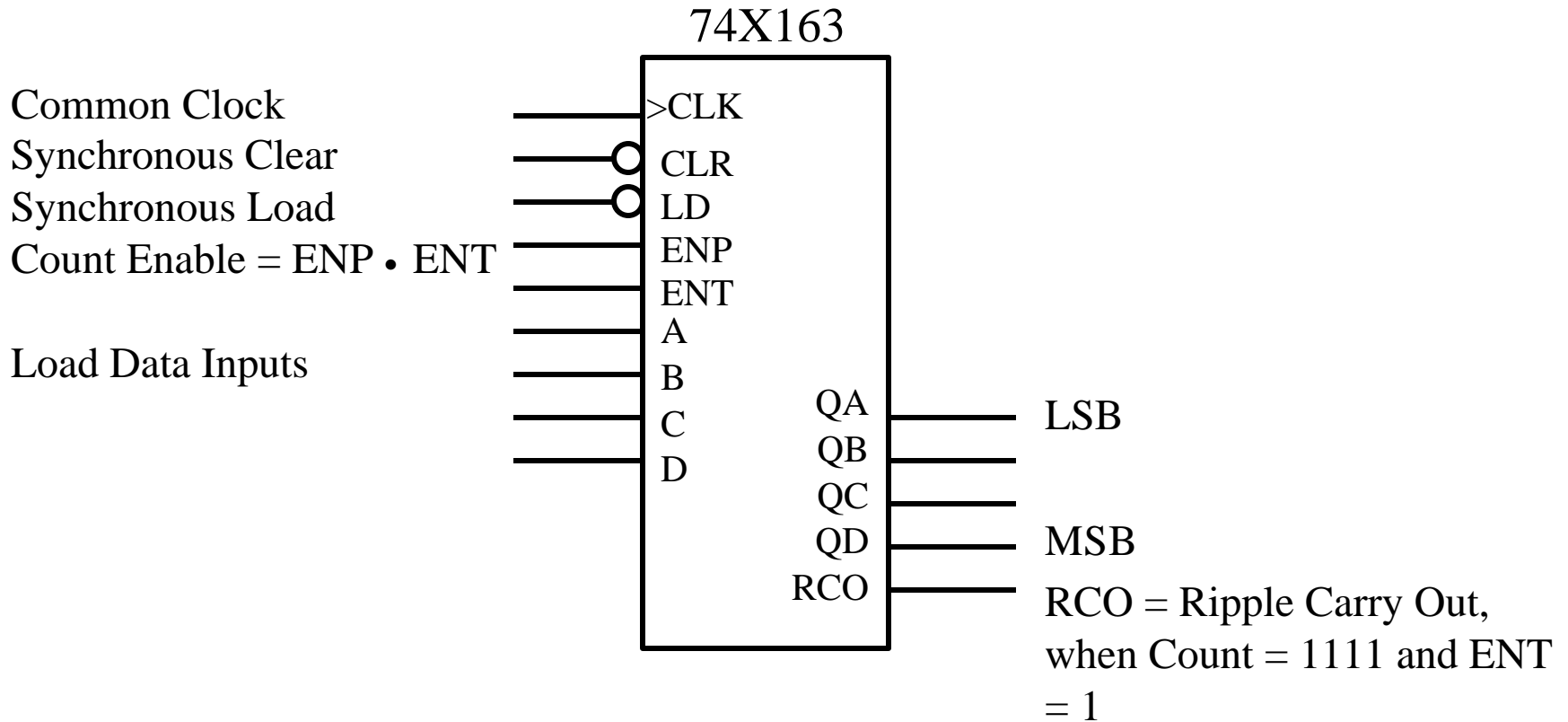
74X163 4-bit Synchronous Parallel Counter



74X163 State Table

Inputs					Current State				Next State			
$\overline{\text{CLR}}$	$\overline{\text{LD}}$	ENT	ENP		QD	QC	QB	QA	QD*	QC*	QB*	QA*
0	X	X	X	Clear	X	X	X	X	0	0	0	0
1	0	X	X	Load	X	X	X	X	D	C	B	A
1	1	0	X	Hold	X	X	X	X	QD	QC	QB	QA
1	1	1	0	Hold	X	X	X	X	QD	QC	QB	QA
1	1	1	1	Count	0	0	0	0	0	0	0	1
1	1	1	1	.	0	0	0	1	0	0	1	0
1	1	1	1	.	0	0	1	0	0	0	1	1
1	1	1	1	.	0	0	1	1	0	1	0	0
1	1	1	1	.	0	1	0	0	0	1	0	1
1	1	1	1	.	0	1	0	1	0	1	1	0
1	1	1	1	.	0	1	1	0	0	1	1	1
1	1	1	1	.	0	1	1	1	1	0	0	0
1	1	1	1	.	1	0	0	0	1	0	0	1
1	1	1	1	.	1	0	0	1	1	0	1	0
1	1	1	1	.	1	0	1	0	1	1	0	0
1	1	1	1	.	1	1	0	0	1	1	0	1
1	1	1	1	.	1	1	1	0	1	1	1	1
1	1	1	1	.	1	1	1	1	0	0	0	0

74X169 Up/Down Counter

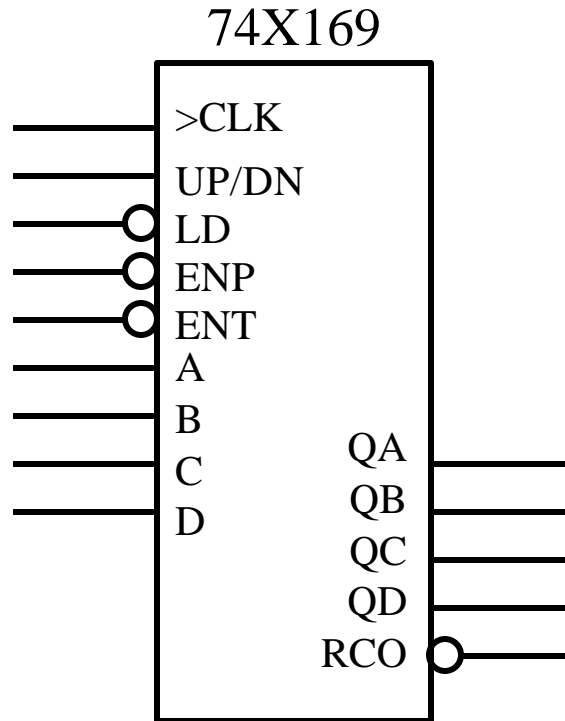

UP/DN = 1 = up → RCO = 15

UP/DN = 0 = down → RCO = 0

up down up
Ex: 0,1,2, 1,0,15,14, 15,0,1,2
 ↓ ↓
 RCO RCO

Counter Applications

- Count the number of times an event takes place
- Control the number of steps in a sequence of fixed actions (a sequencer)
- Generate timing signals (frequency divider, etc.)

