

# State Machine Design Procedure

1. **Build state/output table (or state diagram) from word description using state names.**
2. **Minimize number of states (optional).**
3. **State Assignment: Choose state variables and assign bit combinations to named states.**
4. **Build transition/output table from state/output table (or state diagram) by substituting state variable combinations instead of state names.**
5. **Choose flip-flop type (D, J-K, etc.)**
6. **Build excitation table for flip-flop inputs from transition table.**
7. **Derive excitation equations from excitation table.**
8. **Derive output equations from transition/output table.**
9. **Draw logic diagram with excitation logic, output logic, and state memory elements.**

# State Machine Design Using J-K Flip-Flops

- **State machine design step 6 (building excitation table for flip-flop inputs from transition table):**
  - When using D flip-flops, since the next state  $Q^* = D$ , the excitation table is the same as the transition table with  $Q^*$  replaced with D.
  - In the case of J-K flip-flops, the next state is given by:  
 $Q^* = J \cdot Q' + K' \cdot Q$
  - In this case we cannot rearrange the characteristic equation to find separate equations for J, K.
  - Instead an application (or excitation) table for J-K flip-flops is used to obtain the corresponding values of J, K for a given  $Q$  to  $Q^*$  transition:


Q	Q*	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

J-K Flip-Flop Excitation Table

# State Machine Design Example 1:
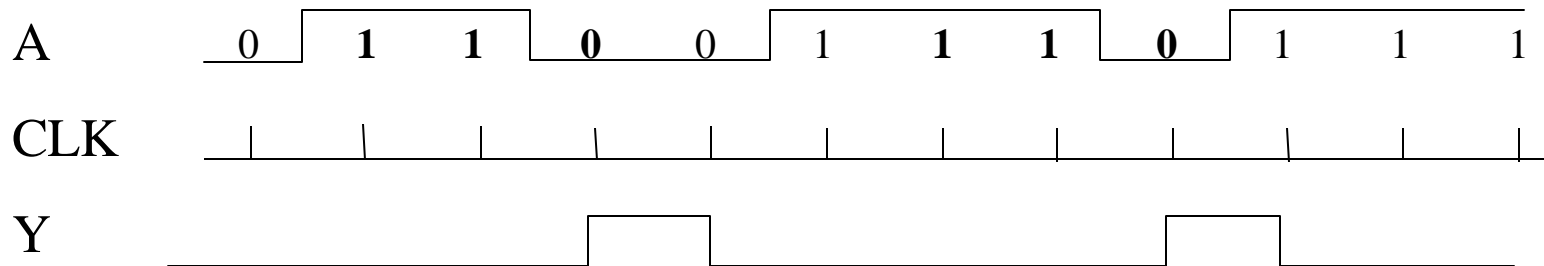
## 110 Detector (Repeated Using J-K Flip-Flops)

- **Word description (110 input sequence detector):**
  - Design a state machine with input A and output Y.
  - Y should be 1 whenever the sequence 1 1 0 has been detected on A on the last 3 consecutive rising clock edges (or ticks).
  - Otherwise,  $Y = 0$
- **Timing diagram interpretation of word description (only rising clock edges are shown):**



# State Machine Design Example 1: 110 Detector

## Step 1: State/Output Table and Diagram


State Table

S	A		Y
	0	1	
No1s	No1s	First1	0
First1	No1s	Two1s	0
Two1s	ALL	Two1s	0
ALL	No1s	First1	1

S\*

Reset

State Diagram

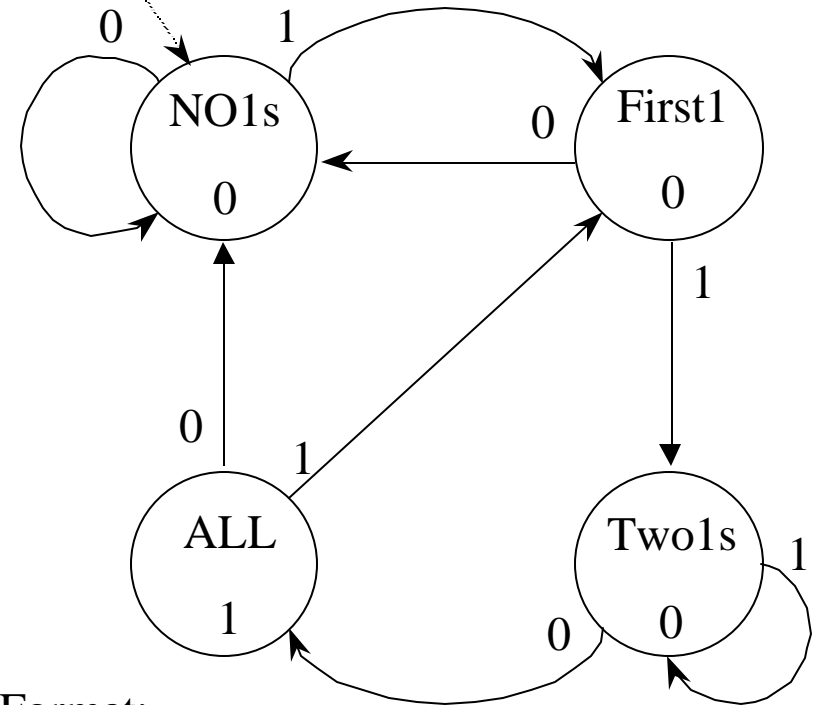

Format:

Arc: input A

Node: state/output Y

# State Machine Design Example 1: 110 Detector

## Using J-K Flip-flops

- Steps 1-4: No change.

Transition Table (step 4):

		A		Y
Q1	Q2	0	1	
0	0	00	01	0
0	1	00	11	0
1	1	10	11	0
1	0	00	01	1

Q1\* Q2\*

Q	Q*	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

J-K Flip-Flop Excitation Table

Excitation table (Step 6):

		A		Y
Q1	Q2	0	1	
0	0	0d, 0d	0d, 1d	0
0	1	0d, d1	1d, d0	0
1	1	d0, d1	d0, d0	0
1	0	d1, 0d	d1, 1d	1

J1 K1, J2 K2

- Step 5: Choose J-K Flip-Flops
- Step 6: Excitation table: Use J-K Flip-Flop Excitation Table.

# State Machine Design Example 1: 110 Detector Using J-K FF

## Steps 7, 8 : Excitation/Output Equations

- Step 7: Excitation equations:  $J1, K1, J2, K2 = F(A, Q1, Q2)$

J1 :

		Q1 Q2			
		00	01	11	10
A	0	0	0	d	d
	1	0	1	d	d

$$J1 = Q2 \cdot A$$

J2 :

		Q1 Q2			
		00	01	11	10
A	0	0	d	d	0
	1	1	d	d	1

$$J2 = A$$

K1 :

		Q1 Q2			
		00	01	11	10
A	0	d	d	0	1
	1	d	d	0	1

$$K1 = Q2'$$

K2 :

		Q1 Q2			
		00	01	11	10
A	0	d	1	1	d
	1	d	0	0	d

$$K2 = A'$$

- Step 8: Output equation:  $Y = G(Q1, Q2)$

$$Y = Q1 \cdot Q2' \text{ (directly read from transition table)}$$