

Major CPU Design Steps

1. Analyze instruction set operations using independent RTN

ISA => RTN => datapath requirements.

- This provides the the required datapath components and how they are connected to meet ISA requirements.

2. Select required datapath components, connections & establish clock methodology (e.g clock edge-triggered).

+ Determine number of cycles per instruction and operations in each cycle.

3. Assemble datapath meeting the requirements.

4. Identify and define the function of all control points or signals needed by the datapath.

- Analyze implementation of each instruction to determine setting of control points that affects its operations and register transfer.

For each cycle of the instruction

5. Design & assemble the control logic.


- Hard-Wired: Finite-state machine implementation.

- Microprogrammed.

i.e using a control program

Single Cycle MIPS Datapath: CPI = 1, Long Clock Cycle

$$T = I \times CPI \times C$$

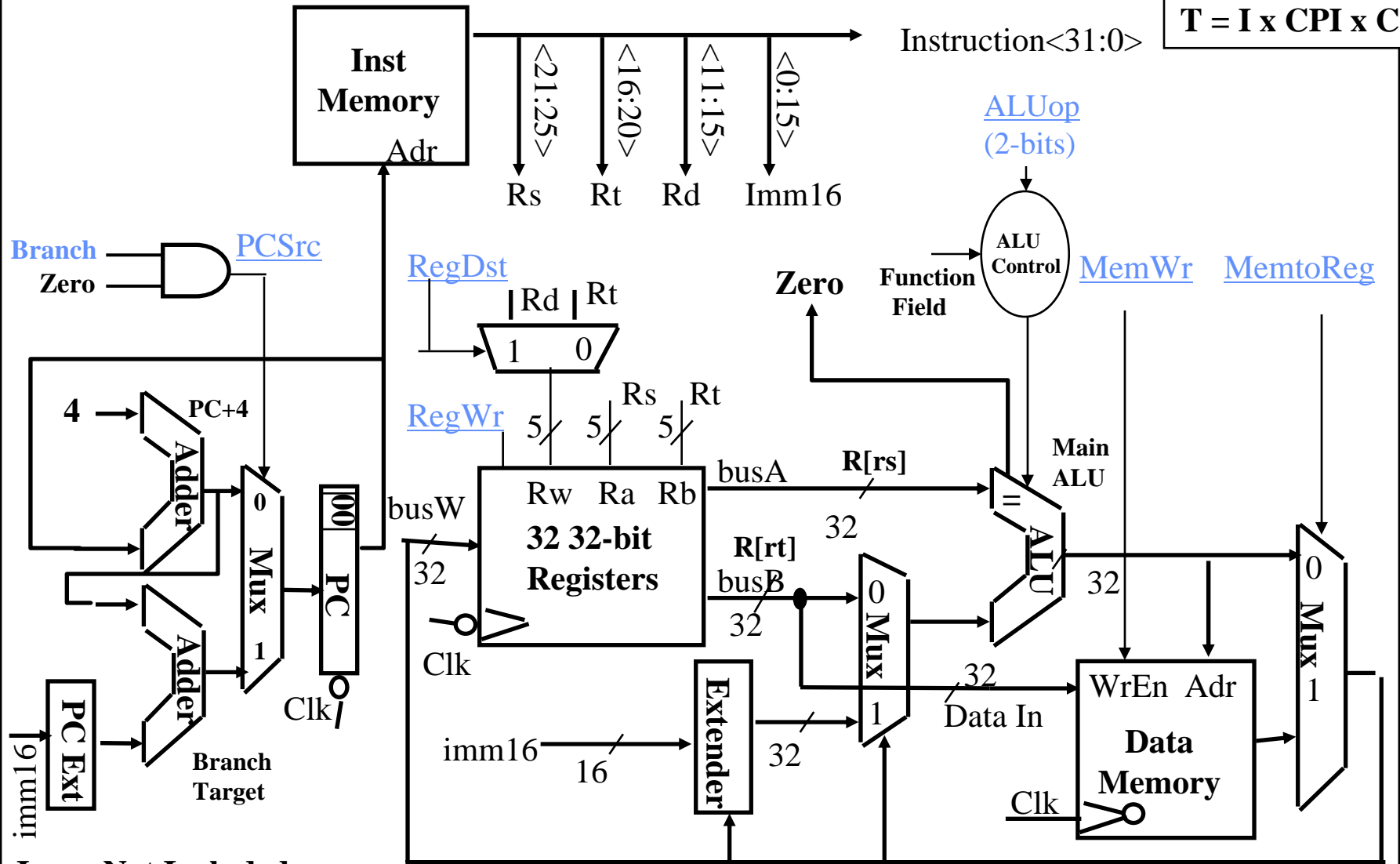


Jump Not Included

(Includes ORI not in book version)

EECC550 - Shaaban

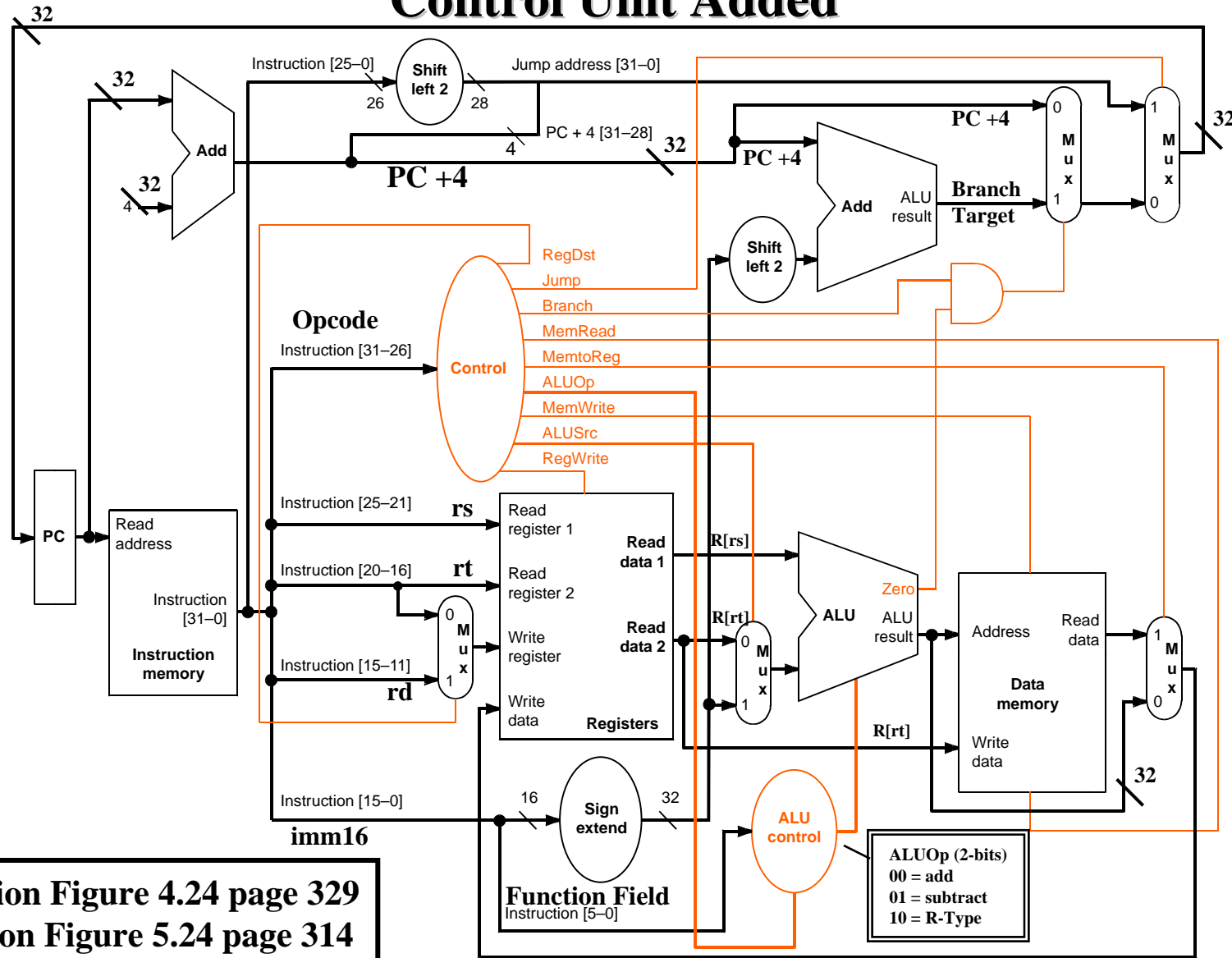Single Cycle MIPS Datapath Extended To Handle Jump with Control Unit Added



4th Edition Figure 4.24 page 329
 3rd Edition Figure 5.24 page 314

In this book version, ORI is not supported—no zero extend of immediate needed.

EECC550 - Shaaban

Drawbacks of Single-Cycle Processor

$$\text{CPI} = 1$$

1. Long cycle time:

- All instructions must take as much time as the slowest:
 - Cycle time for load is longer than needed for all other instructions.
- Real memory is not as well-behaved as idealized memory
 - Cannot always complete data access in one (short) cycle.

2. Impossible to implement complex, variable-length instructions and complex addressing modes in a single cycle.

- e.g indirect memory addressing.


3. High and duplicate hardware resource requirements

- Any hardware functional unit cannot be used more than once in a single cycle (e.g. ALUs).

4. Cannot pipeline (overlap) the processing of one instruction with the previous instructions.

- (instruction pipelining, 4th edition chapter 4 – 3rd edition ch. 6).

Abstract View of Single Cycle CPU

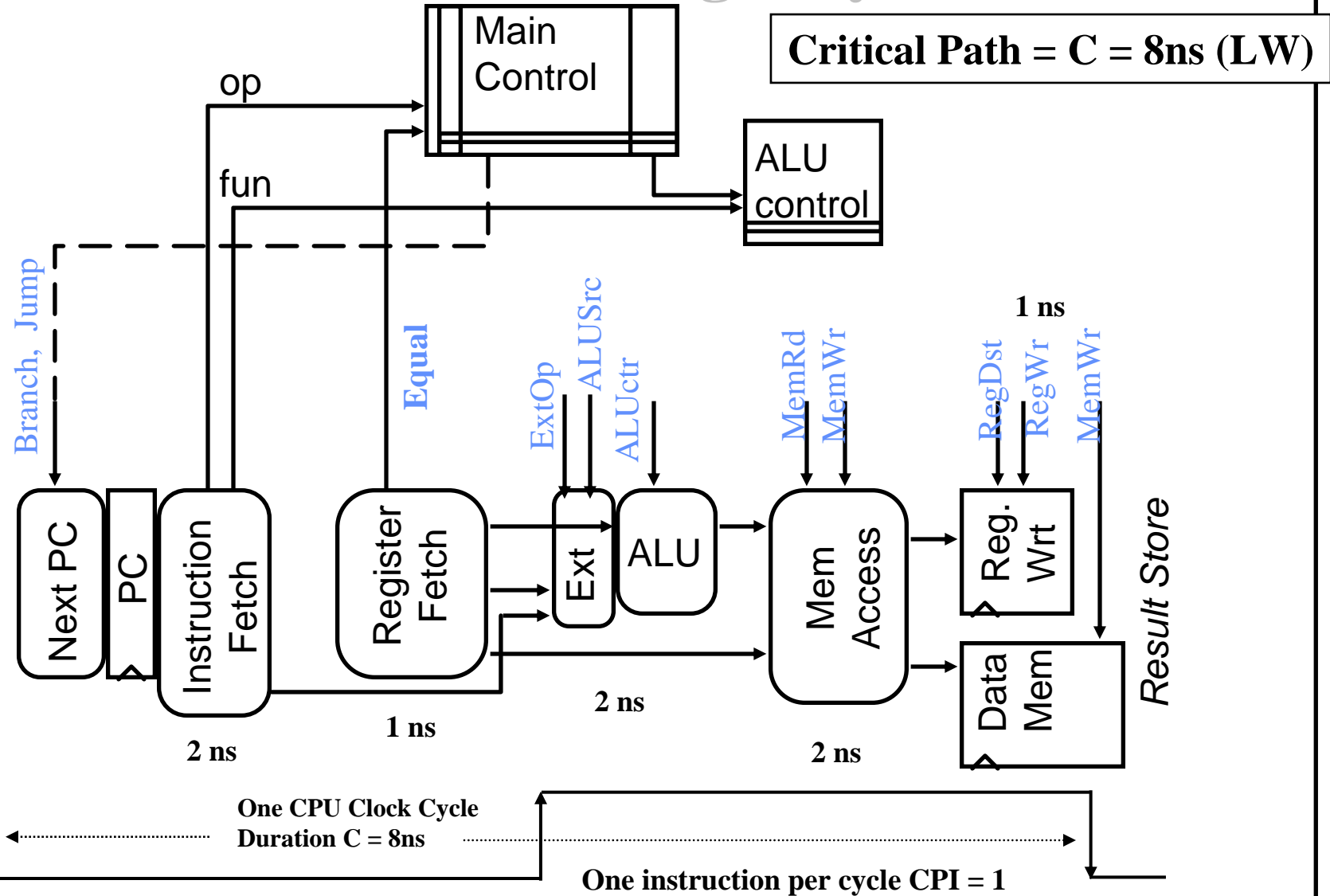


Assuming the following datapath/control hardware components delays:

Memory Units: 2 ns ALU and adders: 2 ns
 Register File: 1 ns Control Unit < 1 ns

EECC550 - Shaaban

Single Cycle Instruction Timing

Arithmetic & Logical

 

Load

2 ns

1 ns

2 ns

2 ns

1 ns



Store

(Determines CPU clock cycle, C)




Branch



Critical Path: Load - LW (e.g C = 8 ns)

Clock Cycle Time & Critical Path

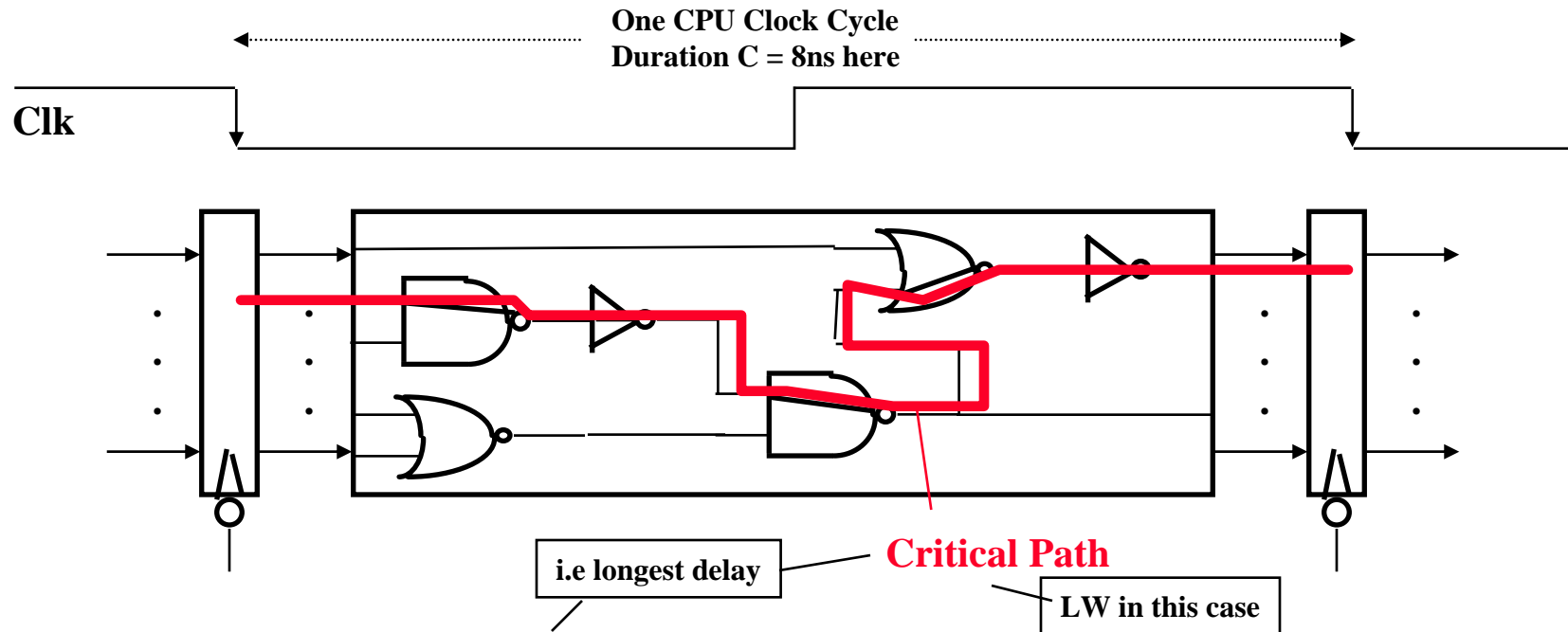

- **Critical path**: the slowest path between any two storage devices
- **Clock Cycle time is a function of the critical path, and must be greater than:**
 - **Clock-to-Q + Longest Delay Path through the Combination Logic + Setup + Clock Skew**


Assuming the following datapath/control hardware components delays:

Memory Units: 2 ns ALU and adders: 2 ns
Register File: 1 ns Control Unit < 1 ns


EECC550 - Shaaban

Reducing Cycle Time: Multi-Cycle Design

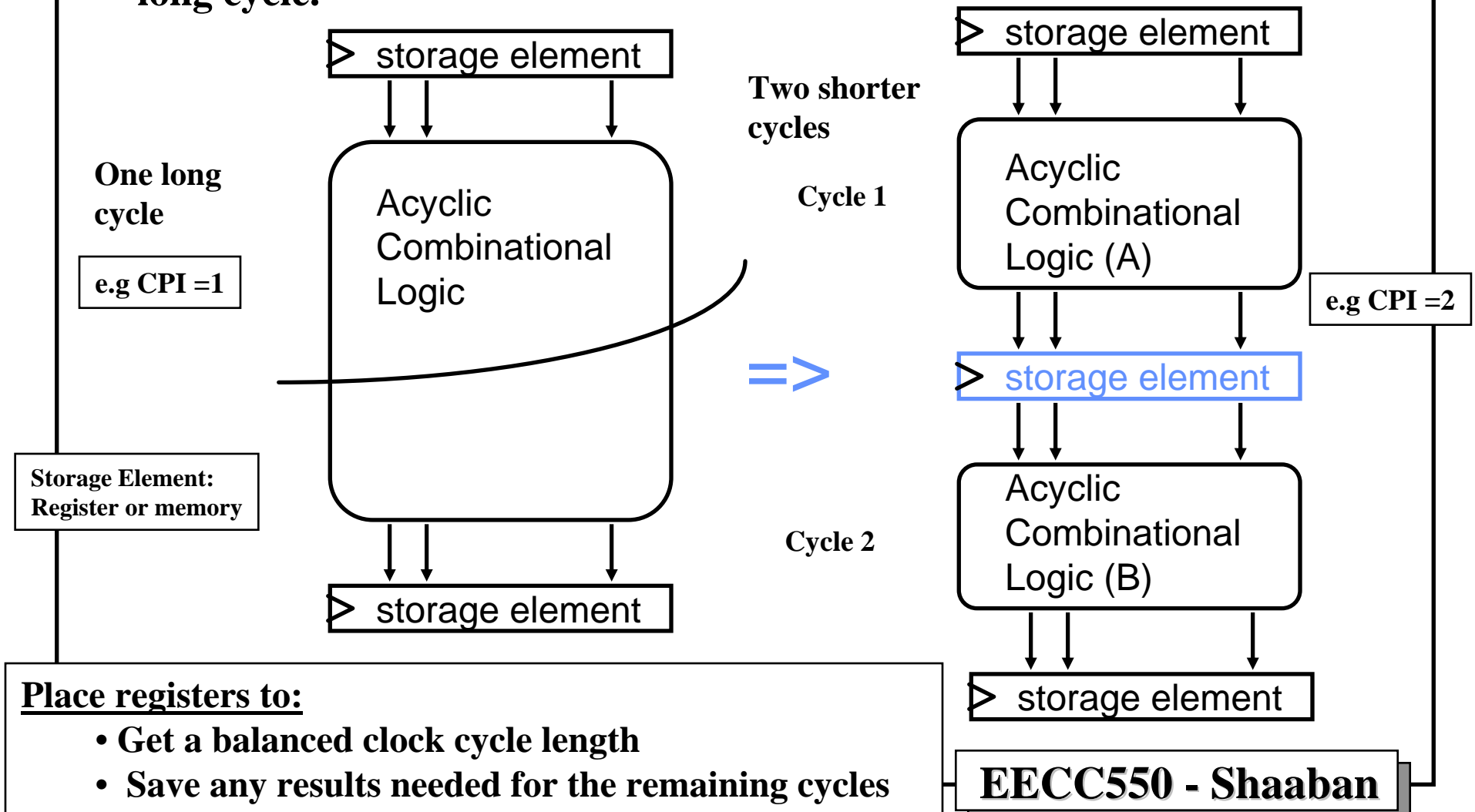- Cut combinational dependency graph by inserting registers / latches.
- The same work is done in two or more shorter cycles, rather than one long cycle.



Basic MIPS Instruction Processing Steps

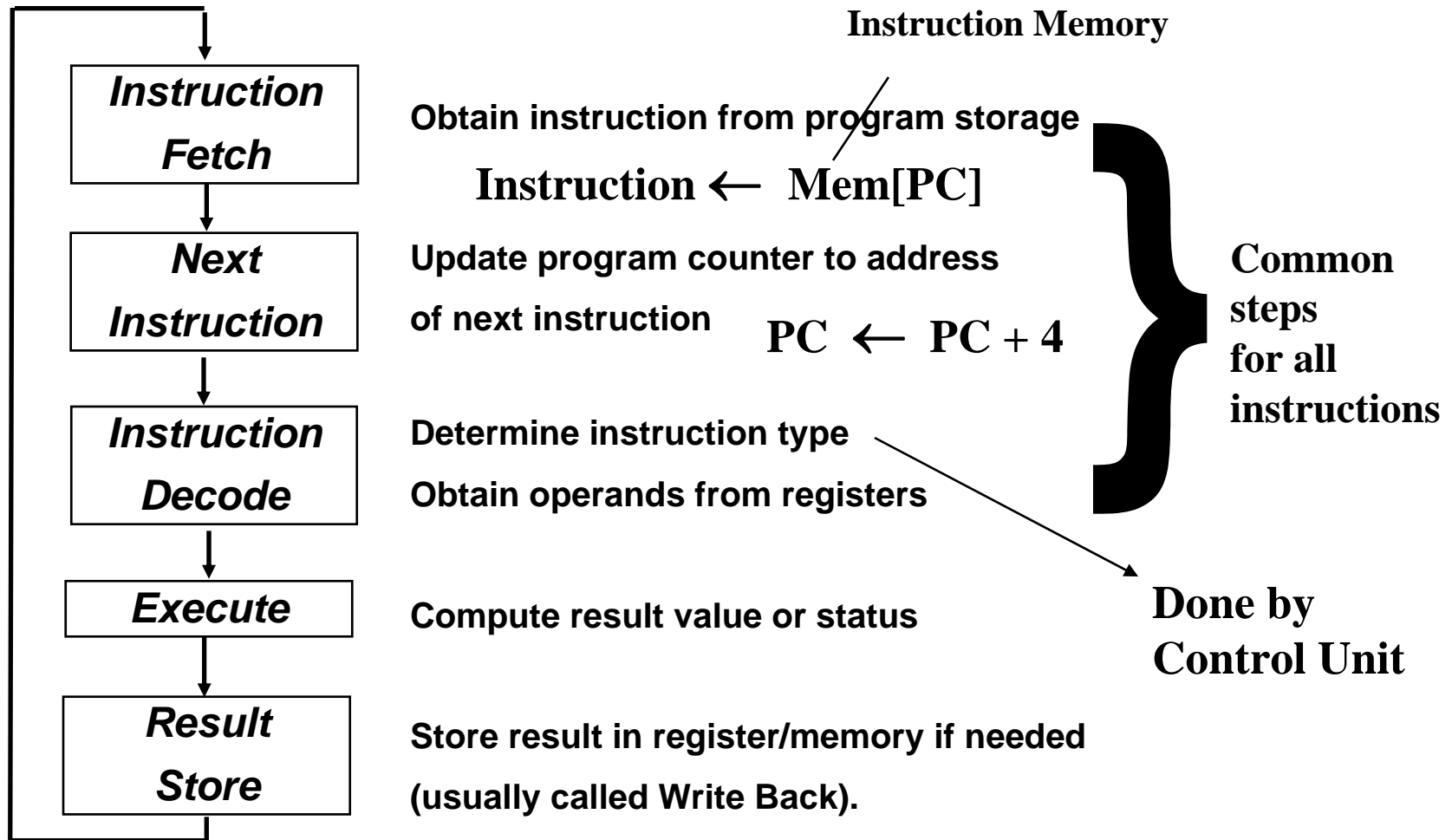


$$T = I \times \text{CPI} \times C$$

EECC550 - Shaaban

Partitioning The Single Cycle Datapath

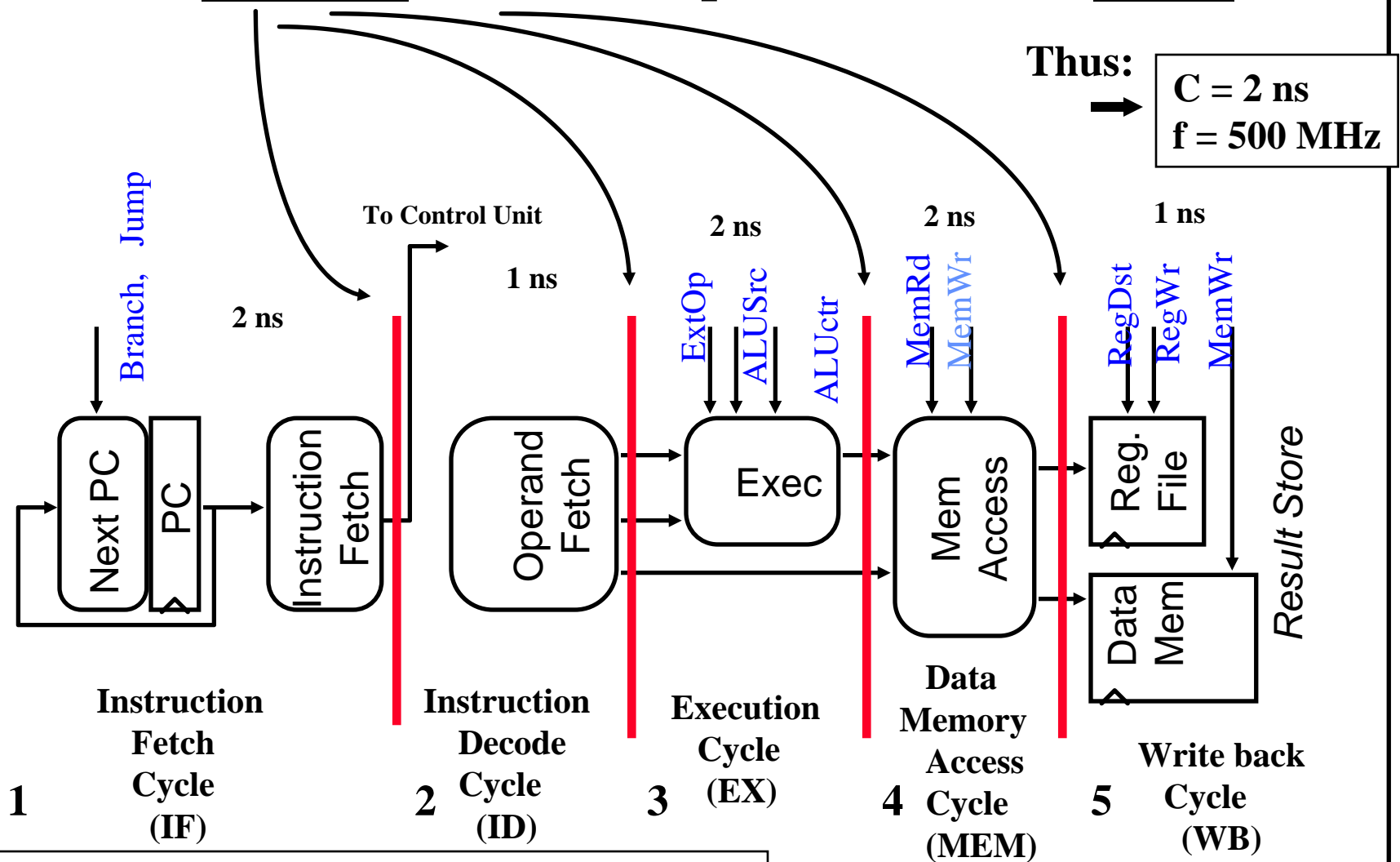
Add registers between steps to break into cycles



Place registers to:

- Get a balanced clock cycle length
- Save any results needed for the remaining cycles

Example Multi-cycle Datapath

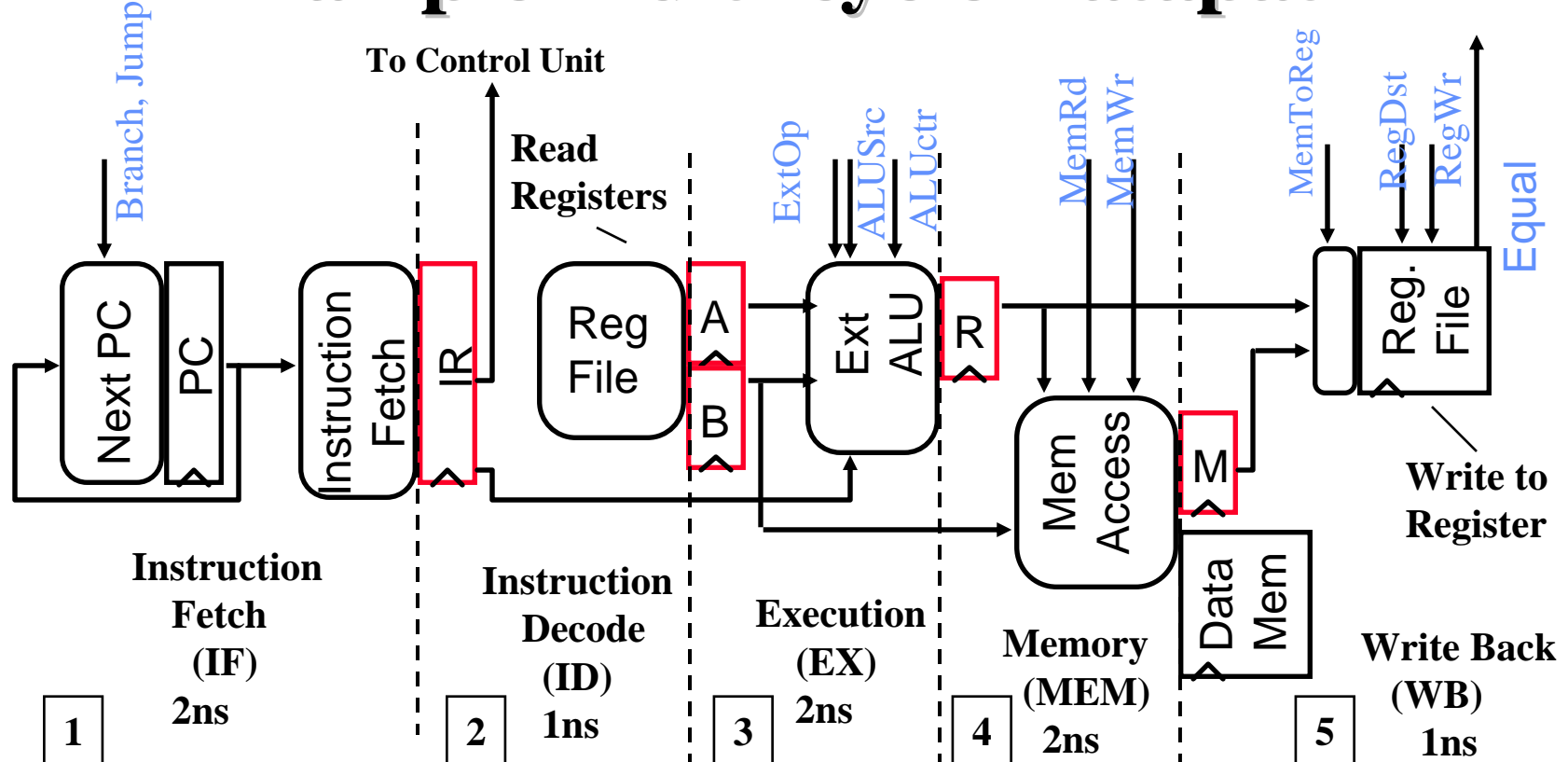

Registers added: All clock-edge triggered (not shown register write enable control lines)

IR: Instruction register

A, B: Two registers to hold operands read from register file. i.e R[rs], R[rt]

R: or ALUOut, holds the output of the main ALU ALU result

M: or Memory data register (MDR) to hold data read from data memory

CPU Clock Cycle Time: Worst cycle delay = $C = 2ns$ (ignoring MUX, CLK-Q delays)

Assuming the following datapath/control hardware components delays:

Memory Units: 2 ns ALU and adders: 2 ns
Register File: 1 ns Control Unit < 1 ns

Thus Clock Rate:
 $f = 1 / 2ns = 500 \text{ MHz}$

EECC550 - Shaaban

Operations (Dependant RTN) for Each Cycle


| | R-Type | Logic Immediate | Load | Store | Branch |
|-----|--|--|--|---|--|
| IF | Instruction Fetch $IR \leftarrow Mem[PC]$ | $IR \leftarrow Mem[PC]$ | $IR \leftarrow Mem[PC]$ | $IR \leftarrow Mem[PC]$ | $IR \leftarrow Mem[PC]$ |
| ID | Instruction Decode $A \leftarrow R[rs]$ $B \leftarrow R[rt]$ | $A \leftarrow R[rs]$ $B \leftarrow R[rt]$ | $A \leftarrow R[rs]$ $B \leftarrow R[rt]$ | $A \leftarrow R[rs]$ $B \leftarrow R[rt]$ | $A \leftarrow R[rs]$ $B \leftarrow R[rt]$ |
| EX | Execution $R \leftarrow A \text{ funct } B$ | $R \leftarrow A \text{ OR } ZeroExt[imm16]$ | $R \leftarrow A + SignEx(Im16)$ | $R \leftarrow A + SignEx(Im16)$ | $Zero \leftarrow A - B$ If $Zero = 1$: $PC \leftarrow PC + 4 +$ $(SignExt(imm16) \times 4)$ else (i.e $Zero = 0$): $PC \leftarrow PC + 4$ |
| MEM | Memory | | $M \leftarrow Mem[R]$ | $Mem[R] \leftarrow B$ $PC \leftarrow PC + 4$ | |
| WB | Write Back $R[rd] \leftarrow R$ $PC \leftarrow PC + 4$ | $R[rt] \leftarrow R$ $PC \leftarrow PC + 4$ | $R[rt] \leftarrow M$ $PC \leftarrow PC + 4$ | | |

Instruction Fetch (IF) & Instruction Decode cycles are common for all instructions

EECC550 - Shaaban

MIPS Multi-Cycle Datapath:

Five Cycles of Load CPI = 5

 

1- Instruction Fetch (IF):

Fetch the instruction from instruction Memory.

2- Instruction Decode (ID):

Operand Register Fetch and Instruction Decode.

3- Execute (EX): Calculate the effective memory address.

4- Memory (MEM): Read the data from the Data Memory.

5- Write Back (WB):

Write the loaded data to the register file. Update PC.

Multi-cycle Datapath Instruction CPI


- **R-Type/Immediate:** Require four cycles, CPI = 4
 - IF, ID, EX, WB
- **Loads:** Require five cycles, CPI = 5
 - IF, ID, EX, MEM, WB
- **Stores:** Require four cycles, CPI = 4
 - IF, ID, EX, MEM
- **Branches/Jumps:** Require three cycles, CPI = 3
 - IF, ID, EX

- **Average or effective program CPI:** $3 \leq \text{CPI} \leq 5$ depending on program profile (instruction mix).

$C = 2 \text{ ns}$ $f = 500 \text{ MHz}$

EECC550 - Shaaban

Single Cycle Vs. Multi-Cycle CPU

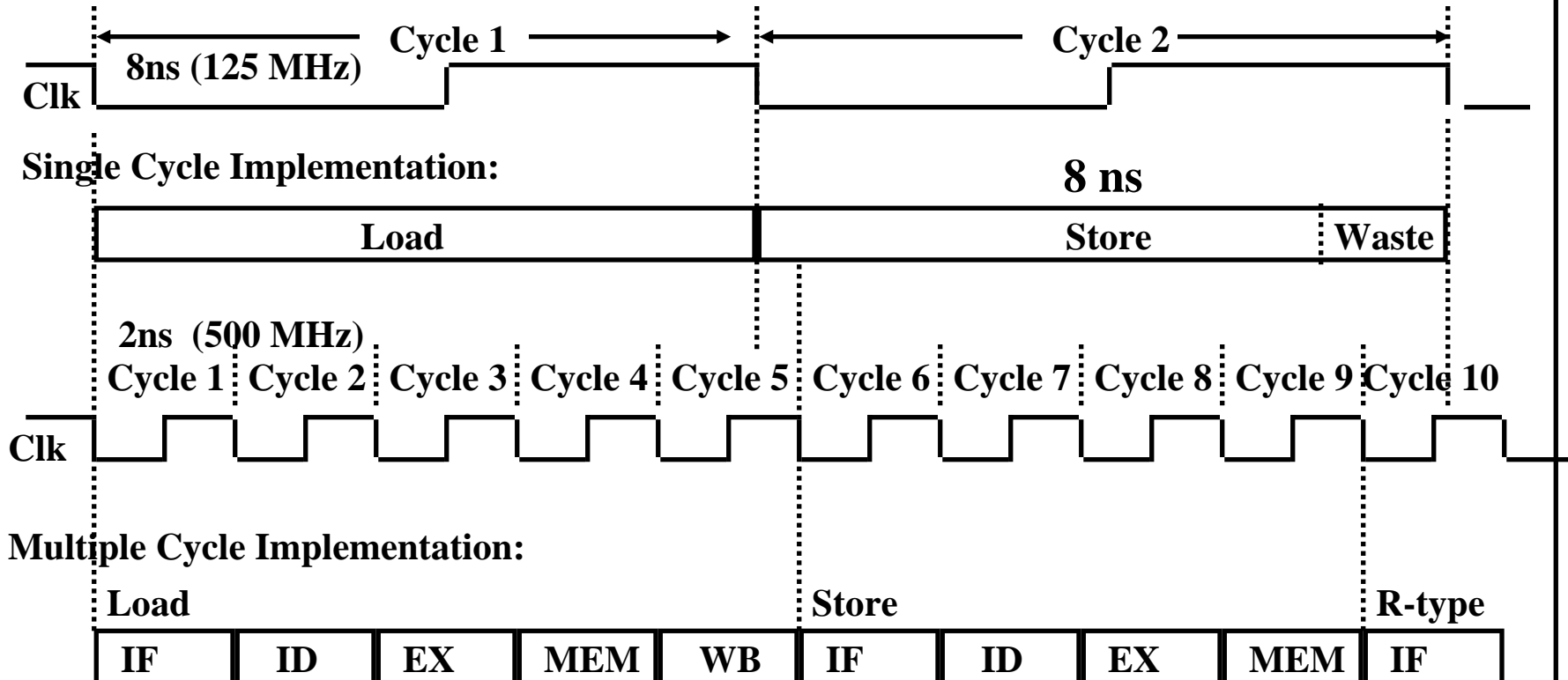

Single-Cycle CPU:

$CPI = 1$ $C = 8ns$ $f = 125 \text{ MHz}$

One million instructions take =

$I \times CPI \times C = 10^6 \times 1 \times 8 \times 10^{-9} = 8 \text{ msec}$

$T = I \times CPI \times C$

Multi-Cycle CPU:

$1 \leq CPI \leq 5$

$CPI = 3 \text{ to } 5$ $C = 2ns$ $f = 500 \text{ MHz}$

One million instructions take from

$10^6 \times 3 \times 2 \times 10^{-9} = 6 \text{ msec}$

to $10^6 \times 5 \times 2 \times 10^{-9} = 10 \text{ msec}$

depending on instruction mix used.

Assuming the following datapath/control hardware components delays:


Memory Units: 2 ns ALU and adders: 2 ns
Register File: 1 ns Control Unit < 1 ns

EECC550 - Shaaban

Finite State Machine (FSM) Control Model


AKA Hardwired Control

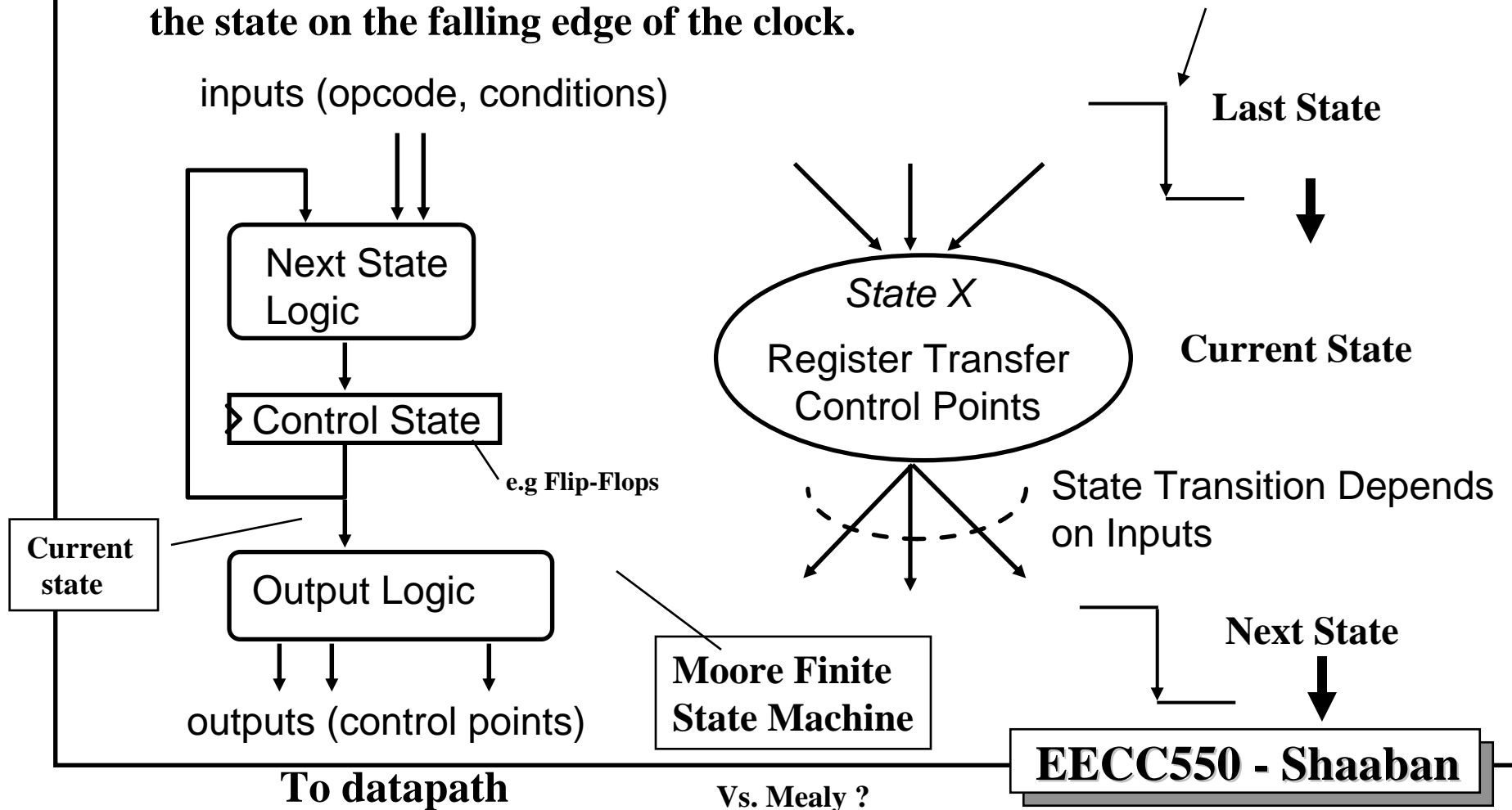- State specifies control points (outputs) for Register Transfer.
- Control points (outputs) are assumed to depend only on the current state and not inputs (i.e. Moore finite state machine)
- Transfer (register/memory writes) and state transition occur upon exiting the state on the falling edge of the clock.



Control Specification For Multi-cycle CPU

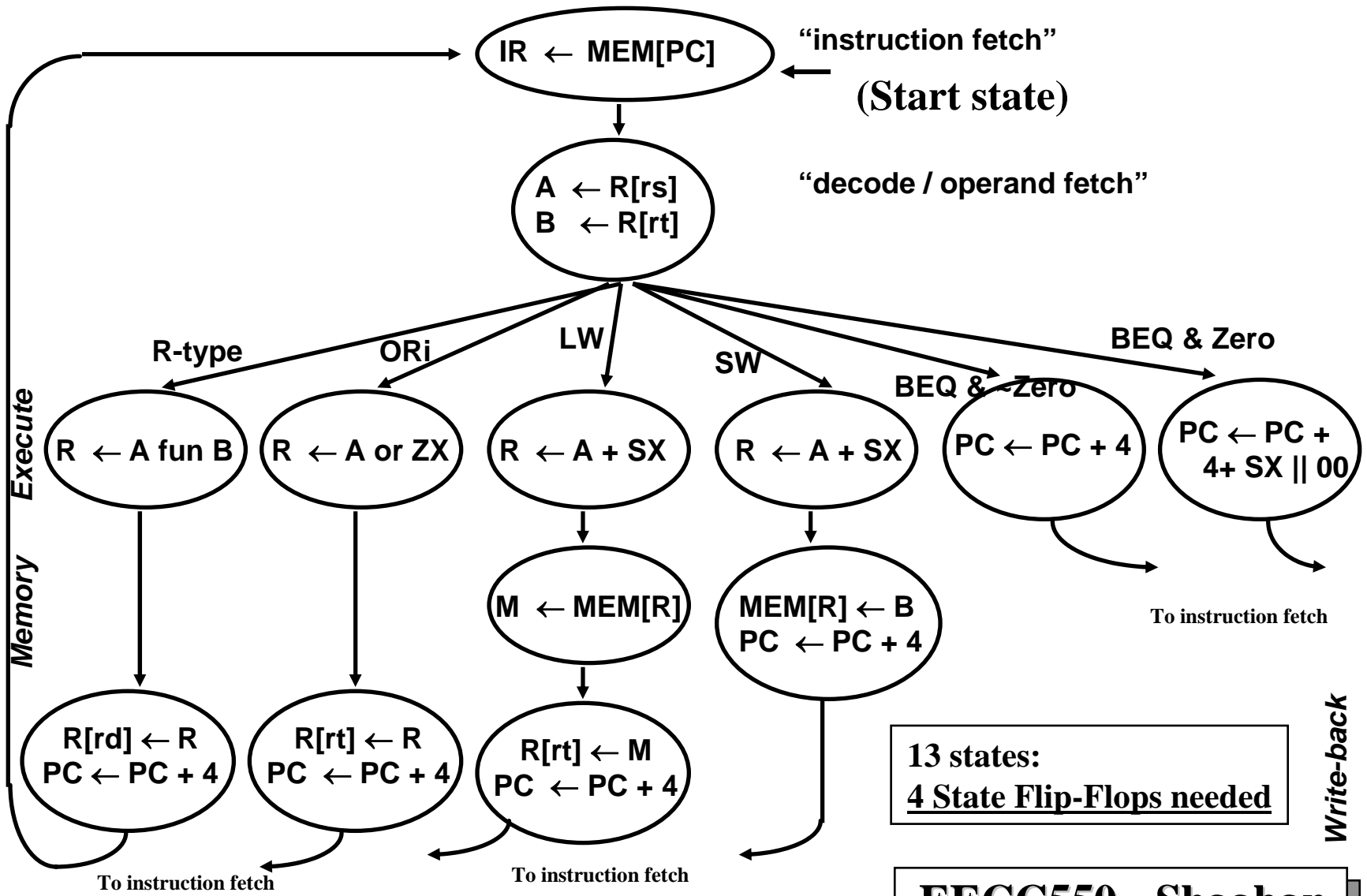Finite State Machine (FSM) - State Transition Diagram



Traditional FSM Controller

| state | op | cond | next state | control points |
|-------|----|------|------------|----------------|
| | | | | |

Outputs (to datapath)

State Transition Table

Inputs

Next State Logic

Output Logic

Equal

Opcode

Current State



State

Outputs (Control points)

To datapath

datapath State

State register (4 Flip-Flops)

EECC550 - Shaaban


Traditional FSM Controller

datapath + state diagram \Rightarrow control

- **Translate RTN statements into control points.**
- **Assign states.**
- **Implement the controller.**

More on FSM controller implementation in Appendix C

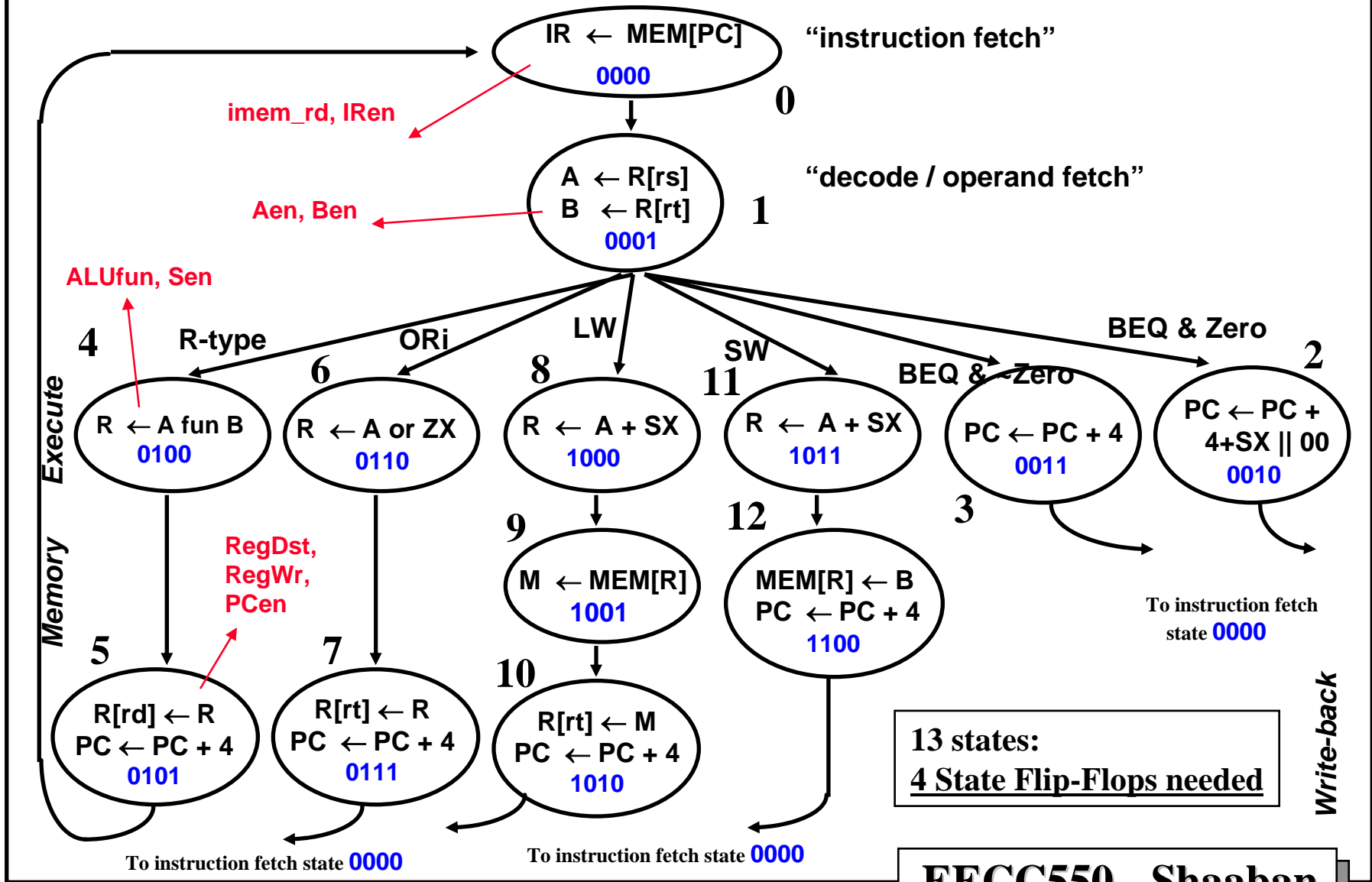Mapping RTNs To Control Points Examples & State Assignments



Detailed Control Specification – (Partial) State Transition Table


| | Current State | Op field | Z | Next | IR | PC en sel | Ops A B | Exec Ex Sr ALU S | Mem R W M | Write-Back M-R Wr Dst |
|-----|---------------|----------|---|------|----|-----------|------------------------------|------------------|-----------|-----------------------|
| IF | 0000 | ?????? | ? | 0001 | 1 | | | | | |
| | 0001 | BEQ | 0 | 0011 | | | 1 1 | | | |
| ID | 0001 | BEQ | 1 | 0010 | | | 1 1 | | | |
| | 0001 | R-type | x | 0100 | | | 1 1 | | | |
| | 0001 | orI | x | 0110 | | | 1 1 | | | |
| | 0001 | LW | x | 1000 | | | 1 1 | | | |
| | 0001 | SW | x | 1011 | | | 1 1 | | | |
| BEQ | 0010 | xxxxxx | x | 0000 | | 1 1 | Can be combined in one state | | | |
| | 0011 | xxxxxx | x | 0000 | | 1 0 | | | | |
| R | 0100 | xxxxxx | x | 0101 | | | | 0 1 fun 1 | | |
| | 0101 | xxxxxx | x | 0000 | | 1 0 | | | 0 1 1 | |
| ORI | 0110 | xxxxxx | x | 0111 | | | | 0 0 or 1 | | |
| | 0111 | xxxxxx | x | 0000 | | 1 0 | | | 0 1 0 | |
| LW | 1000 | xxxxxx | x | 1001 | | | | 1 0 add 1 | | |
| | 1001 | xxxxxx | x | 1010 | | | | | 1 0 1 | |
| | 1010 | xxxxxx | x | 0000 | | 1 0 | | | 1 1 0 | |
| SW | 1011 | xxxxxx | x | 1100 | | | | 1 0 add 1 | | |
| | 1100 | xxxxxx | x | 0000 | | 1 0 | | | 0 1 | |

More on FSM controller implementation in Appendix C


EECC550 - Shaaban

Alternative Multiple Cycle Datapath (In Textbook)

- Minimizes Hardware: 1 memory, 1 ALU

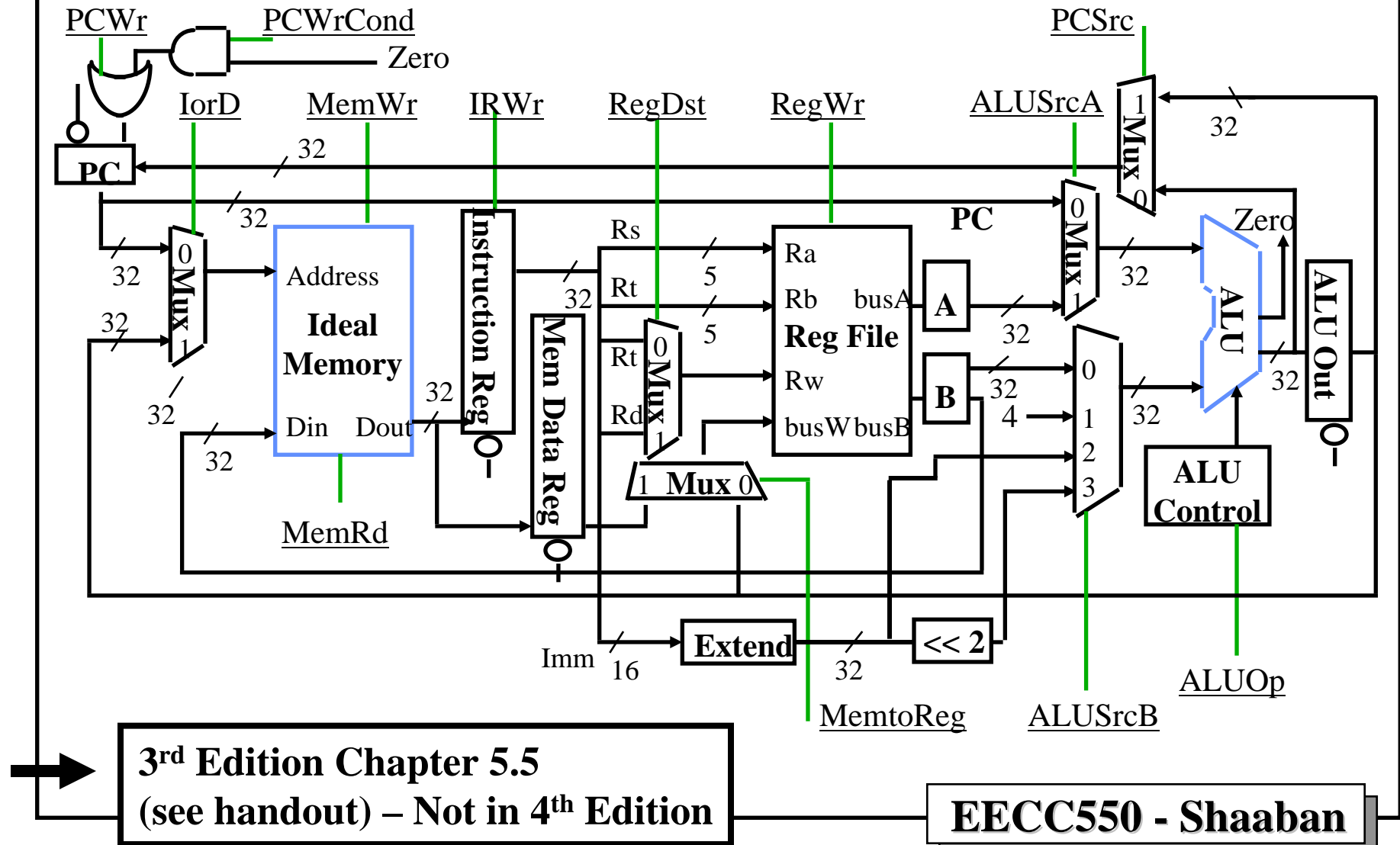

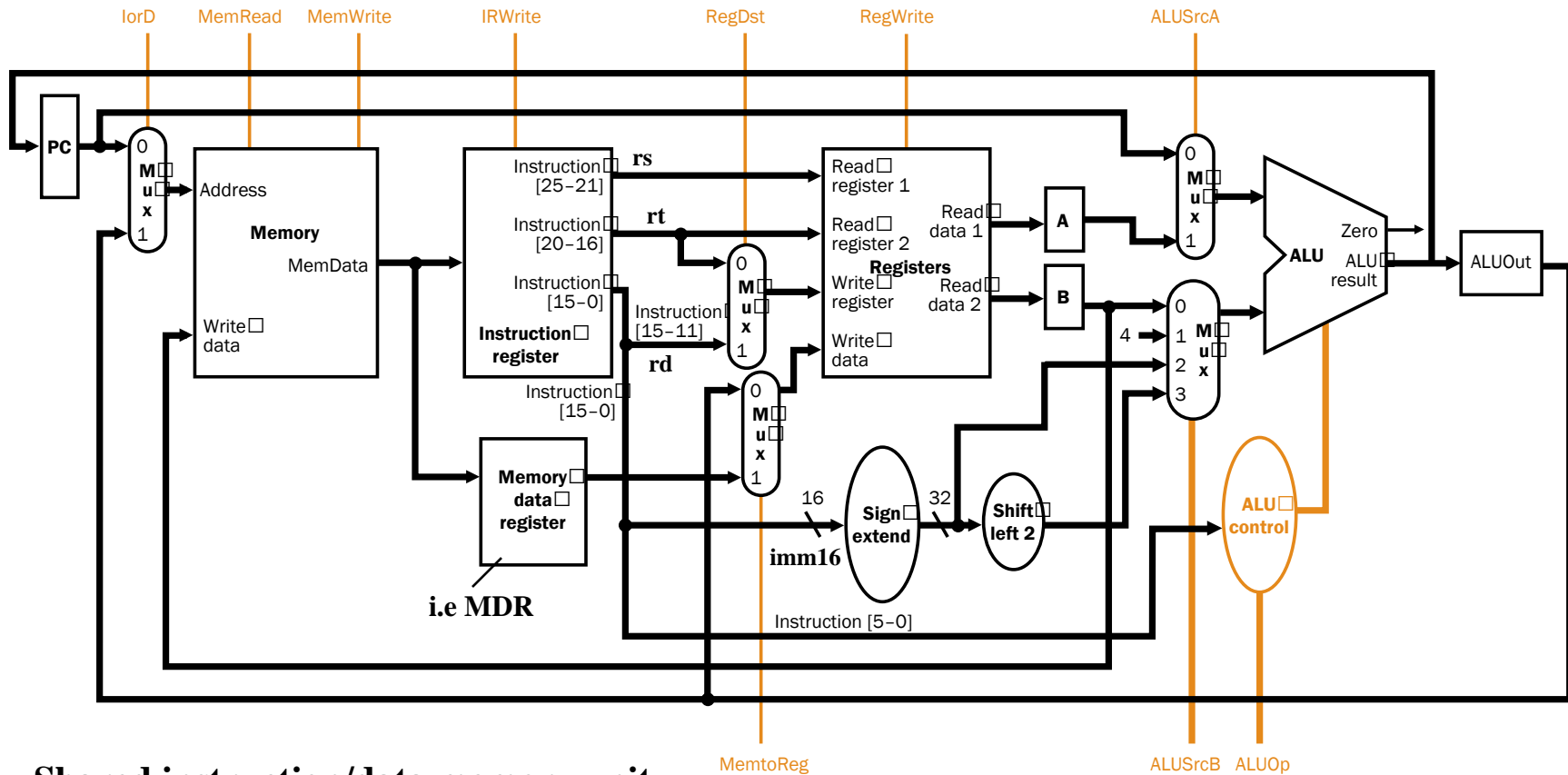Alternative Multiple Cycle Datapath (In Textbook)




- Shared instruction/data memory unit
- A single ALU shared among instructions
- Shared units require additional or widened multiplexers
- Temporary registers to hold data between clock cycles of the instruction:
 - Additional registers:
Instruction Register (IR), Memory Data Register (MDR), A, B, ALUOut

(Figure 5.27 page 322)

EECC550 - Shaaban

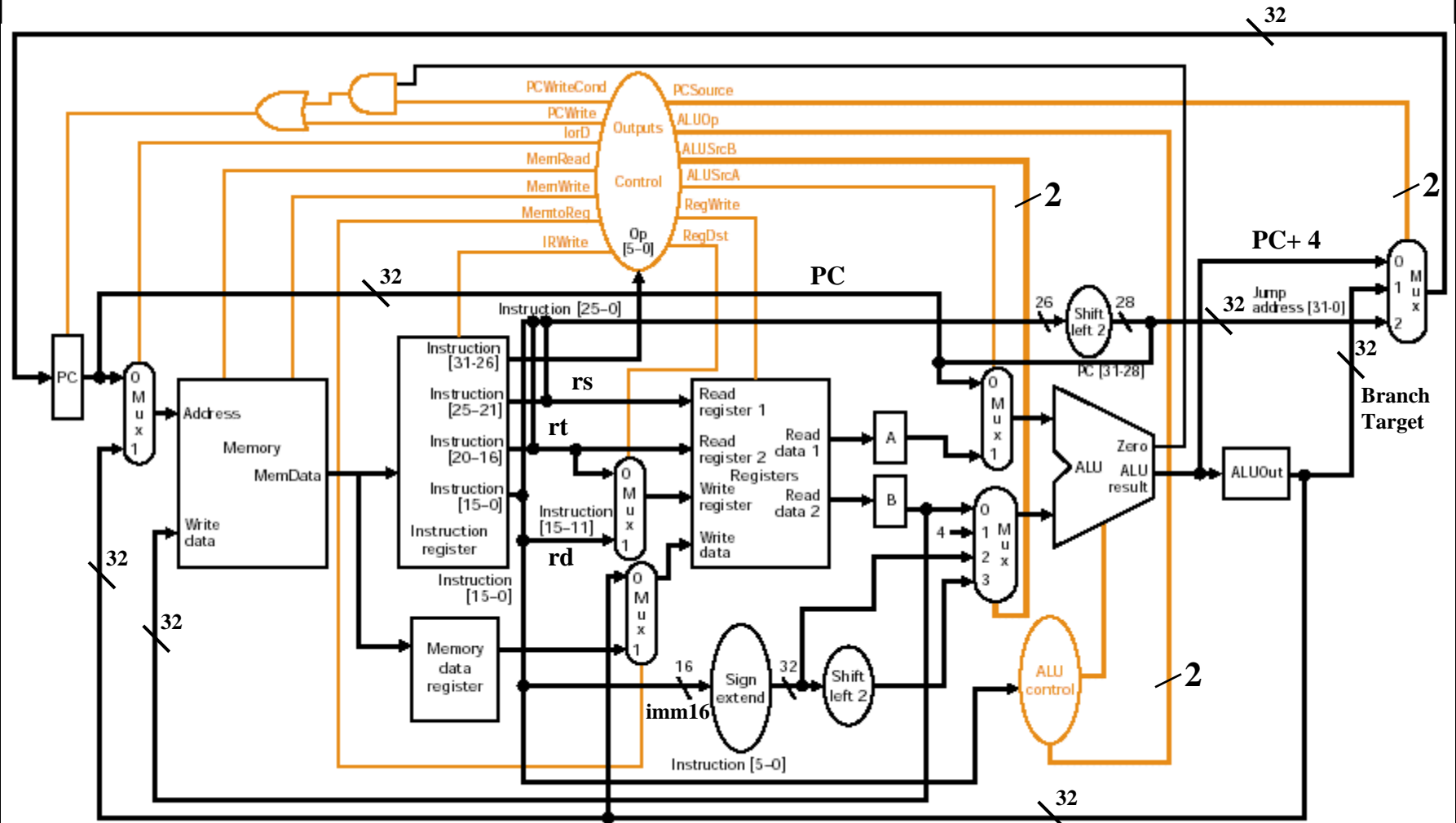Alternative Multiple Cycle Datapath With Control Lines (Fig 5.28 In Textbook)



(ORI not supported, Jump supported)

(Figure 5.28 page 323)

The Effect of The 1-bit Control Signals

| Signal Name | Effect when deasserted (=0) | Effect when asserted (=1) |
|-----------------------------------|--|--|
| RegDst | The register destination number for the write register comes from the rt field (instruction bits 20:16). | The register destination number for the write register comes from the rd field (instruction bits 15:11). |
| RegWrite | None | The register on the write register input is written with the value on the Write data input. |
| ALUSrcA | The first ALU operand is the PC | The First ALU operand is register A (i.e R[rs]) |
| MemRead | None | Content of memory specified by the address input are put on the memory data output. |
| MemWrite | None | Memory contents specified by the address input is replaced by the value on the Write data input. |
| MemtoReg | The value fed to the register write data input comes from ALUOut register. | The value fed to the register write data input comes from data memory register (MDR). |
| IorD | The PC is used to supply the address to the memory unit. | The ALUOut register is used to supply the the address to the memory unit. |
| IRWrite | None | The output of the memory is written into Instruction Register (IR) |
| PCWrite | None | The PC is written; the source is controlled by PCSource |
| PCWriteCond i.e. Branch | None | The PC is written if the Zero output of the ALU is also active. |

(Figure 5.29 page 324)

EECC550 - Shaaban

The Effect of The 2-bit Control Signals

| Signal Name | Value (Binary) | Effect |
|-------------|----------------|---|
| ALUOp | 00 | The ALU performs an add operation |
| | 01 | The ALU performs a subtract operation |
| | 10 | The funct field of the instruction determines the ALU operation (R-Type) |
| ALUSrcB | 00 | The second input of the ALU comes from register B (i.e R[rs]) |
| | 01 | The second input of the ALU is the constant 4 |
| | 10 | The second input of the ALU is the sign-extended 16-bit immediate (imm16) field of the instruction in IR |
| | 11 | The second input of the ALU is the sign-extended 16-bit immediate field of IR shifted left 2 bits (for branches) |
| PCSource | 00 | Output of the ALU (PC+4) is sent to the PC for writing |
| | 01 | The content of ALUOut (the branch target address) is sent to the PC for writing |
| | 10 | The jump target address (IR[25:0] shifted left 2 bits and concatenated with PC+4[31:28] is sent to the PC for writing i.e jump address |

(Figure 5.29 page 324)


Operations (Dependant RTN) for Each Cycle

| | R-Type | Load | Store | Branch | Jump |
|-----|---|--|--|--|--|
| IF | Instruction Fetch IR ← Mem[PC] PC ← PC + 4 | IR ← Mem[PC] PC ← PC + 4 | IR ← Mem[PC] PC ← PC + 4 | IR ← Mem[PC] PC ← PC + 4 | IR ← Mem[PC] PC ← PC + 4 |
| ID | Instruction Decode A ← R[rs] B ← R[rt] ALUout ← PC + (SignExt(imm16) x4) | A ← R[rs] B ← R[rt] ALUout ← PC + (SignExt(imm16) x4) | A ← R[rs] B ← R[rt] ALUout ← PC + (SignExt(imm16) x4) | A ← R[rs] B ← R[rt] ALUout ← PC + (SignExt(imm16) x4) | A ← R[rs] B ← R[rt] ALUout ← PC + (SignExt(imm16) x4) |
| EX | Execution ALUout ← A funct B | ALUout ← A + SignEx(Imm16) | ALUout ← A + SignEx(Imm16) | Zero ← A - B Zero: PC ← ALUout | PC ← Jump Address |
| MEM | Memory | MDR ← Mem[ALUout] | Mem[ALUout] ← B | | |
| WB | Write Back R[rd] ← ALUout | R[rt] ← MDR | | | |

Instruction Fetch (IF) & Instruction Decode (ID) cycles are common for all instructions

EECC550 - Shaaban

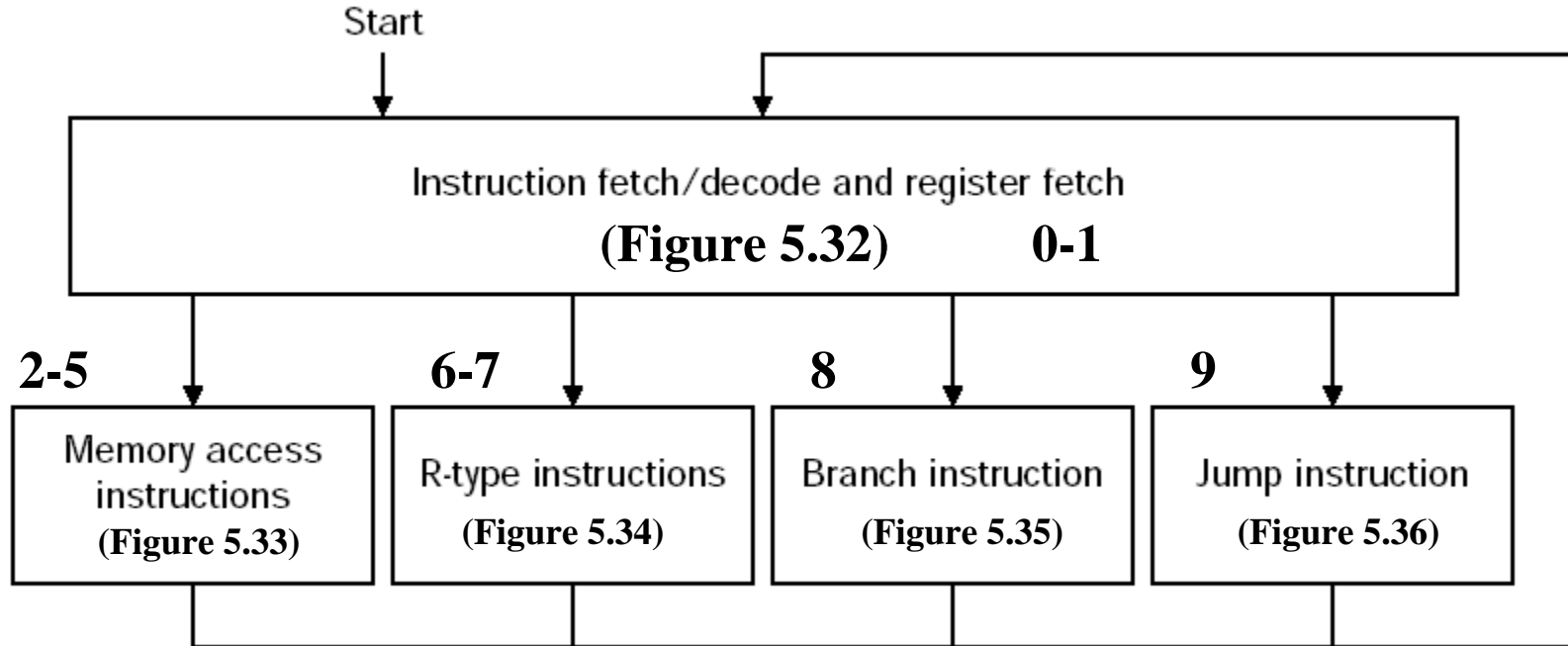
High-Level View of Finite State Machine Control



- **First steps are independent of the instruction class**
- **Then a series of sequences that depend on the instruction opcode**
- **Then the control returns to fetch a new instruction.**
- **Each box above represents one or several state.**

FSM State Transition Diagram (From Book)

(Figure 5.38 page 339)

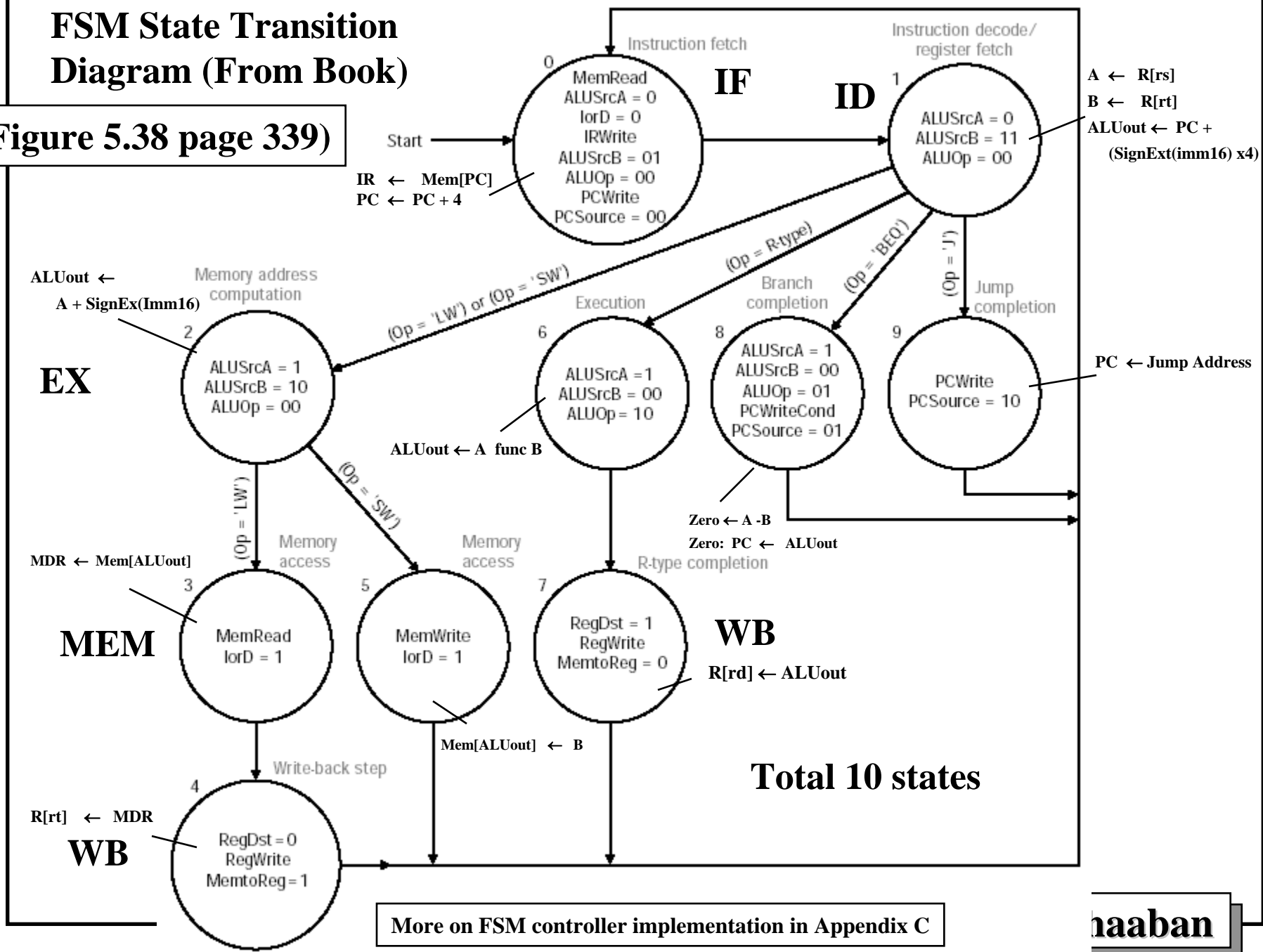

More on FSM controller implementation in Appendix C

naaban


Instruction Fetch (IF) and Decode (ID)

FSM States

$$A \leftarrow R[rs]$$

$$B \leftarrow R[rt]$$

$$ALUout \leftarrow PC + (\text{SignExt}(\text{imm16}) \times 4)$$

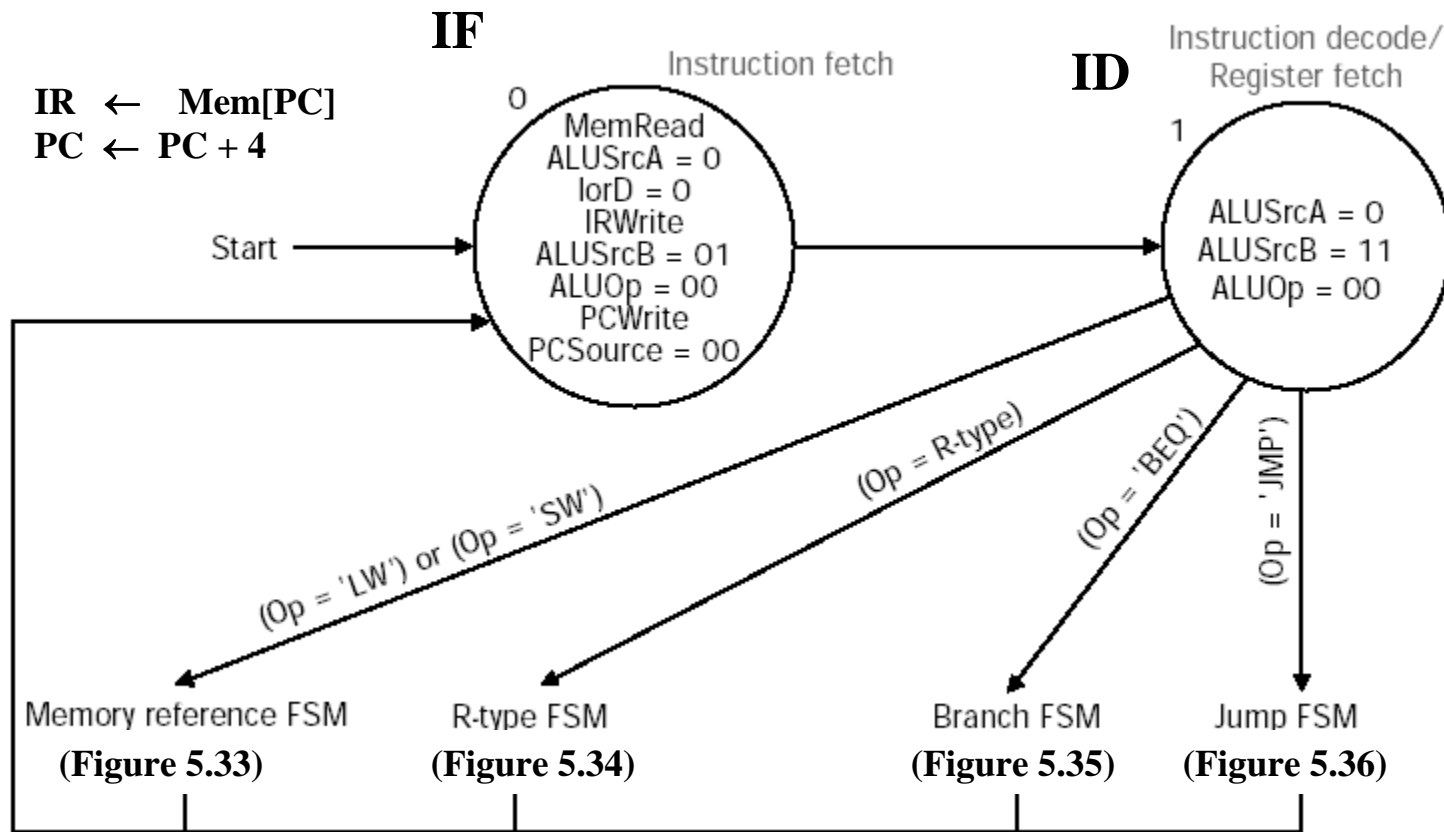


(Figure 5.32 page 333)

EECC550 - Shaaban

Instruction Fetch (IF) Cycle (State 0)

$IR \leftarrow Mem[PC]$
 $PC \leftarrow PC + 4$

| | | | |
|--------------|------------------|-------------|---------------|
| MemRead = 1 | ALUSrcA = 0 | IorD = 0 | IRWrite = 1 |
| ALUSrcB = 01 | ALUOp = 00 (add) | PCWrite = 1 | PCSource = 00 |

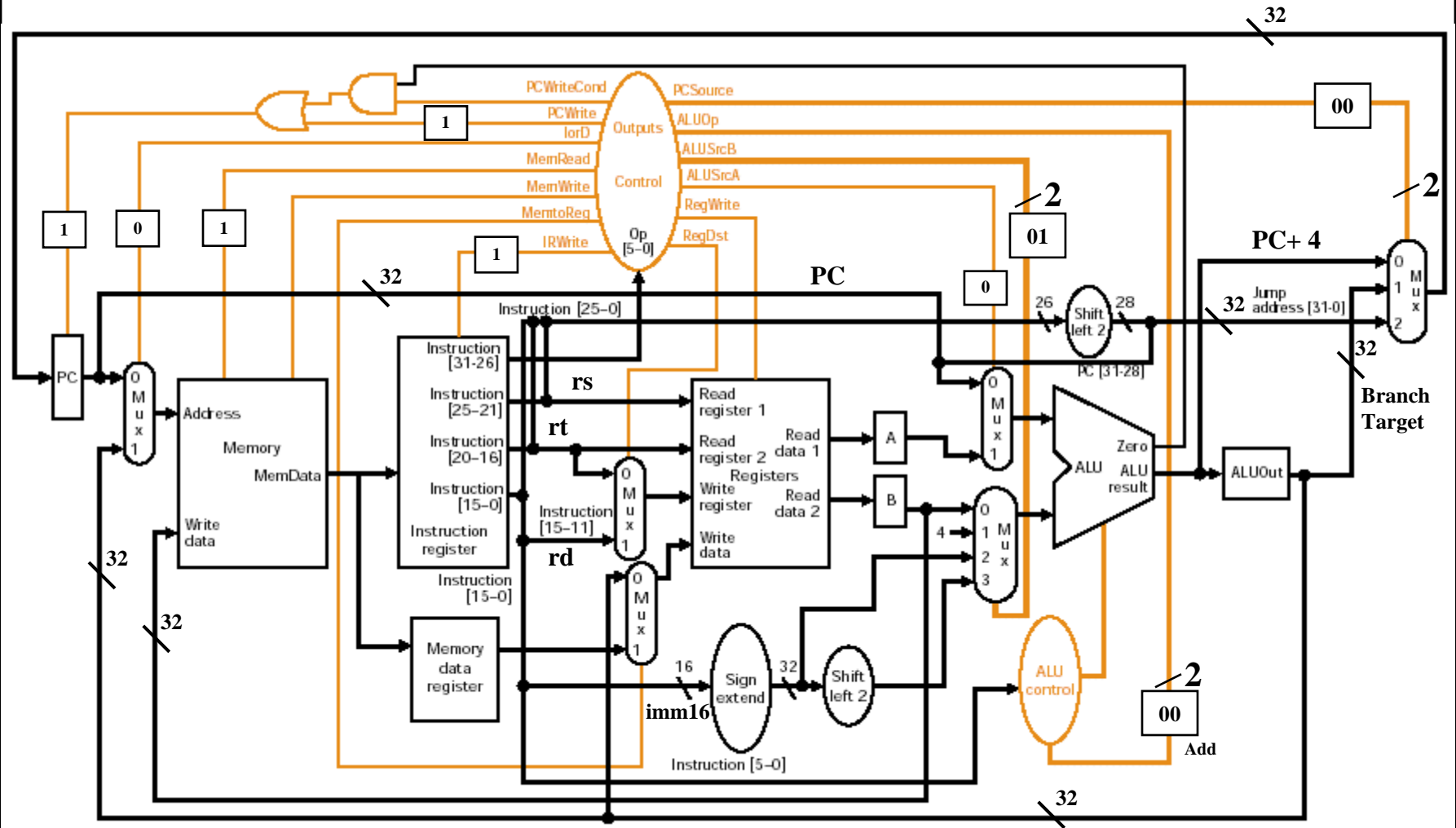

(ORI not supported, Jump supported)

Instruction Decode (ID) Cycle (State 1)

$A \leftarrow R[rs]$


$B \leftarrow R[rt]$

$ALUout \leftarrow PC + (\text{SignExt}(\text{imm16}) \times 4)$ (Calculate branch target)

ALUSrcA = 0


ALUSrcB = 11

ALUOp = 00 (add)

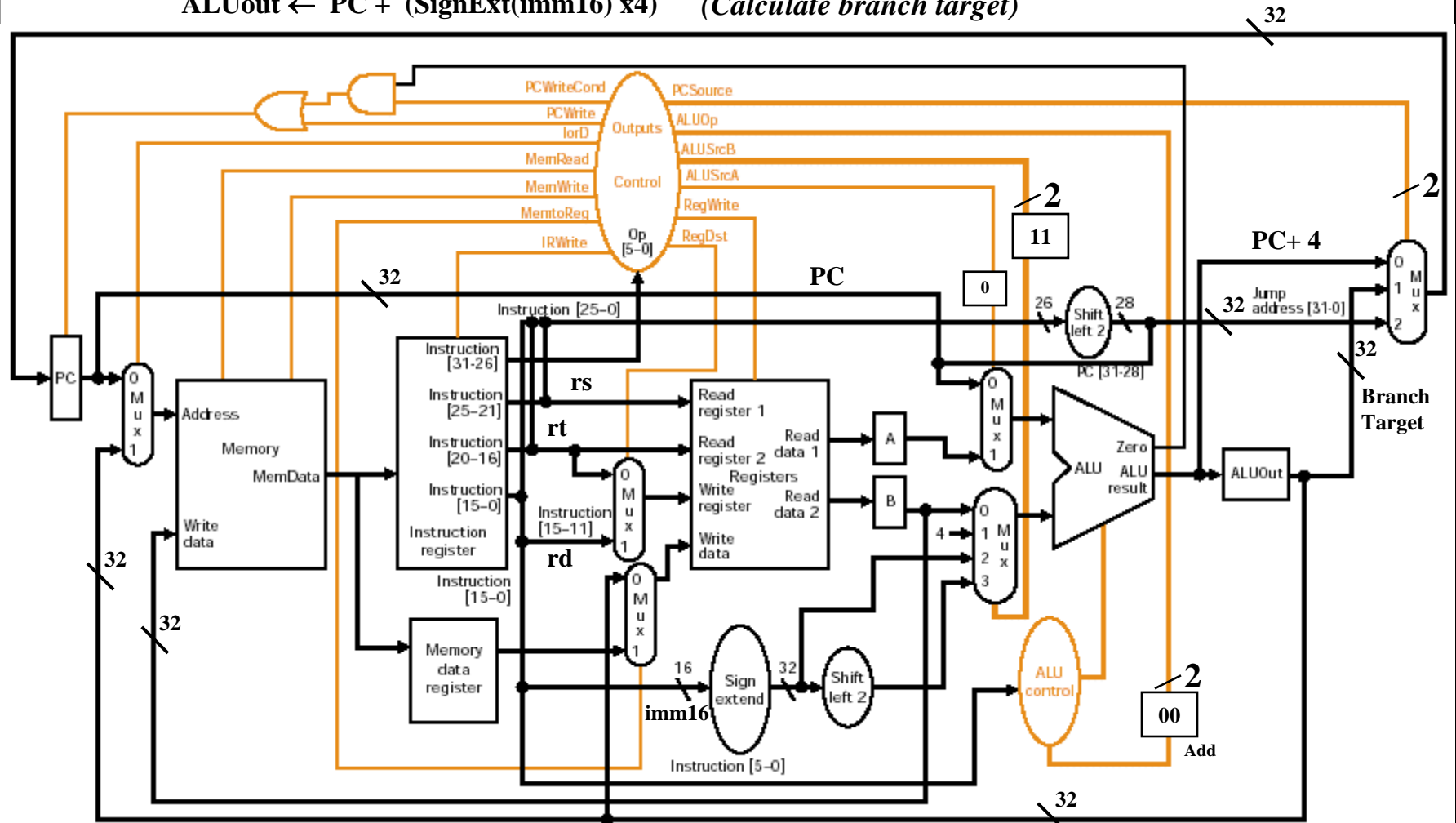

(ORI not supported, Jump supported)

Load/Store Instructions FSM States

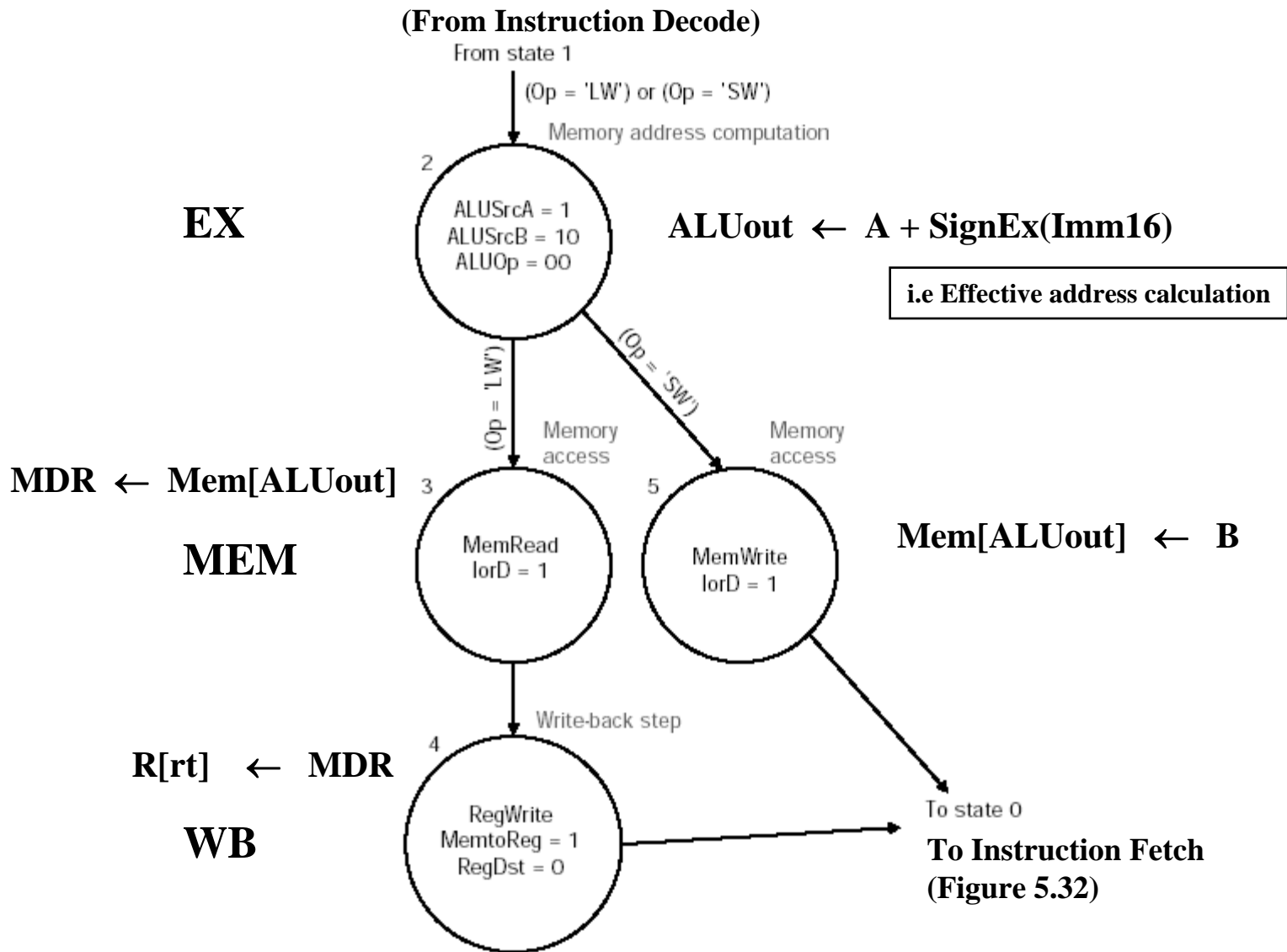

(Figure 5.33 page 334)

Load/Store Execution (EX) Cycle (State 2)


Effective address calculation

$$\text{ALUout} \leftarrow A + \text{SignEx}(\text{Imm16})$$

ALUSrcA = 1

ALUSrcB = 10

ALUOp = 00 (add)

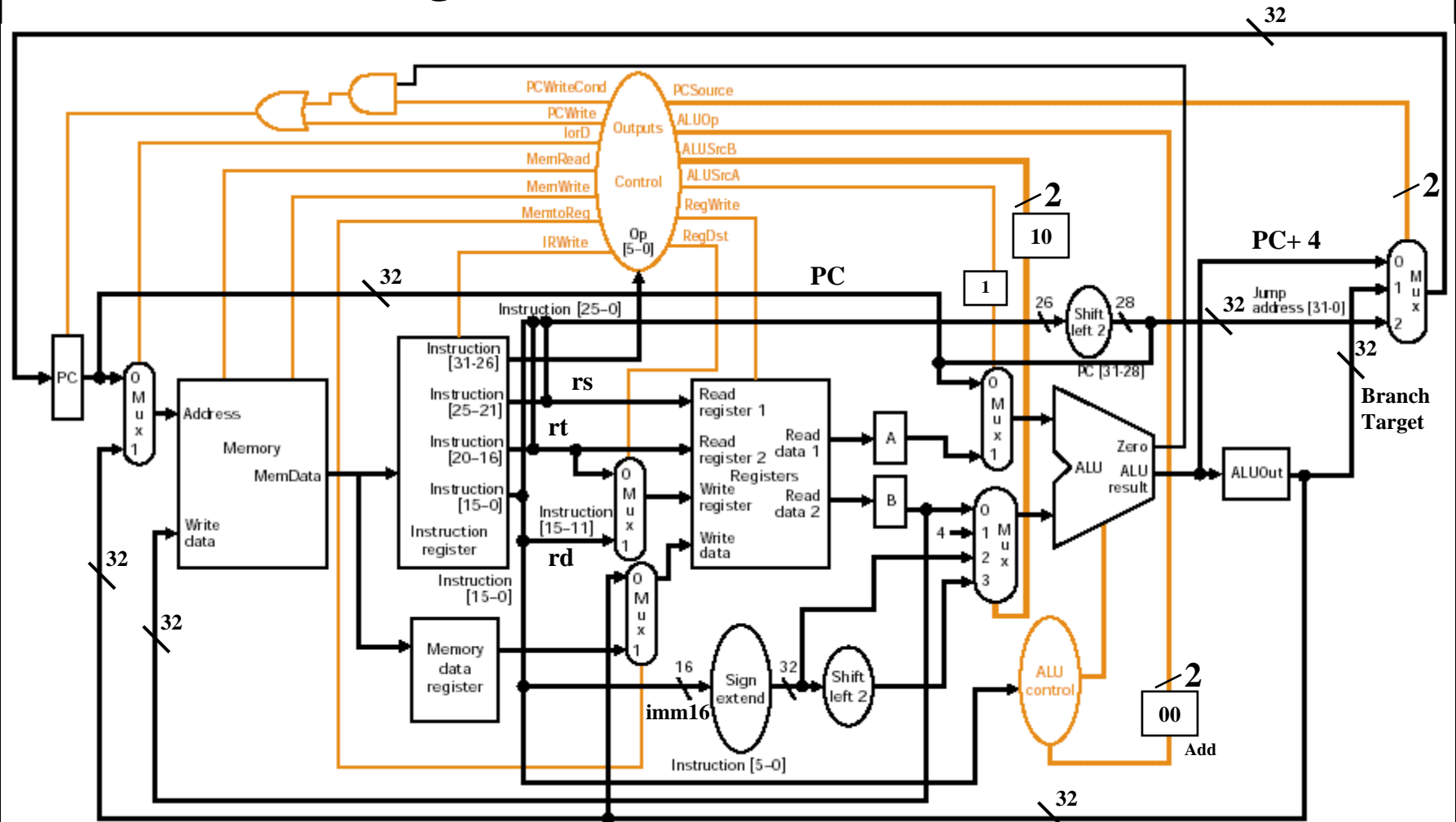

(ORI not supported, Jump supported)


EECC550 - Shaaban

(Figure 5.28 page 323)

Load Memory (MEM) Cycle (State 3)

$MDR \leftarrow Mem[ALUout]$

$MemRead = 1 \quad IorD = 1$

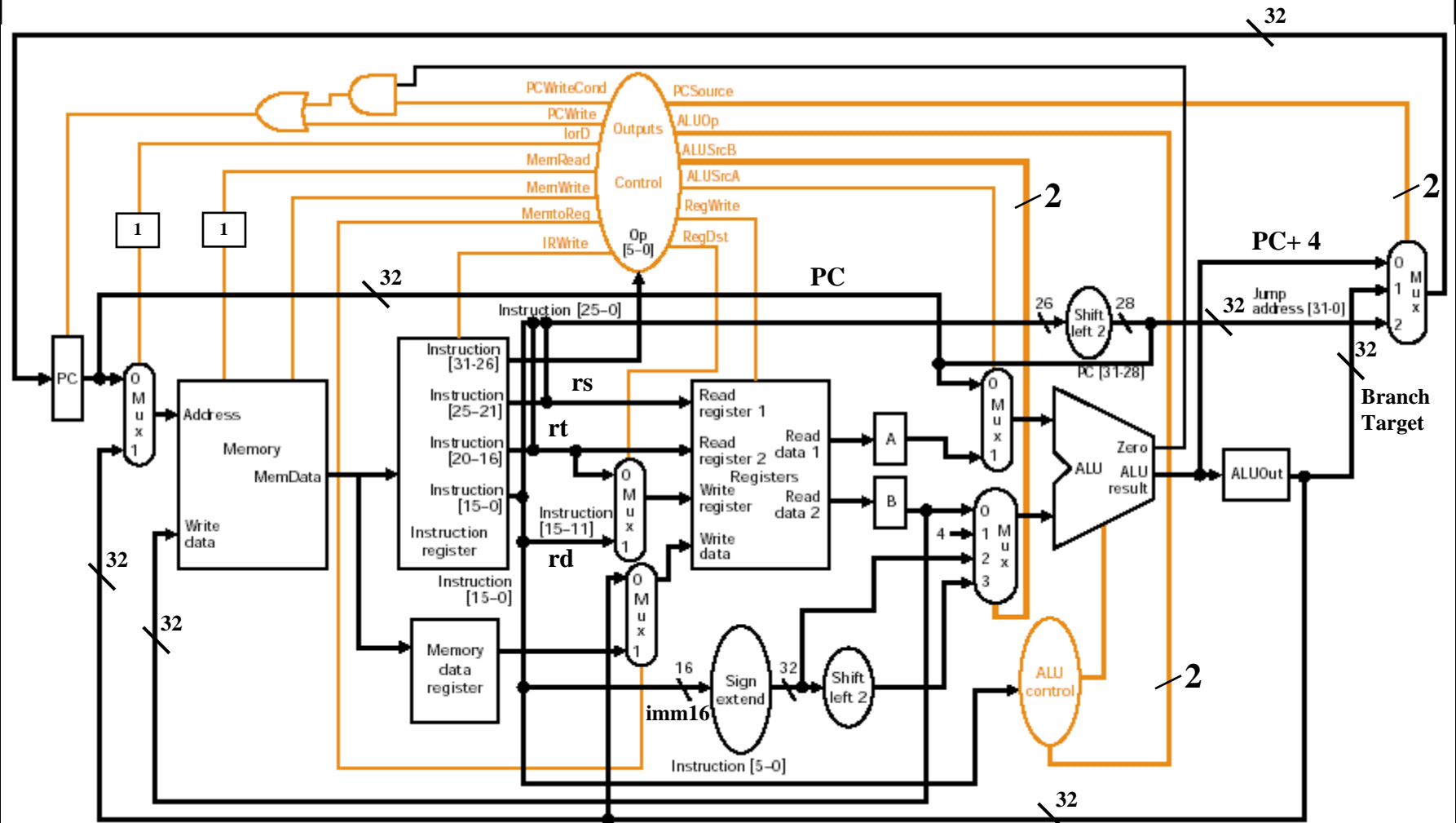

(ORI not supported, Jump supported)


EECC550 - Shaaban

(Figure 5.28 page 323)

Load Write Back (WB) Cycle (State 4)

$R[rt] \leftarrow MDR$

RegWrite = 1 MemtoReg = 1 RegDst = 0

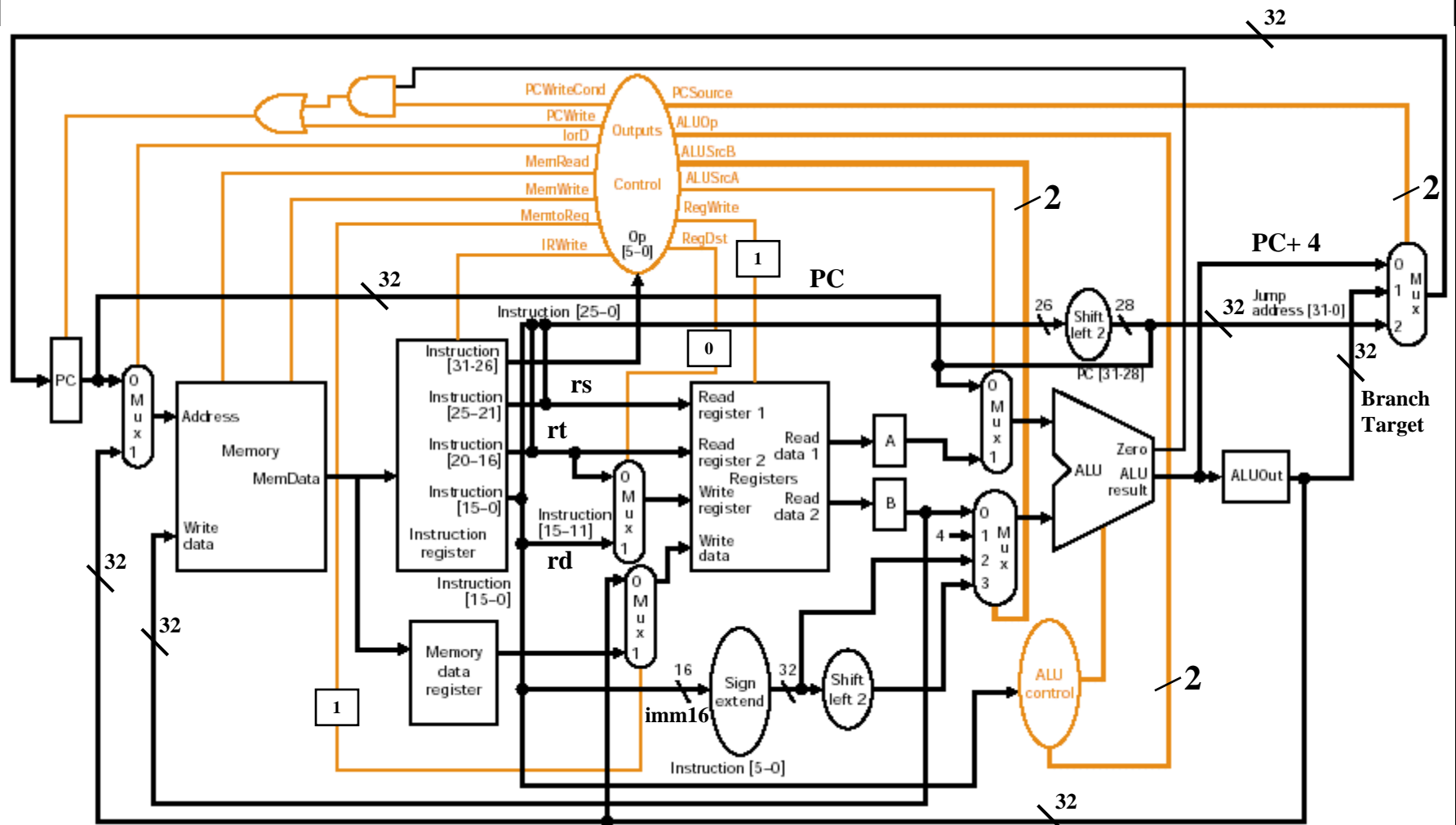


(ORI not supported, Jump supported)

Store Memory (MEM) Cycle (State 5)

Mem[ALUout] ← B

MemWrite = 1 IorD = 1

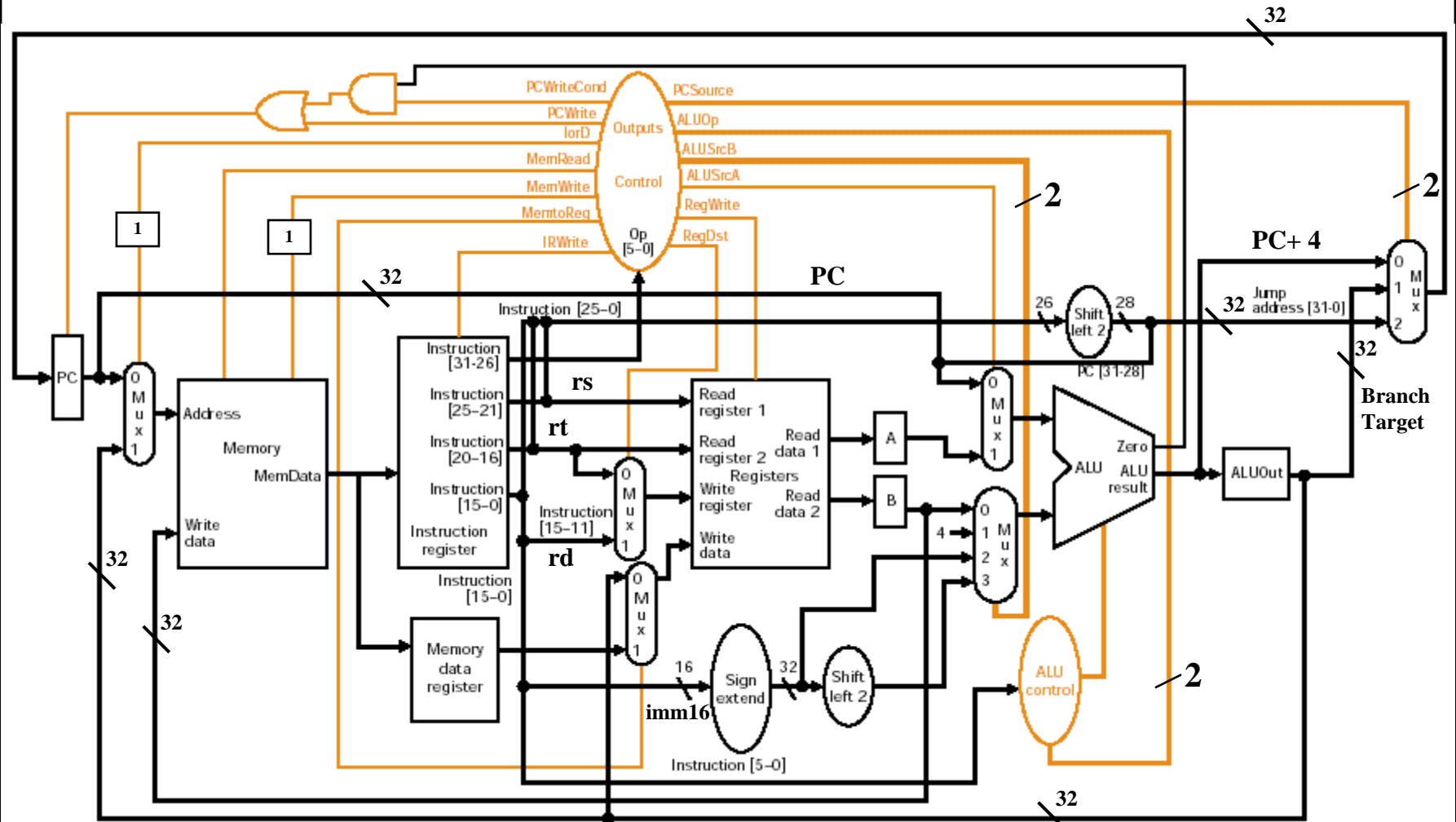


(ORI not supported, Jump supported)

EECC550 - Shaaban

(Figure 5.28 page 323)

R-Type Instructions FSM States

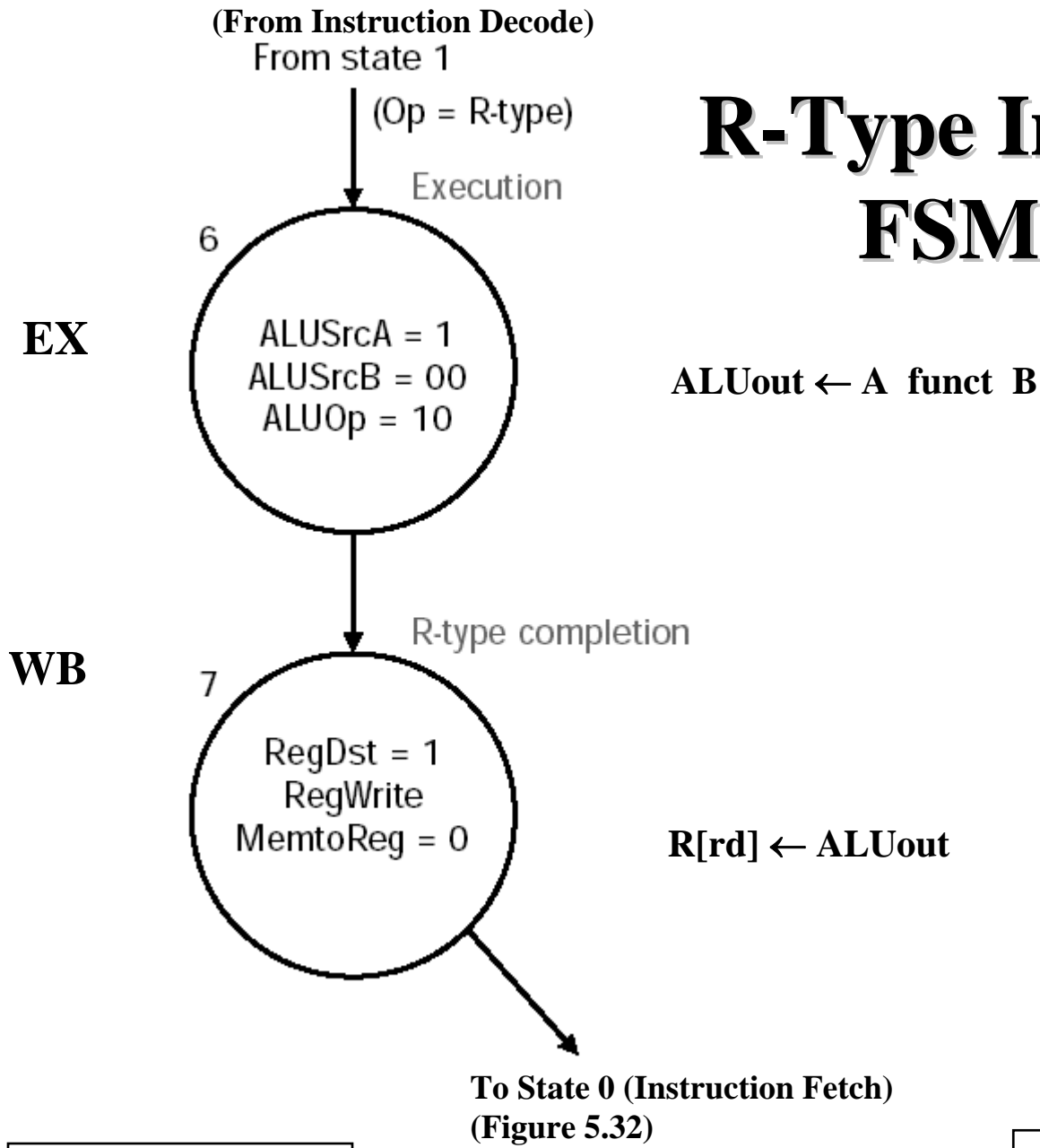


(Figure 5.34 page 335)

EECC550 - Shaaban

R-Type Execution (EX) Cycle (State 6)

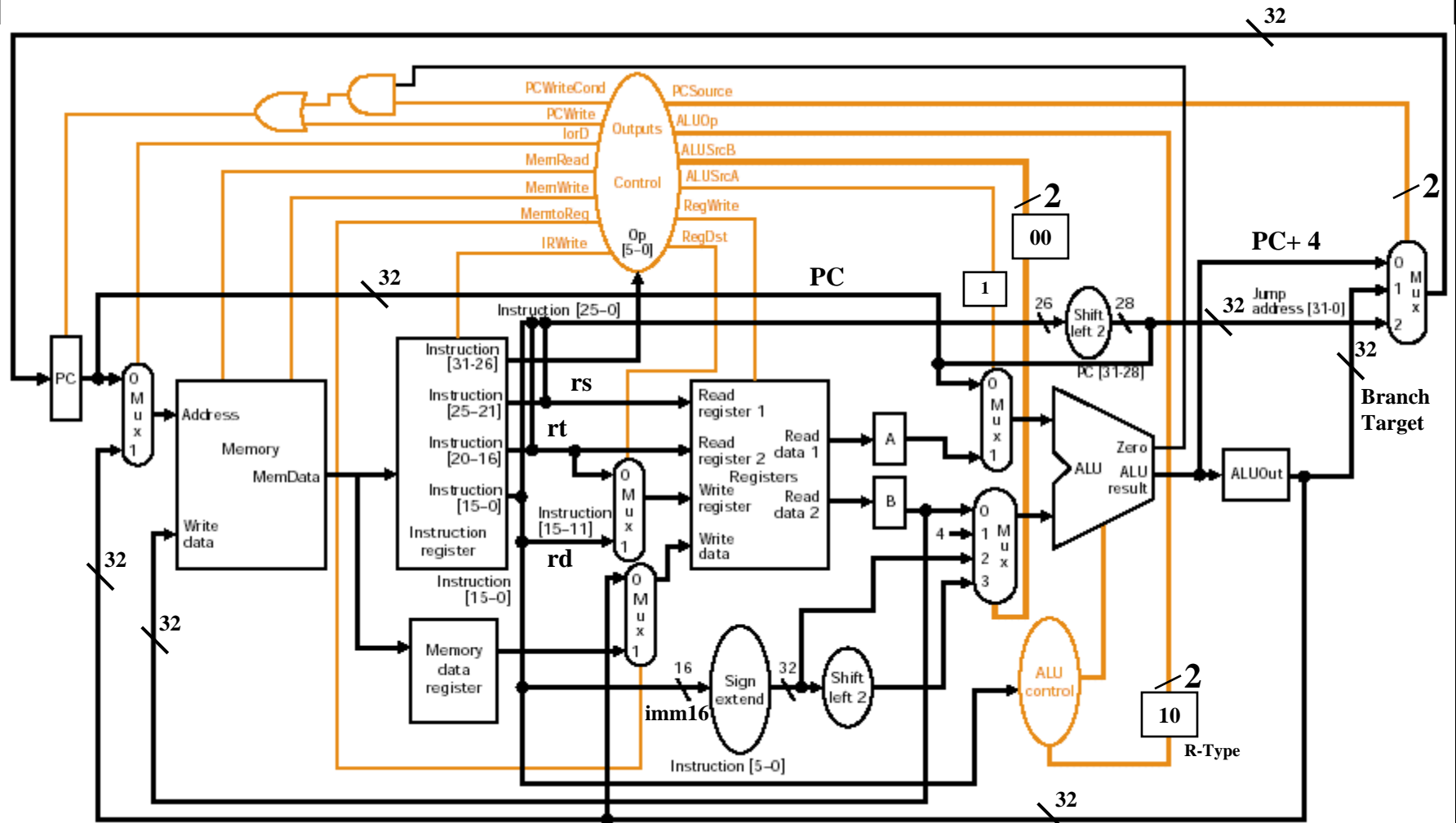$ALUout \leftarrow A \text{ funct } B$ $ALUSrcA = 1$ $ALUSrcB = 00$ $ALUOp = 10$ (R-Type)



(ORI not supported, Jump supported)

EECC550 - Shaaban

(Figure 5.28 page 323)


R-Type Write Back (WB) Cycle (State 7)

$R[rd] \leftarrow ALUout$

RegWrite = 1

MemtoReg = 0

RegDst = 1

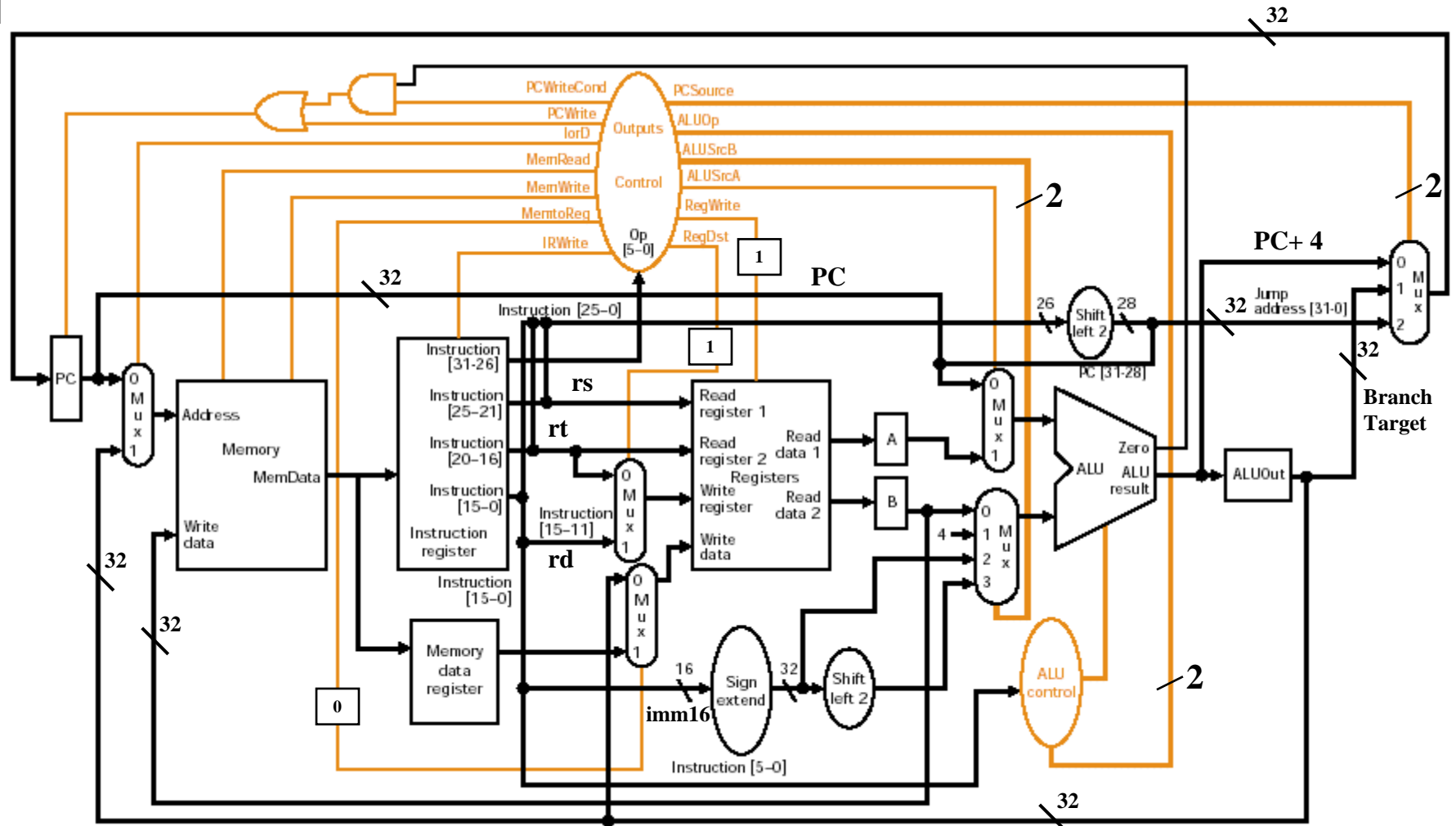


(ORI not supported, Jump supported)

EECC550 - Shaaban

(Figure 5.28 page 323)


#40 Lec # 5 Winter 2012 12-18-2012

Branch Instruction Single EX State

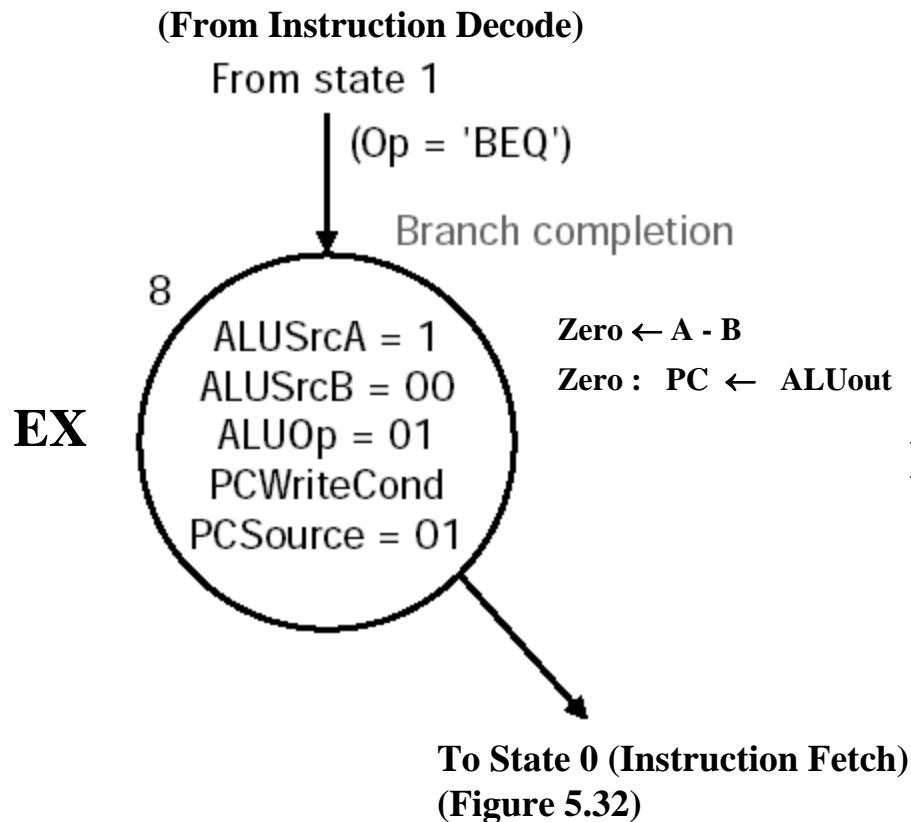

(Figures 5.35, 5.36 page 337)

Jump Instruction Single EX State

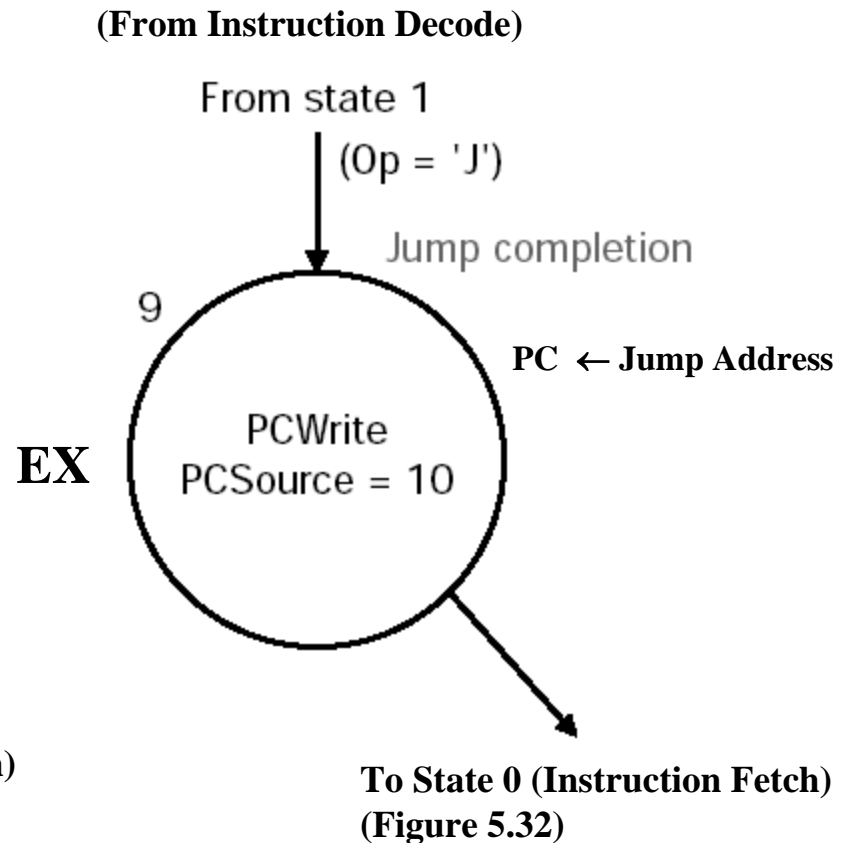

EECC550 - Shaaban

Branch Execution (EX) Cycle (State 8)

Zero ← A - B

Zero : PC ← ALUout


ALUSrcA = 1

ALUSrcB = 00

ALUOp = 01 (Subtract)

PCWriteCond = 1

PCSource = 01

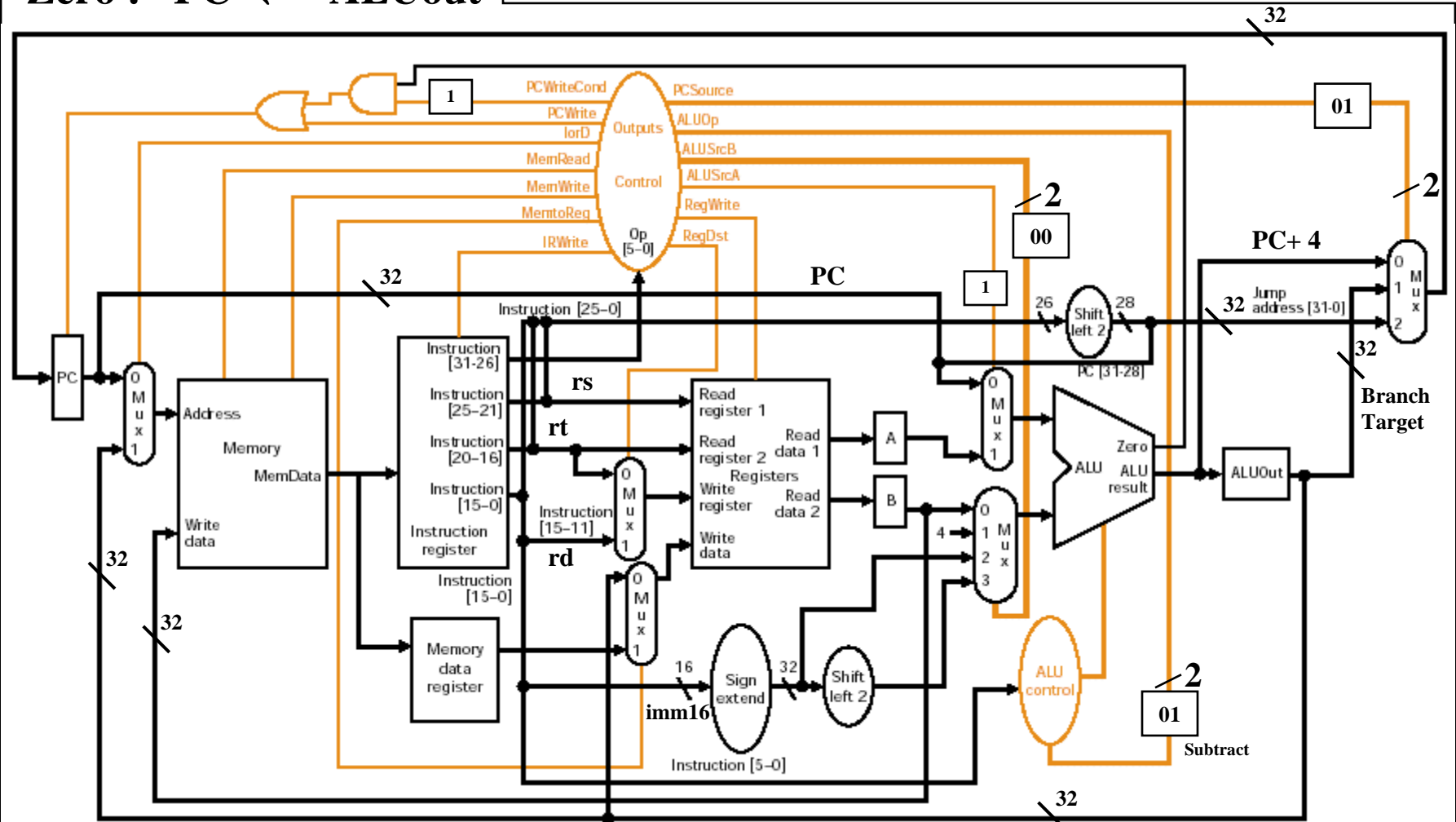

(ORI not supported, Jump supported)

EECC550 - Shaaban


(Figure 5.28 page 323)

Jump Execution (EX) Cycle (State 9)

$PC \leftarrow \text{Jump Address}$

PCWrite = 1

PCSource = 10

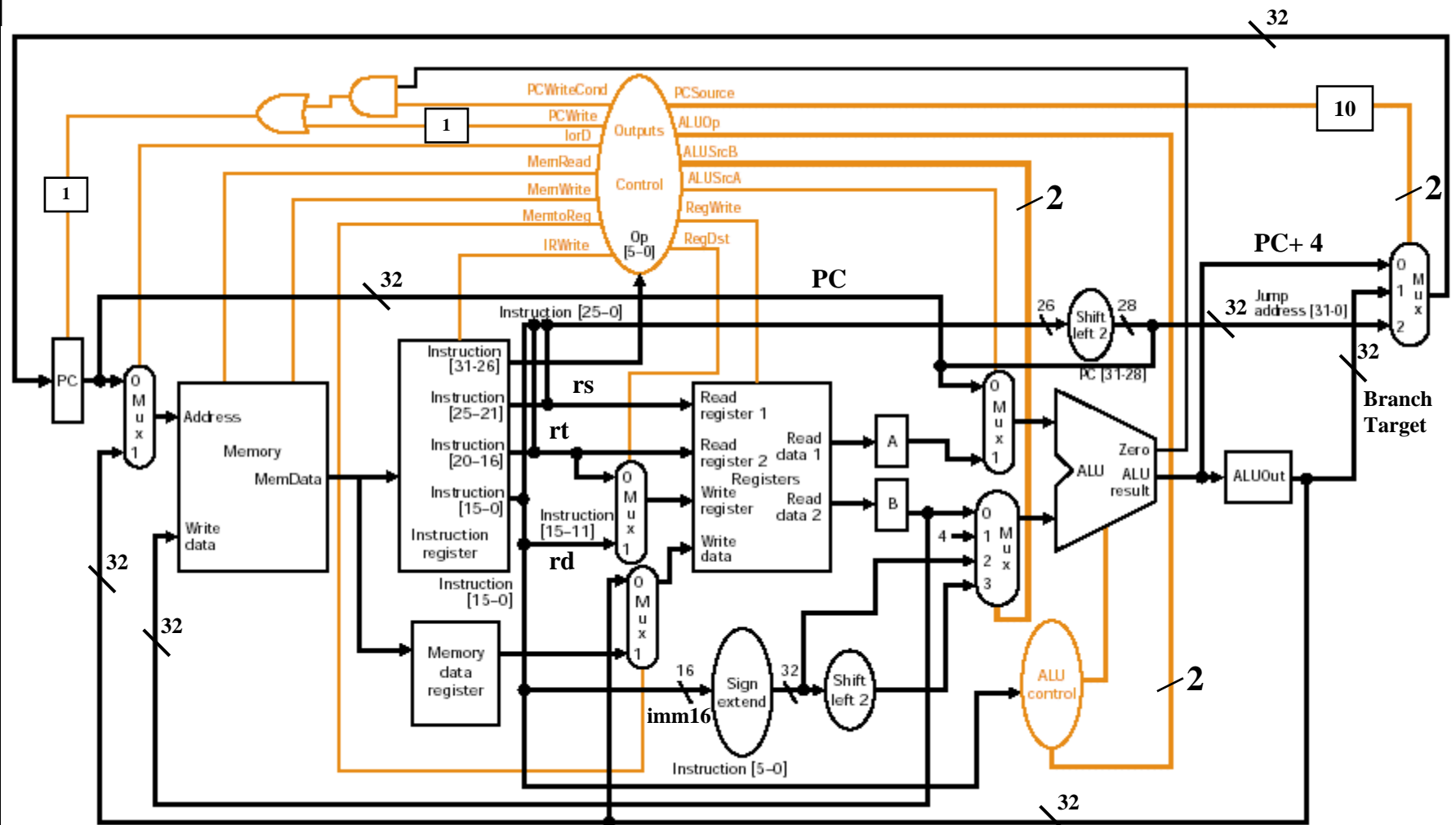

(ORI not supported, Jump supported)

EECC550 - Shaaban

(Figure 5.28 page 323)

MIPS Multi-cycle Datapath Performance Evaluation

$$1 \leq \text{CPI} \leq 5$$

- What is the average CPI?
 - State diagram gives CPI for each instruction type.
 - Workload (program) below gives frequency of each type.

| Type | CPI _i for type | Frequency | CPI _i x frequ _i |
|--------------|---------------------------|-----------|---------------------------------------|
| Arith/Logic | 4 | 40% | 1.6 |
| Load | 5 | 30% | 1.5 |
| Store | 4 | 10% | 0.4 |
| branch | 3 | 20% | 0.6 |
| Average CPI: | | | 4.1 |

Better than CPI = 5 if all instructions took the same number of clock cycles (5).

$$C = 2 \text{ ns } f = 500 \text{ MHz}$$

$$T = I \times \text{CPI} \times C$$

EECC550 - Shaaban

Adding Support for swap to Multi Cycle Datapath

- You are to add support for a new instruction, swap that exchanges the values of two registers to the MIPS multicyle datapath of Figure 5.28 on page 232

swap \$rs, \$rt

i.e. $R[rt] \leftarrow R[rs]$

$R[rs] \leftarrow R[rt]$

- Swap used the R-Type format with:

the value of field rs = the value of field rd

- Add any necessary datapaths and control signals to the multicyle datapath. Find a solution that minimizes the number of clock cycles required for the new instruction without modifying the register file. Justify the need for the modifications, if any.

i.e No additional register write ports

- Show the necessary modifications to the multicyle control finite state machine of Figure 5.38 on page 339 when adding the swap instruction. For each new state added, provide the dependent RTN and active control signal values.



Adding swap Instruction Support to Multi Cycle Datapath

Swap \$rs, \$rt

$R[rt] \leftarrow R[rs]$


$R[rs] \leftarrow R[rt]$

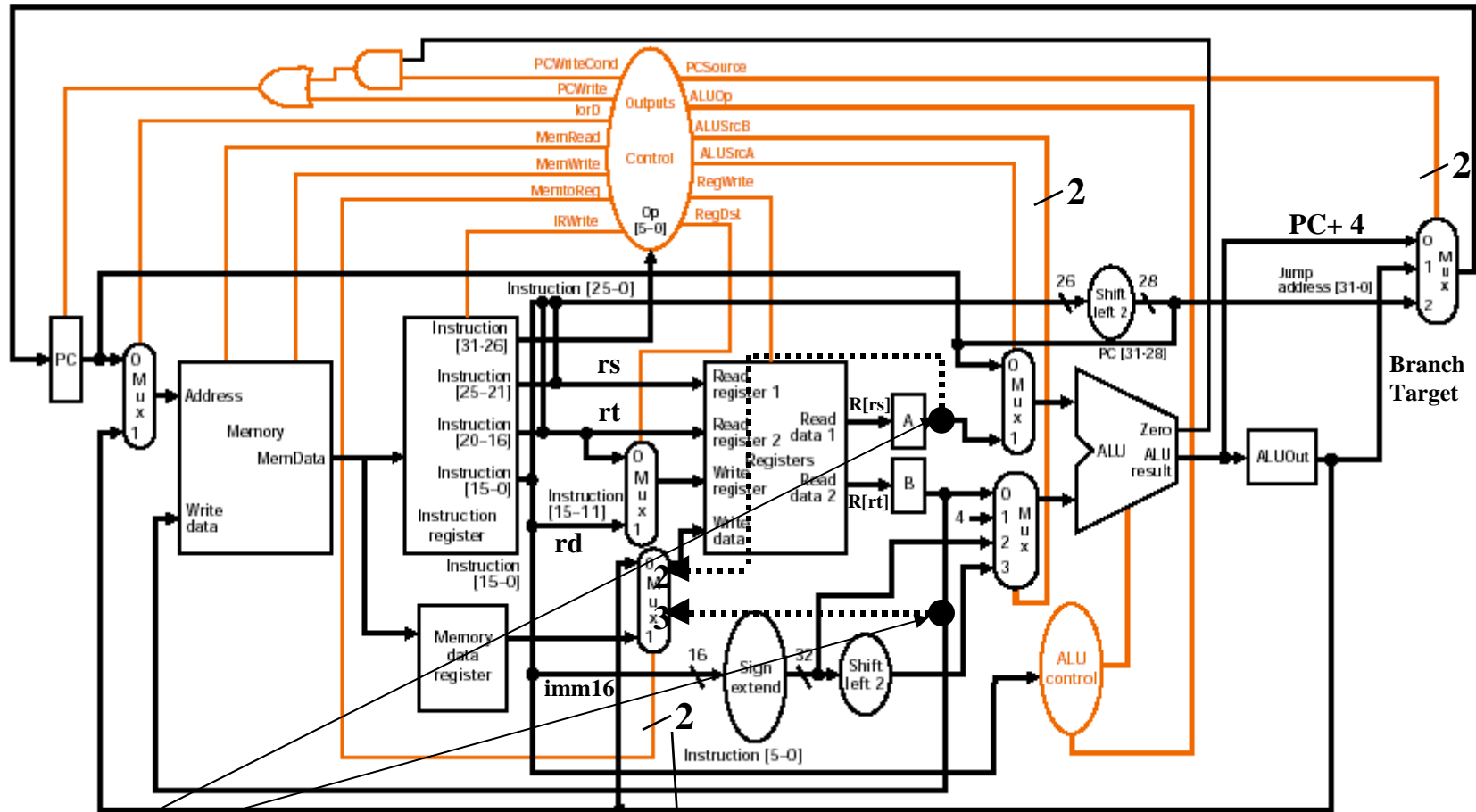 We assume here $rs = rd$ in instruction encoding



The outputs of A and B should be connected to the multiplexor controlled by MemtoReg if one of the two fields (rs and rd) contains the name of one of the registers being swapped. The other register is specified by rt. The MemtoReg control signal becomes two bits.

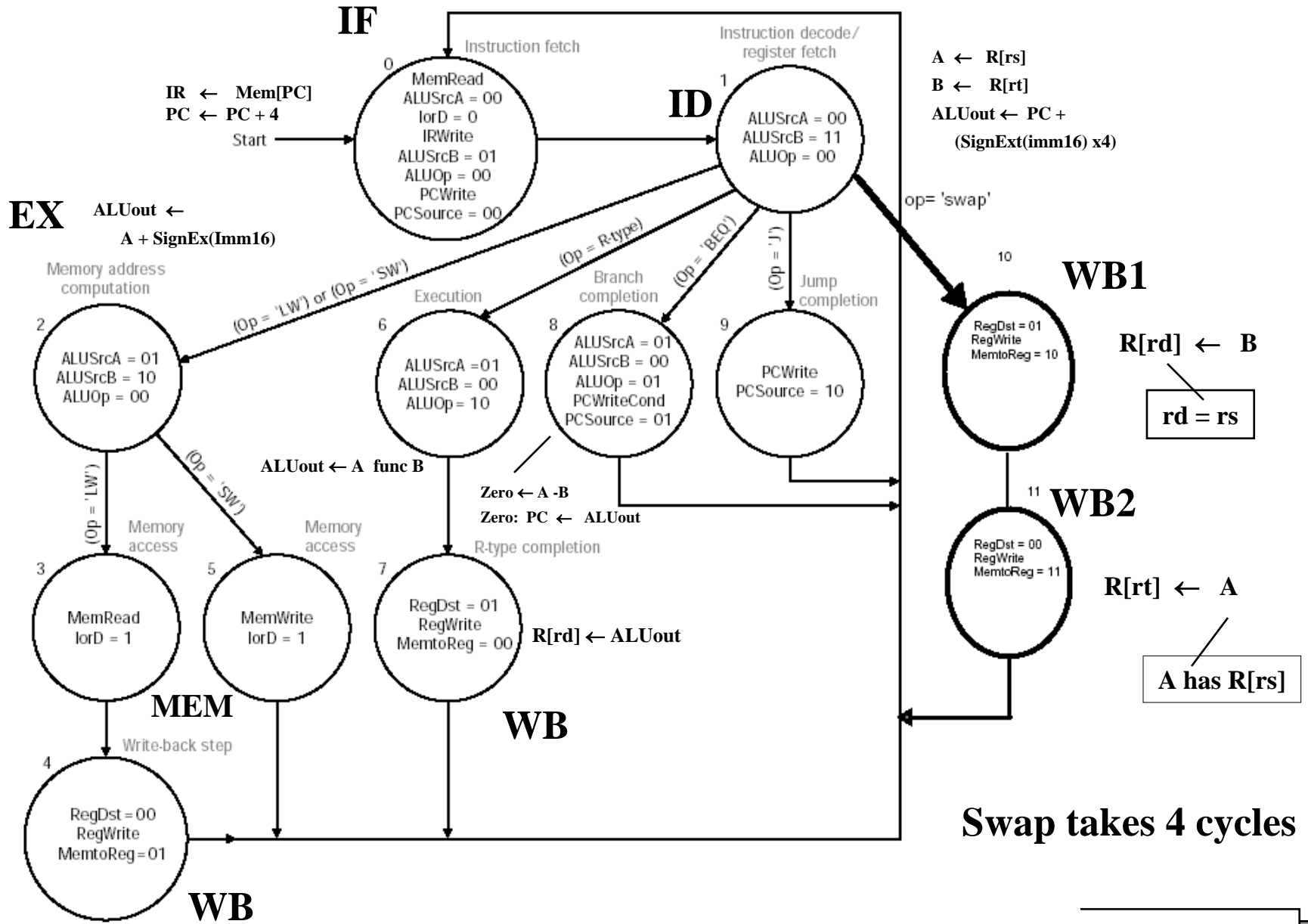Adding swap Instruction Support to Multi Cycle Datapath




Adding Support for add3 to Multi Cycle Datapath

- You are to add support for a new instruction, add3, that adds the values of three registers, to the MIPS multicycle datapath of Figure 5.28 on page 232
For example:

add3 \$s0,\$s1, \$s2, \$s3

Register \$s0 gets the sum of \$s1, \$s2 and \$s3.

 The instruction encoding uses a modified R-format, with an additional register specifier rx added replacing the five low bits of the “funct” field.



- Add necessary datapath components, connections, and control signals to the multicycle datapath without modifying the register bank or adding additional ALUs. Find a solution that minimizes the number of clock cycles required for the new instruction. Justify the need for the modifications, if any.
- Show the necessary modifications to the multicycle control finite state machine of Figure 5.38 on page 339 when adding the add3 instruction. For each new state added, provide the dependent RTN and active control signal values.

add3 instruction support to Multi Cycle Datapath



Add3 \$rd, \$rs, \$rt, \$rx

$$R[rd] \leftarrow R[rs] + R[rt] + R[rx]$$

rx is a new register specifier in field [0-4] of the instruction

No additional register read ports or ALUs allowed

Modified
R-Format

  

1. ALUOut is added as an extra input to first ALU operand MUX to use the previous ALU result as an input for the second addition.
2. A multiplexor should be added to select between rt and the new field rx containing register number of the 3rd operand (bits 4-0 for the instruction) for input for Read Register 2. This multiplexor will be controlled by a new one bit control signal called ReadSrc.

3. WriteB control line added to enable writing R[rx] to B

EECC550 - Shaaban

add3 instruction support to Multi Cycle Datapath

IF

